

## Problem Solutions

- 18.1 From  $\Delta V = I(R + r)$ , the internal resistance is

$$r = \frac{\Delta V}{I} - R = \frac{9.00 \text{ V}}{0.117 \text{ A}} - 72.0 \Omega = \boxed{4.92 \Omega}$$

- 18.2 (a)  $R_{eq} = R_1 + R_2 + R_3 = 4.0 \Omega + 8.0 \Omega + 12 \Omega = \boxed{24 \Omega}$

- (b) The same current exists in all resistors in a series combination.

$$I = \frac{\Delta V}{R_{eq}} = \frac{24 \text{ V}}{24 \Omega} = \boxed{1.0 \text{ A}}$$

- (c) If the three resistors were connected in parallel,

$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = \left( \frac{1}{4.0 \Omega} + \frac{1}{8.0 \Omega} + \frac{1}{12 \Omega} \right)^{-1} = \boxed{2.18 \Omega}$$

Resistors in parallel have the same potential difference across them, so

$$I_4 = \frac{\Delta V}{R_4} = \frac{24 \text{ V}}{4.0 \Omega} = 6.0 \text{ A}, \quad I_8 = \frac{24 \text{ V}}{8.0 \Omega} = 3.0 \text{ A}, \quad \text{and} \quad I_{12} = \frac{24 \text{ V}}{12 \Omega} = \boxed{2.0 \text{ A}}$$

- 18.3 For the bulb in use as intended,


$$R_{\text{bulb}} = \frac{(\Delta V)^2}{\mathcal{P}} = \frac{(120 \text{ V})^2}{75.0 \text{ W}} = 192 \Omega$$

Now, presuming the bulb resistance is unchanged, the current in the circuit shown is

$$I = \frac{\Delta V}{R_{eq}} = \frac{120 \text{ V}}{0.800 \Omega + 192 \Omega + 0.800 \Omega} = 0.620 \text{ A},$$

and the actual power dissipated in the bulb is
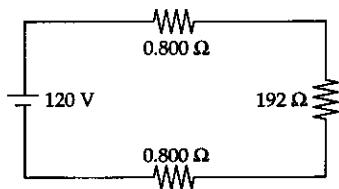
$$\mathcal{P} = I^2 R_{\text{bulb}} = (0.620 \text{ A})^2 (192 \Omega) = \boxed{73.8 \text{ W}}$$



- 18.4 (a) The current through this series combination is


$$I = \frac{(\Delta V)_{bc}}{R_{bc}} = \frac{12 \text{ V}}{6.0 \Omega} = 2.0 \text{ A}$$

Therefore, the terminal potential difference of the power supply is

$$\Delta V = IR_{eq} = (2.0 \text{ A})(9.0 \Omega + 6.0 \Omega) = \boxed{30 \text{ V}}$$

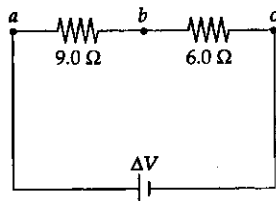- (b) When connected in parallel, the potential difference across either resistor is the voltage setting of the power supply. Thus,

$$\Delta V = I_y R_y = (0.25 \text{ A})(9.0 \Omega) = \boxed{2.3 \text{ V}}$$



- 18.5 (a) The equivalent resistance of the two parallel resistors is

$$R_p = \left( \frac{1}{7.00 \Omega} + \frac{1}{10.0 \Omega} \right)^{-1} = 4.12 \Omega$$

Thus,


$$R_{ab} = R_4 + R_p + R_9 = (4.00 + 4.12 + 9.00) \Omega = \boxed{17.1 \Omega}$$

- (b)
- $I_{ab} = \frac{(\Delta V)_{ab}}{R_{ab}} = \frac{34.0 \text{ V}}{17.1 \Omega} = 1.99 \text{ A}$
- , so
- $I_4 = I_9 = 1.99 \text{ A}$

Also,  $(\Delta V)_p = I_{ab} R_p = (1.99 \text{ A})(4.12 \Omega) = 8.18 \text{ V}$

Then,  $I_7 = \frac{(\Delta V)_p}{R_7} = \frac{8.18 \text{ V}}{7.00 \Omega} = \boxed{1.17 \text{ A}}$

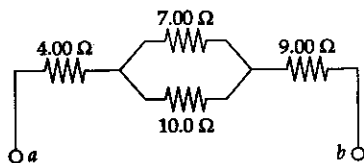and  $I_{10} = \frac{(\Delta V)_p}{R_{10}} = \frac{8.18 \text{ V}}{10.0 \Omega} = \boxed{0.818 \text{ A}}$




- 18.6 The equivalent resistance of the parallel combination of three resistors is

$$R_p = \left( \frac{1}{18 \Omega} + \frac{1}{9.0 \Omega} + \frac{1}{6.0 \Omega} \right)^{-1} = 3.0 \Omega$$

Hence, the equivalent resistance of the circuit connected to the 30 V source is

$$R_{eq} = R_{12} + R_p = 12 \Omega + 3.0 \Omega = \boxed{15 \Omega}$$

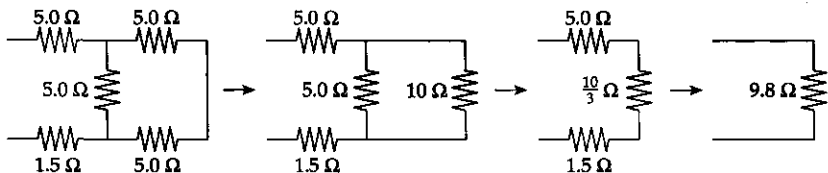- 18.7 The rules for combining resistors in series and parallel are used to reduce the circuit to an equivalent resistance in the stages shown below. The result is  $R_{eq} = \boxed{9.8 \Omega}$ .



- 18.8 (a) The rules for combining resistors in series and parallel are used to reduce the circuit to an equivalent resistor in the stages shown below. The result is  $R_{eq} = \boxed{5.13 \Omega}$ .

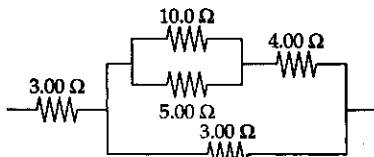


Figure 1

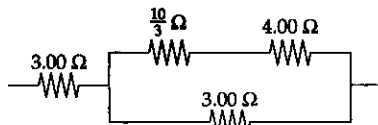


Figure 2

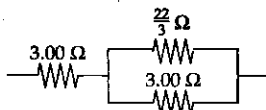


Figure 3

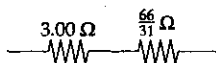


Figure 4

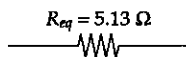


Figure 5

- (b) From  $\varphi = (\Delta V)^2 / R_{eq}$ , the emf of the power source is

$$\Delta V = \sqrt{\varphi \cdot R_{eq}} = \sqrt{(4.00 \text{ W})(5.13 \Omega)} = \boxed{4.53 \text{ V}}$$

- 18.9** Turn the circuit given in Figure P18.9 90° counterclockwise to observe that it is equivalent to that shown in Figure 1 below. This reduces, in stages, as shown in the following figures.

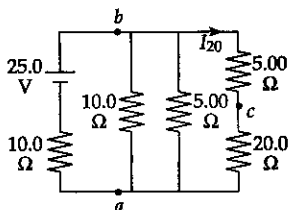


Figure 1

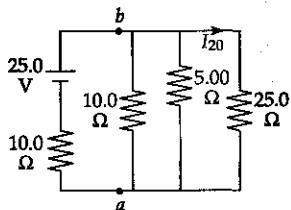


Figure 2

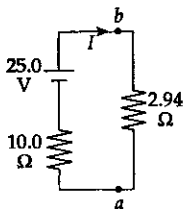


Figure 3

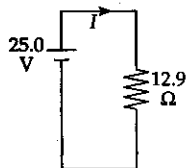


Figure 4

From Figure 4,

$$I = \frac{\Delta V}{R} = \frac{25.0 \text{ V}}{12.9 \Omega} = 1.93 \text{ A}$$

(b) From Figure 3,

$$\begin{aligned} (\Delta V)_{ba} &= IR_{ba} \\ &= (1.93 \text{ A})(2.94 \Omega) = \boxed{5.68 \text{ V}} \end{aligned}$$

(a) From Figures 1 and 2, the current through the 20.0 Ω resistor is

$$I_{20} = \frac{(\Delta V)_{ba}}{R_{\text{box}}} = \frac{5.68 \text{ V}}{25.0 \Omega} = \boxed{0.227 \text{ A}}$$

- 18.10 First, consider the parallel case. The resistance of resistor B is

$$R_B = \frac{(\Delta V)_B}{I_B} = \frac{6.0 \text{ V}}{2.0 \text{ A}} = \boxed{3.0 \Omega}$$

In the series combination, the potential difference across B is given by

$$(\Delta V)_B = (\Delta V)_{\text{battery}} - (\Delta V)_A = 6.0 \text{ V} - 4.0 \text{ V} = 2.0 \text{ V}$$

The current through the series combination is then

$$I_s = \frac{(\Delta V)_B}{R_B} = \frac{2.0 \text{ V}}{3.0 \Omega} = \frac{2}{3} \text{ A},$$

and the resistance of resistor A is  $R_A = \frac{(\Delta V)_A}{I_s} = \frac{4.0 \text{ V}}{2/3 \text{ A}} = \boxed{6.0 \Omega}$

- 18.11 The equivalent resistance is  $R_{eq} = R + R_p$ , where  $R_p$  is the total resistance of the three parallel branches;

$$R_p = \left( \frac{1}{120 \Omega} + \frac{1}{40 \Omega} + \frac{1}{R + 5.0 \Omega} \right)^{-1} = \left( \frac{1}{30 \Omega} + \frac{1}{R + 5.0 \Omega} \right)^{-1} = \frac{(30 \Omega)(R + 5.0 \Omega)}{R + 35 \Omega}$$


$$\text{Thus, } 75 \Omega = R + \frac{(30 \Omega)(R + 5.0 \Omega)}{R + 35 \Omega} = \frac{R^2 + (65 \Omega)R + 150 \Omega^2}{R + 35 \Omega},$$

which reduces to  $R^2 - (10 \Omega)R + 2475 \Omega^2 = 0$  or  $(R - 55 \Omega)(R + 45 \Omega) = 0$ .

Only the positive solution is physically acceptable, so  $R = \boxed{55 \Omega}$

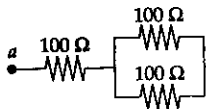- 18.12 (a) The total current from *a* to *b* is equal to the maximum current allowed in the  $100 \Omega$  series resistor adjacent to point *a*. This current has a value of

$$I_{\text{max}} = \sqrt{\frac{P_{\text{max}}}{R}} = \sqrt{\frac{25.0 \text{ W}}{100 \Omega}} = 0.500 \text{ A}$$



The total resistance is

$$R_{ab} = 100 \Omega + \left( \frac{1}{100 \Omega} + \frac{1}{100 \Omega} \right)^{-1} = 100 \Omega + 50.0 \Omega = 150 \Omega$$

Thus,  $(\Delta V)_{max} = I_{max} R_{ab} = (0.500 \text{ A})(150 \Omega) = \boxed{75.0 \text{ V}}$

- (b) The power dissipated in the series resistor is  $\phi_1 = I_{max}^2 R = \boxed{25.0 \text{ W}}$ , and the power dissipated in each of the identical parallel resistors is

$$\phi_2 = \phi_3 = (I_{max}/2)^2 R = (0.250 \text{ A})^2 (100 \Omega) = \boxed{6.25 \text{ W}}$$

The total power delivered is

$$\phi = \phi_1 + \phi_2 + \phi_3 = (25.0 + 6.25 + 6.25) \text{ W} = \boxed{37.5 \text{ W}}$$

- 18.13 The resistors in the circuit can be combined in the stages shown below to yield an equivalent resistance of  $R_{ad} = (63/11) \Omega$ .

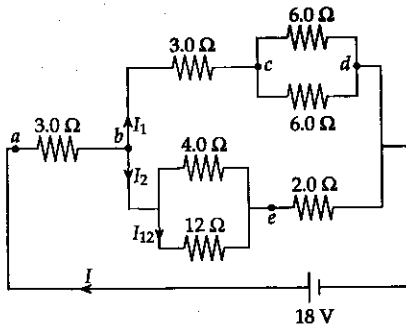


Figure 1

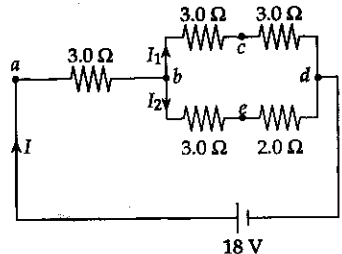


Figure 2

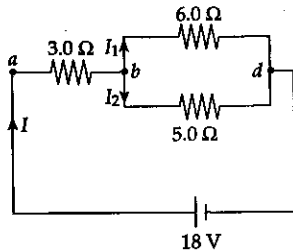


Figure 3

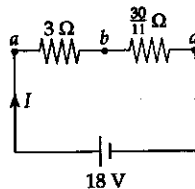


Figure 4

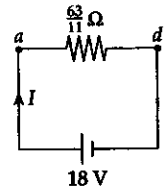


Figure 5

From Figure 5,  $I = \frac{(\Delta V)_{ad}}{R_{ad}} = \frac{18 \text{ V}}{(63/11) \Omega} = 3.14 \text{ A}$ .

Then, from Figure 4,  $(\Delta V)_{bd} = IR_{bd} = (3.14 \text{ A})(30/11 \Omega) = 8.57 \text{ V}$ .

Now, look at Figure 2 and observe that

$$I_2 = \frac{(\Delta V)_{bd}}{3.0 \Omega + 2.0 \Omega} = \frac{8.57 \text{ V}}{5.0 \Omega} = 1.71 \text{ A},$$

so  $(\Delta V)_{be} = I_2 R_{be} = (1.71 \text{ A})(3.0 \Omega) = 5.14 \text{ V}$

Finally, from Figure 1,  $I_{12} = \frac{(\Delta V)_{be}}{R_{12}} = \frac{5.14 \text{ V}}{12 \Omega} = \boxed{0.43 \text{ A}}$

- 18.14 The resistance of the parallel combination of the  $3.00 \Omega$  and  $1.00 \Omega$  resistors is

$$R_p = \left( \frac{1}{3.00 \Omega} + \frac{1}{1.00 \Omega} \right)^{-1} = 0.750 \Omega$$

The equivalent resistance of the circuit connected to the battery is

$$R_{eq} = 2.00 \Omega + R_p + 4.00 \Omega = 6.75 \Omega,$$

and the current supplied by the battery is



$$I = \frac{\Delta V}{R_{eq}} = \frac{18.0 \text{ V}}{6.75 \Omega} = 2.67 \text{ A}$$

The power dissipated in the  $2.00\text{-}\Omega$  resistor is

$$\phi_2 = I^2 R_2 = (2.67 \text{ A})^2 (2.00 \Omega) = \boxed{14.2 \text{ W}}$$

and that dissipated in the  $4.00\text{-}\Omega$  resistor is
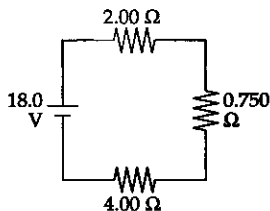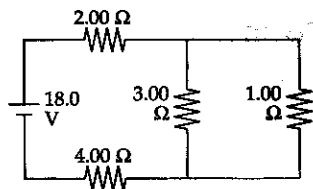
$$\phi_4 = I^2 R_4 = (2.67 \text{ A})^2 (4.00 \Omega) = \boxed{28.4 \text{ W}}$$



The potential difference across the parallel combination of the  $3.00\ \Omega$  and  $1.00\ \Omega$  resistors is

$$(\Delta V)_p = IR_p = (2.67\ \text{A})(0.750\ \Omega) = 2.00\ \text{V}$$

Thus, the power dissipation in these resistors is given by

$$P_3 = \frac{(\Delta V)_p^2}{R_3} = \frac{(2.00\ \text{V})^2}{3.00\ \Omega} = \boxed{1.33\ \text{W}}$$

and 
$$P_1 = \frac{(\Delta V)_p^2}{R_1} = \frac{(2.00\ \text{V})^2}{1.00\ \Omega} = \boxed{4.00\ \text{W}}$$

- 18.15 (a) Connect two  $50\text{-}\Omega$  resistors in parallel to get  $25\ \Omega$ . Then connect that combination in series with a  $20\text{-}\Omega$  resistor for a total resistance of  $45\ \Omega$ .
- (b) Connect two  $50\text{-}\Omega$  resistors in parallel to get  $25\ \Omega$ , and connect two  $20\text{-}\Omega$  resistors in parallel to get  $10\ \Omega$ . Then connect these two combinations in series to obtain  $35\ \Omega$ .

- 18.16 Going counterclockwise around the upper loop, applying Kirchoff's loop rule, gives

$$+15.0\ \text{V} - (7.00)\ I_1 - (5.00)(2.00\ \text{A}) = 0,$$

or 
$$I_1 = \frac{15.0\ \text{V} - 10.0\ \text{V}}{7.00\ \Omega} = \boxed{0.714\ \text{A}}$$


From Kirchoff's junction rule,  $I_1 + I_2 - 2.00\ \text{A} = 0$ ,

so 
$$I_2 = 2.00\ \text{A} - I_1 = 2.00\ \text{A} - 0.714\ \text{A} = \boxed{1.29\ \text{A}}$$

Going around the lower loop in a clockwise direction gives

$$+\varepsilon - (2.00)\ I_2 - (5.00)(2.00\ \text{A}) = 0$$

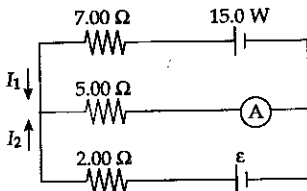or 
$$\varepsilon = (2.00\ \Omega)(1.29\ \text{A}) + (5.00\ \Omega)(2.00\ \text{A}) = \boxed{12.6\ \text{V}}$$





- 18.17 We name the currents  $I_1$ ,  $I_2$ , and  $I_3$  as shown. Using Kirchhoff's loop rule on the rightmost loop gives

$$+12.0 \text{ V} - (1.00 + 3.00)I_3 - (5.00 + 1.00)I_2 - 4.00 \text{ V} = 0$$

or  $(2.00)I_3 + (3.00)I_2 = 4.00 \text{ V}$  (1)

Applying the loop rule to the leftmost loop yields

$$+4.00 \text{ V} + (1.00 + 5.00)I_2 - (8.00)I_1 = 0,$$


or  $(4.00)I_1 - (3.00)I_2 = 2.00 \text{ V}$  (2)

From Kirchhoff's junction rule,  $I_1 + I_2 = I_3$  (3)


Solving equations (1), (2) and (3) simultaneously gives

$$I_1 = 0.846 \text{ A}, I_2 = 0.462 \text{ A}, \text{ and } I_3 = 1.31 \text{ A}$$

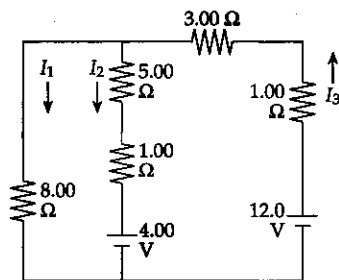All currents are in the directions indicated by the arrows in the circuit diagram.



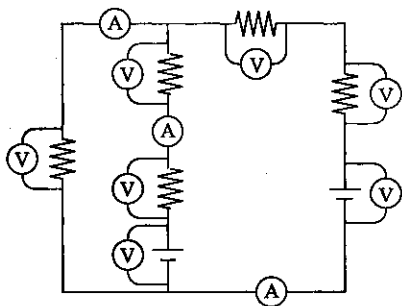- 18.18 The solution figure is shown to the right.



- 18.19 (a) Applying Kirchhoff's loop rule, as you go clockwise around the loop, gives

$$+20.0 \text{ V} - (2000)I - 30.0 \text{ V} - (2500)I + 25.0 \text{ V} - (500)I = 0,$$

or  $I = 3.00 \times 10^{-3} \text{ A} = \boxed{3.00 \text{ mA}}$

- (b) Start at the grounded point and move up the left side, recording changes in potential as you go, to obtain

$$V_A = +20.0 \text{ V} - (2000 \Omega)(3.00 \times 10^{-3} \text{ A}) - 30.0 \text{ V} - (1000 \Omega)(3.00 \times 10^{-3} \text{ A})$$

$$\text{or } V_A = \boxed{-19.0 \text{ V}}$$

(c)  $(\Delta V)_{1500} = (1500 \Omega)(3.00 \times 10^{-3} \text{ A}) = \boxed{4.50 \text{ V}}$

(The upper end is at the higher potential.)

- 18.20 Following the path of  $I_1$  from  $a$  to  $b$ , and recording changes in potential gives

$$V_b - V_a = +24 \text{ V} - (6.0 \Omega)(3.0 \text{ A}) = +6.0 \text{ V}$$


Now, following the path of  $I_2$  from  $a$  to  $b$ , and recording changes in potential gives

$$V_b - V_a = -(3.0 \Omega)I_2 = +6.0 \text{ V}, \text{ or } I_2 = \boxed{-2.0 \text{ A}}$$

Thus,  $I_2$  is directed from from  $b$  toward  $a$  and has magnitude of 2.0 A.


Applying Kirchhoff's junction rule at point  $a$  gives
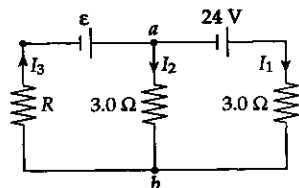
$$I_3 = I_1 + I_2 = 3.0 \text{ A} + (-2.0 \text{ A}) = \boxed{1.0 \text{ A}}$$



- 18.21 First simplify the circuit by combining the series resistors. Then, apply Kirchhoff's junction rule at point  $a$  to find

$$I_1 + I_2 = 2.00 \text{ A}$$

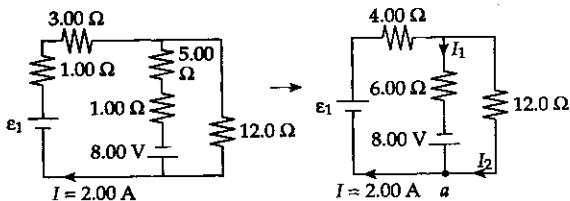

Next, we apply Kirchhoff's loop rule to the rightmost loop to obtain

$$-8.00 \text{ V} + (6.00)I_1 - (12.0)I_2 = 0,$$

or  $-8.00 \text{ V} + (6.00)I_1 - (12.0)(2.00 \text{ A} - I_1) = 0$  This yields  $I_1 = 1.78 \text{ A}$ .

Finally, apply Kirchhoff's loop rule to the leftmost loop to obtain

$$+\varepsilon_1 - (4.00)(2.00 \text{ A}) - (6.00)I_1 + 8.00 \text{ V} = 0,$$

or  $\varepsilon_1 = (4.00)(2.00 \text{ A}) + (6.00)(1.78 \text{ A}) - 8.00 \text{ V} = \boxed{10.7 \text{ V}}$

- 18.22 (a) The resistors can be combined as shown below to yield an equivalent of  $6.6 \Omega$ .

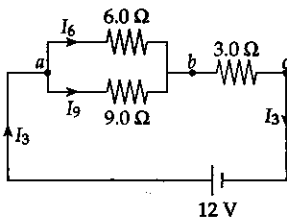


Figure 1

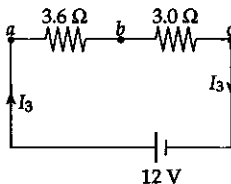


Figure 2

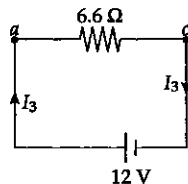


Figure 3

From Figure 3,  $I_3 = \frac{(\Delta V)_{ac}}{R_{ac}} = \frac{12 \text{ V}}{6.6 \Omega} = \boxed{1.8 \text{ A}}$

Then, from Figure 2,  $(\Delta V)_{ab} = I_3 R_{ab} = (1.82 \text{ A})(3.6 \Omega) = 6.6 \text{ V}$

From Figure 1,

$$I_6 = \frac{(\Delta V)_{ab}}{6.0 \Omega} = \frac{6.6 \text{ V}}{6.0 \Omega} = \boxed{1.1 \text{ A}} \text{ and } I_9 = \frac{(\Delta V)_{ab}}{9.0 \Omega} = \boxed{0.73 \text{ A}}$$

- (b) Using Figure 1 above, apply Kirchhoff's junction rule at point *a* to obtain

$$I_3 = I_6 + I_9 \quad (1)$$

Next, apply Kirchhoff's loop rule to the small loop containing the  $6.0\text{-}\Omega$  and  $9.0\text{-}\Omega$  resistors to find

$$-(6.0)I_6 + (9.0)I_9 = 0, \text{ or } I_9 = (2/3)I_6 \quad (2)$$

Finally, apply Kirchhoff's loop rule to the outside perimeter of Figure 1 to obtain

$$-(6.0)I_6 - (3.0)I_3 + 12 \text{ V} = 0, \text{ or } (2.0)I_6 + I_3 = 4.0 \text{ V} \quad (3)$$

Solving equations (1), (2), and (3) simultaneously yields

$$\boxed{I_3 = 1.8 \text{ A}, I_6 = 1.1 \text{ A}, I_9 = 0.73 \text{ A}}$$

- 18.23 (a) We name the currents  $I_1$ ,  $I_2$ , and  $I_3$  as shown.

Applying Kirchhoff's loop rule to loop  $abcfa$ , gives  $+\varepsilon_1 - \varepsilon_2 - R_2 I_2 - R_1 I_1 = 0$ ,

$$\text{or } 3I_2 + 2I_1 = 10.0 \text{ mA} \quad (1)$$

Applying the loop rule to loop  $edcfe$  yields

$$+\varepsilon_3 - R_3 I_3 - \varepsilon_2 - R_2 I_2 = 0,$$

$$\text{or } 3I_2 + 4I_3 = 20.0 \text{ mA} \quad (2)$$

Finally, applying Kirchhoff's junction rule at junction  $c$  gives

$$I_2 = I_1 + I_3 \quad (3)$$

Solving equations (1), (2), and (3) simultaneously yields

$$\boxed{I_1 = 0.385 \text{ mA}, I_2 = 3.08 \text{ mA}, \text{ and } I_3 = 2.69 \text{ mA}}$$

- (b) Start at point  $c$  and go to point  $f$ , recording changes in potential to obtain



$$V_f - V_c = -\varepsilon_2 - R_2 I_2 = -60.0 \text{ V} - (3.00 \times 10^3 \Omega)(3.08 \times 10^{-3} \text{ A}) = -69.2 \text{ V},$$

$$\text{or } |\Delta V|_{cf} = \boxed{69.2 \text{ V}} \text{ and point } c \text{ is at the higher potential}$$

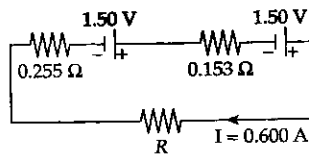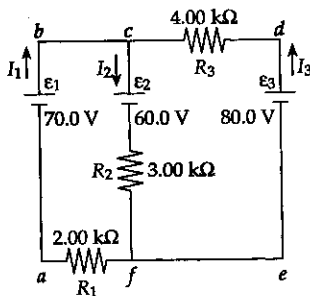- 18.24 (a) Applying Kirchhoff's loop rule to the circuit gives

$$+3.00 \text{ V} - (0.255 \Omega + 0.153 \Omega + R)(0.600 \text{ A}) = 0$$

$$\text{or } R = \frac{3.00 \text{ V}}{0.600 \text{ A}} - (0.255 \Omega + 0.153 \Omega) = \boxed{4.59 \Omega}$$



(b) The total power input to the circuit is

$$\mathcal{P}_{\text{input}} = (\mathcal{E}_1 + \mathcal{E}_2)I = (1.50 \text{ V} + 1.50 \text{ V})(0.600 \text{ A}) = 1.80 \text{ W},$$

$$\mathcal{P}_{\text{loss}} = I^2(r_1 + r_2) = (0.600 \text{ A})^2(0.255 \Omega + 0.153 \Omega) = 0.147 \text{ W}$$

Thus, the fraction of the power input that is dissipated internally is

$$\frac{\mathcal{P}_{\text{loss}}}{\mathcal{P}_{\text{input}}} = \frac{0.147 \text{ W}}{1.80 \text{ W}} = \boxed{0.0816 \text{ or } 8.16\%}$$

18.25 Applying Kirchhoff's junction rule at junction *a* gives

$$I_1 = I_2 + I_3 \quad (1)$$

Using Kirchhoff's loop rule on the upper loop yields

$$+24 \text{ V} - (2.0 + 4.0)I_1 - (3.0)I_3 = 0$$

$$\text{or } 2I_1 + I_3 = 8.0 \text{ A}, \quad (2)$$


and for the lower loop,

$$+12 \text{ V} + (3.0)I_3 - (1.0 + 5.0)I_2 = 0$$

$$\text{or } 2I_2 - I_3 = 4.0 \text{ A} \quad (3)$$

Solving equations (1), (2), and (3) simultaneously gives

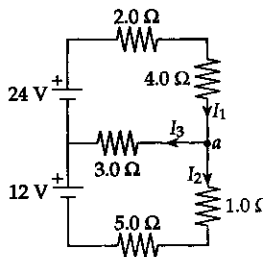
$$\boxed{I_1 = 3.5 \text{ A}, I_2 = 2.5 \text{ A}, \text{ and } I_3 = 1.0 \text{ A}}$$



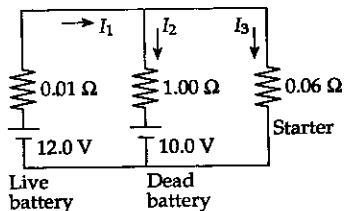- 18.26 Using Kirchhoff's loop rule on the outer perimeter of the circuit gives

$$+12 \text{ V} - (0.01)I_1 - (0.06)I_3 = 0,$$

or  $I_1 + 6I_3 = 1.2 \times 10^3 \text{ A},$  (1)



For the rightmost loop, the loop rule gives

$$+10 \text{ V} + (1.00)I_2 - (0.06)I_3 = 0,$$

or  $I_2 - 0.06I_3 = -10 \text{ A},$  (2)

Applying Kirchhoff's junction rule at either junction gives

$$I_1 = I_2 + I_3. \quad (3)$$

Solving equations (1), (2), and (3) simultaneously yields

$$I_2 = 0.28 \text{ A (in dead battery)} \text{ and } I_3 = 1.7 \times 10^2 \text{ A (in starter)}$$

- 18.27 Assume currents  $I_1$ ,  $I_2$ , and  $I_3$  in the directions shown. Then, using Kirchhoff's junction rule at junction  $a$  gives

$$I_3 = I_1 + I_2 \quad (1)$$

Applying Kirchhoff's loop rule on the upper loop,

$$+20.0 \text{ V} - (30.0)I_1 + (5.00)I_2 - 10.0 \text{ V} = 0,$$


or  $6I_1 - I_2 = 2.00 \text{ A}$  (2)

and for the lower loop,  $+10.0 \text{ V} - (5.00)I_2 - (20.0)I_3 = 0,$

or  $I_2 + 4I_3 = 2.00 \text{ A}$  (3)

Solving equations (1), (2), and (3) simultaneously yields

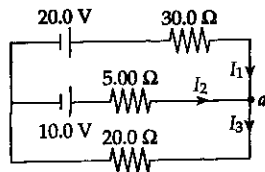
$$I_1 = 0.353 \text{ A}, I_2 = 0.118 \text{ A}, \text{ and } I_3 = 0.471 \text{ A}$$



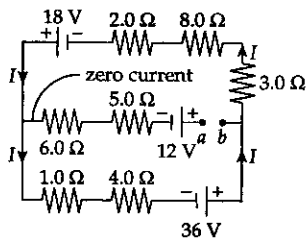- 18.28 (a) Since there is not a continuous path in the center branch, no current exists in that part of the circuit. Then, applying Kirchhoff's loop rule to the outer perimeter gives

$$+18 \text{ V} + 36 \text{ V} - [(1.0 + 4.0 + 3.0 + 8.0 + 2.0) \Omega] I = 0$$

$$\text{or } I = \frac{54 \text{ V}}{18 \Omega} = 3.0 \text{ A}$$



Now, start at point  $b$  and go around the lower loop to point  $a$ , recording changes in potential to obtain


$$V_a - V_b = -36 \text{ V} + (4.0 \Omega + 1.0 \Omega)(3.0 \text{ A}) + (6.0 \Omega + 5.0 \Omega)(0) + 12 \text{ V} = -9.0 \text{ V},$$

$$\text{or } |\Delta V|_{ab} = \boxed{9.0 \text{ V with point } b \text{ at a higher potential than } a}$$

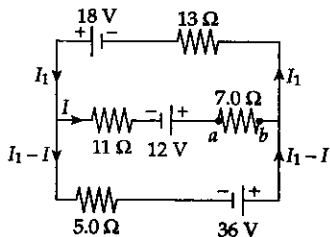- (b) Assume currents as shown in the modified circuit. Applying Kirchhoff's loop rule to the upper loop gives

$$-(11)I + 12 \text{ V} - (7.0)I - (13)I_1 + 18 \text{ V} = 0$$

$$\text{or } 18I + 13I_1 = 30 \text{ A} \quad (1)$$



For the lower loop, the loop rule yields

$$-(5.0)(I_1 - I) + 36 \text{ V} + (7.0)I - 12 \text{ V} + (11)I = 0,$$

$$\text{or } 23I - 5I_1 = -24 \text{ A}. \quad (2)$$

Solving equations (1) and (2) simultaneously gives  $I_1 = 2.9 \text{ A}$ , and

$$I = -0.42 \text{ A}$$

Thus, the current in the  $7.0\text{-}\Omega$  resistor is  $\boxed{0.42 \text{ A flowing from } b \text{ to } a}$ .

- 18.29 Applying Kirchoff's junction rule at junction  $a$  gives

$$I_3 = I_1 + I_2. \quad (1)$$

Using Kirchoff's loop rule on the leftmost loop yields

$$-3.00 \text{ V} - (4.00)I_3 - (5.00)I_1 + 12.0 \text{ V} = 0$$

$$\text{or } 5I_1 + 4I_3 = 9.00 \text{ A}, \quad (2)$$

and for the rightmost loop,

$$-3.00 \text{ V} - (4.00)I_3 - (3.00 + 2.00)I_2 + 18.0 \text{ V} = 0$$

$$\text{or } 5I_2 + 4I_3 = 15.0 \text{ A}, \quad (3)$$


Solving equations (1), (2), and (3) simultaneously gives

$$I_1 = 0.323 \text{ A}, I_2 = 1.523 \text{ A}, \text{ and } I_3 = 1.846 \text{ A}$$

Therefore, the potential differences across the resistors are

$$\Delta V_2 = I_2(2.00 \Omega) = \boxed{3.05 \text{ V}}, \Delta V_3 = I_2(3.00 \Omega) = \boxed{4.57 \text{ V}},$$
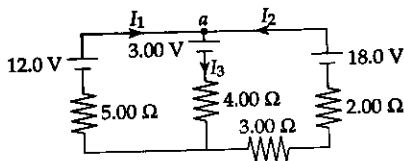
$$\Delta V_4 = I_3(4.00 \Omega) = \boxed{7.38 \text{ V}}, \text{ and } \Delta V_5 = I_1(5.00 \Omega) = \boxed{1.62 \text{ V}}$$



- 18.30 The time constant is  $\tau = RC$ . Considering units, we find

$$RC \rightarrow (\text{Ohms})(\text{Farads}) = \left( \frac{\text{Volts}}{\text{Amperes}} \right) \left( \frac{\text{Coulombs}}{\text{Volts}} \right) = \left( \frac{\text{Coulombs}}{\text{Amperes}} \right)$$



$$18.32 \quad (a) \quad \tau = RC = (100 \, \Omega)(20.0 \times 10^{-6} \, \text{F}) = 2.00 \times 10^{-3} \, \text{s} = \boxed{2.00 \, \text{ms}}$$

$$(b) \quad Q_{\max} = C\mathcal{E} = (20.0 \times 10^{-6} \, \text{F})(9.00 \, \text{V}) = 1.80 \times 10^{-4} \, \text{C} = \boxed{180 \, \mu\text{C}}$$

$$(c) \quad Q = Q_{\max}(1 - e^{-t/\tau}) = Q_{\max}\left(1 - \frac{1}{e}\right) = \boxed{114 \, \mu\text{C}}$$

$$18.33 \quad Q_{\max} = C\mathcal{E} = (5.0 \times 10^{-6} \, \text{F})(30 \, \text{V}) = 1.5 \times 10^{-6} \, \text{C}, \text{ and}$$

$$\tau = RC = (1.0 \times 10^6 \, \Omega)(5.0 \times 10^{-6} \, \text{F}) = 5.0 \, \text{s}$$

Thus, at  $t = 10 \, \text{s} = 2\tau$

$$Q = Q_{\max}(1 - e^{-t/\tau}) = (1.5 \times 10^{-6} \, \text{C})(1 - e^{-2}) = \boxed{1.3 \times 10^{-6} \, \text{C}}$$

18.34 The charge on the capacitor at time  $t$  is  $Q = Q_{\max}(1 - e^{-t/\tau})$ , where

$$Q = C(\Delta V) \text{ and } Q_{\max} = C\mathcal{E}. \text{ Thus, } \Delta V = \mathcal{E}(1 - e^{-t/\tau}) \text{ or } e^{-t/\tau} = 1 - (\Delta V)/\mathcal{E}$$

We are given that,  $\mathcal{E} = 12 \, \text{V}$ , and at  $t = 1.0 \, \text{s}$ ,  $\Delta V = 10 \, \text{V}$

$$\text{Therefore, } e^{-1.0 \, \text{s}/\tau} = 1 - \frac{10}{12} = \frac{12 - 10}{12} = \frac{1}{6.0} \text{ or } e^{+1.0 \, \text{s}/\tau} = 6.0$$

Taking the natural logarithm of each side of the equation gives

$$\frac{1.0 \, \text{s}}{\tau} = \ln(6.0) \quad \text{or} \quad \tau = \frac{1.0 \, \text{s}}{\ln(6.0)} = 0.56 \, \text{s}$$

Since the time constant is  $\tau = RC$ , we have

$$C = \frac{\tau}{R} = \frac{0.56 \, \text{s}}{12 \times 10^3 \, \Omega} = 4.7 \times 10^{-5} \, \text{F} = \boxed{47 \, \mu\text{F}}$$

18.35 From  $Q = Q_{\max}(1 - e^{-t/\tau})$ , we have at  $t = 0.900$  s,

$$\frac{Q}{Q_{\max}} = 1 - e^{-0.900/\tau} = 0.600$$

Thus,  $e^{-0.900/\tau} = 0.400$ , or  $-\frac{0.900 \text{ s}}{\tau} = \ln(0.400)$

giving the time constant as  $\tau = -\frac{0.900 \text{ s}}{\ln(0.400)} = \boxed{0.982 \text{ s}}$

18.36 (a)  $I_{\max} = \frac{\mathcal{E}}{R}$ , so the resistance is

$$R = \frac{\mathcal{E}}{I_{\max}} = \frac{48.0 \text{ V}}{0.500 \times 10^{-3} \text{ A}} = 9.60 \times 10^4 \Omega.$$

The time constant is  $\tau = RC$ , so the capacitance is found to be

$$C = \frac{\tau}{R} = \frac{0.960 \text{ s}}{9.60 \times 10^4 \Omega} = 1.00 \times 10^{-5} \text{ F} = \boxed{10.0 \mu\text{F}}$$

(b)  $Q_{\max} = C\mathcal{E} = (10.0 \mu\text{F})(48.0 \text{ V}) = 480 \mu\text{C}$ , so the charge stored in the capacitor at  $t = 1.92$  s is

$$Q = Q_{\max}(1 - e^{-t/\tau}) = (480 \mu\text{C})\left(1 - e^{-\frac{1.92 \text{ s}}{0.960 \text{ s}}}\right) = (480 \mu\text{C})(1 - e^{-2}) = \boxed{415 \mu\text{C}}$$

18.37 (a) The current drawn by each appliance is

$$\text{Heater: } I = \frac{P}{\Delta V} = \frac{1300 \text{ W}}{120 \text{ V}} = \boxed{10.8 \text{ A}}$$

$$\text{Toaster: } I = \frac{P}{\Delta V} = \frac{1000 \text{ W}}{120 \text{ V}} = \boxed{8.33 \text{ A}}$$

$$\text{Grill: } I = \frac{P}{\Delta V} = \frac{1500 \text{ W}}{120 \text{ V}} = \boxed{12.5 \text{ A}}$$

(b) If the three appliances are operated simultaneously, they will draw a total current of

$$I_{\text{total}} = (10.8 + 8.33 + 12.5) \text{ A} = 31.7 \text{ A}. \text{ Therefore, a 30 ampere circuit breaker is}$$

insufficient to handle the load.

- 18.38 (a) The equivalent resistance of the parallel combination is

$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = \left( \frac{1}{150 \Omega} + \frac{1}{25 \Omega} + \frac{1}{50 \Omega} \right)^{-1} = 15 \Omega,$$

so the total current supplied to the circuit is

$$I_{total} = \frac{\Delta V}{R_{eq}} = \frac{120 \text{ V}}{15 \Omega} = \boxed{8.0 \text{ A}}$$

- (b) Since the appliances are connected in parallel,

the voltage across each one is  $\Delta V = \boxed{120 \text{ V}}$ .

$$(c) I_{lamp} = \frac{\Delta V}{R_{lamp}} = \frac{120 \text{ V}}{150 \Omega} = \boxed{0.80 \text{ A}}$$

$$(d) \phi_{heater} = \frac{(\Delta V)^2}{R_{heater}} = \frac{(120 \text{ V})^2}{25 \Omega} = \boxed{5.8 \times 10^2 \text{ W}}$$

- 18.39 From  $\phi = (\Delta V)^2/R$ , the resistance of the element is

$$R = \frac{(\Delta V)^2}{\phi} = \frac{(240 \text{ V})^2}{3000 \text{ W}} = 19.2 \Omega$$

When the element is connected to a 120-V source, we find that

$$(a) I = \frac{\Delta V}{R} = \frac{120 \text{ V}}{19.2 \Omega} = \boxed{6.25 \text{ A}}, \text{ and}$$

$$(b) \phi = (\Delta V)I = (120 \text{ V})(6.25 \text{ A}) = \boxed{750 \text{ W}}$$

- 18.40 The maximum power available from this line is

$$\phi_{max} = (\Delta V)I_{max} = (120 \text{ V})(15 \text{ A}) = 1800 \text{ W}$$

Thus, the combined power requirements (2400 W) exceeds the available power, and you cannot operate the two appliances together.

- 18.41 (a) The area of each surface of this axon membrane is

$$A = \ell(2\pi r) = (0.10 \text{ m})[2\pi(10 \times 10^{-6} \text{ m})] = 2\pi \times 10^{-6} \text{ m}^2,$$

and the capacitance is

$$C = \kappa \epsilon_0 \frac{A}{d} = 3.0(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2) \left( \frac{2\pi \times 10^{-6} \text{ m}^2}{1.0 \times 10^{-8} \text{ m}} \right) = 1.67 \times 10^{-8} \text{ F}$$

In the resting state, the charge on the outer surface of the membrane is

$$Q_i = C(\Delta V)_i = (1.67 \times 10^{-8} \text{ F})(70 \times 10^{-3} \text{ V}) = 1.17 \times 10^{-9} \text{ C} \rightarrow \boxed{1.2 \times 10^{-9} \text{ C}}$$

The number of potassium ions required to produce this charge is

$$N_{\text{K}^+} = \frac{Q_i}{e} = \frac{1.17 \times 10^{-9} \text{ C}}{1.6 \times 10^{-19} \text{ C}} = \boxed{7.3 \times 10^9 \text{ K}^+ \text{ ions}},$$

and the charge per unit area on this surface is

$$\sigma = \frac{Q_i}{A} = \frac{1.17 \times 10^{-9} \text{ C}}{2\pi \times 10^{-6} \text{ m}^2} \left( \frac{1e}{1.6 \times 10^{-19} \text{ C}} \right) \left( \frac{10^{-20} \text{ m}^2}{1 \text{ \AA}^2} \right) = \frac{1e}{8.6 \times 10^4 \text{ \AA}^2} = \boxed{\frac{1e}{(290 \text{ \AA})^2}}$$

This corresponds to a low charge density of one electronic charge per square of side 290 Å, compared to a normal atomic spacing of one atom per several Å<sup>2</sup>.

- (b) In the resting state, the net charge on the inner surface of the membrane is  $-Q_i = -1.17 \times 10^{-9} \text{ C}$ , and the net positive charge on this surface in the excited state is

$$Q_f = C(\Delta V)_f = (1.67 \times 10^{-8} \text{ F})(+30 \times 10^{-3} \text{ V}) = +5.0 \times 10^{-10} \text{ C}$$

The total positive charge which must pass through the membrane to produce the excited state is therefore

$$\begin{aligned} \Delta Q &= Q_f - Q_i \\ &= +5.0 \times 10^{-10} \text{ C} - (-1.17 \times 10^{-9} \text{ C}) = 1.67 \times 10^{-9} \text{ C} \rightarrow \boxed{1.7 \times 10^{-9} \text{ C}} \end{aligned}$$

corresponding to

$$N_{\text{Na}^+} = \frac{\Delta Q}{e} = \frac{1.67 \times 10^{-9} \text{ C}}{1.6 \times 10^{-19} \text{ C/Na}^+ \text{ ion}} = \boxed{1.0 \times 10^{10} \text{ Na}^+ \text{ ions}}$$

- (c) If the sodium ions enter the axon in a time of  $\Delta t = 2.0 \text{ ms}$ , the average current is

$$I = \frac{\Delta Q}{\Delta t} = \frac{1.67 \times 10^{-9} \text{ C}}{2.0 \times 10^{-3} \text{ s}} = 8.3 \times 10^{-7} \text{ A} = \boxed{0.83 \mu\text{A}}$$

- (d) When the membrane becomes permeable to sodium ions, the initial influx of sodium ions neutralizes the capacitor with no required energy input. The energy input required to charge the now neutral capacitor to the potential difference of the excited state is

$$W = \frac{1}{2} C (\Delta V)^2 = \frac{1}{2} (1.67 \times 10^{-8} \text{ F}) (30 \times 10^{-3} \text{ V})^2 = \boxed{7.5 \times 10^{-12} \text{ J}}$$

- 18.42** The capacitance of the 10 cm length of axon was found to be  $C = 1.67 \times 10^{-8} \text{ F}$  in the solution of Problem 18.41.

- (a) When the membrane becomes permeable to potassium ions, these ions flow out of the axon with no energy input required until the capacitor is neutralized. To maintain this outflow of potassium ions and charge the now neutral capacitor to the resting action potential requires an energy input of

$$W = \frac{1}{2} C (\Delta V)^2 = \frac{1}{2} (1.67 \times 10^{-8} \text{ F}) (70 \times 10^{-3} \text{ V})^2 = \boxed{4.1 \times 10^{-11} \text{ J}}$$

- (b) As found in the solution of Problem 18.41, the charge on the inner surface of the membrane in the resting state is  $-1.17 \times 10^{-9} \text{ C}$  and the charge on this surface in the excited state is  $+5.0 \times 10^{-10} \text{ C}$ . Thus, the positive charge which must flow out of the axon as it goes from the excited state to the resting state is

$$\Delta Q = 5.0 \times 10^{-10} \text{ C} + 1.17 \times 10^{-9} \text{ C} = 1.67 \times 10^{-9} \text{ C},$$

and the average current during the 3.0 ms required to return to the resting state is

$$I = \frac{\Delta Q}{\Delta t} = \frac{1.67 \times 10^{-9} \text{ C}}{3.0 \times 10^{-3} \text{ s}} = 5.6 \times 10^{-7} \text{ A} = \boxed{0.56 \mu\text{A}}$$


- 18.43** From Figure 18.27, the duration of an action potential pulse is 4.5 ms. From the solution problem 18.41, the energy input required to reach the excited state is  $W_1 = 7.5 \times 10^{-12} \text{ J}$ . The energy input required during the return to the resting state is found in problem 18.42 to be  $W_2 = 4.1 \times 10^{-11} \text{ J}$ . Therefore, the average power input required during an action potential pulse is

$$\bar{P} = \frac{W_{\text{total}}}{\Delta t} = \frac{W_1 + W_2}{\Delta t} = \frac{7.5 \times 10^{-12} \text{ J} + 4.1 \times 10^{-11} \text{ J}}{4.5 \times 10^{-3} \text{ s}} = 1.1 \times 10^{-8} \text{ W} = \boxed{11 \text{ nW}}$$

18.44 From  $Q = Q_{\max}(1 - e^{-t/\tau})$ , the ratio  $Q/Q_{\max}$  at  $t = 2\tau$  is found to be

$$\frac{Q}{Q_{\max}} = 1 - e^{-2t/\tau} = 1 - \frac{1}{e^2} = \boxed{0.865}, \text{ or } Q \text{ is } \boxed{86.5\%} \text{ of } Q_{\max} \text{ at } t = 2\tau$$

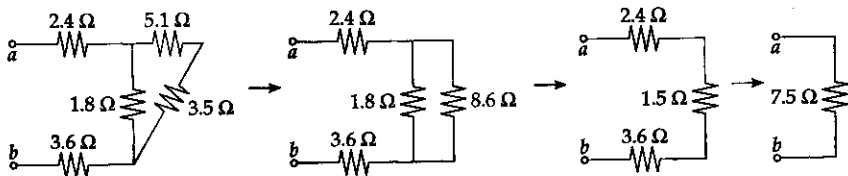18.45 The resistive network between  $a$  and  $b$  reduces, in the stages shown below, to an equivalent resistance of  $R_{\text{eq}} = \boxed{7.5 \Omega}$ .



18.46 (a) The circuit reduces as shown below to an equivalent resistance of  $R_{\text{eq}} = \boxed{14 \Omega}$ .

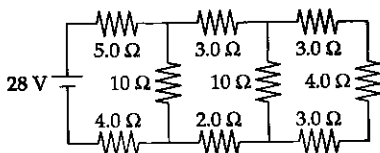


Figure 1

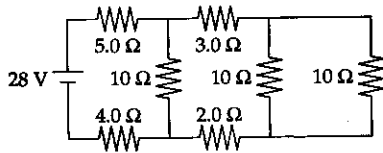


Figure 2

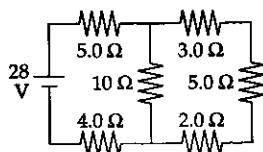


Figure 3

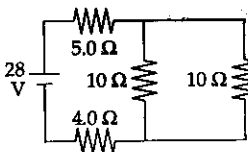


Figure 4

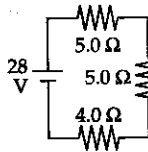


Figure 5

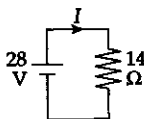


Figure 6

(b) The power dissipated in the circuit is  $\mathcal{P} = \frac{(\Delta V)^2}{R_{\text{eq}}} = \frac{(28 \text{ V})^2}{14 \Omega} = \boxed{56 \text{ W}}$

(c) The current in the original  $5.0\text{-}\Omega$  resistor (in Figure 1) is the total current supplied by the battery. From Figure 6, this is

$$I = \frac{\Delta V}{R_{\text{eq}}} = \frac{28 \text{ V}}{14 \Omega} = \boxed{2.0 \text{ A}}$$

- 18.47 (a) The resistors combine to an equivalent resistance of  $R_{eq} = 15 \Omega$  as shown.

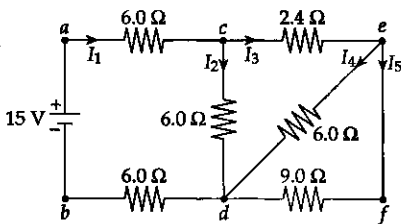


Figure 1

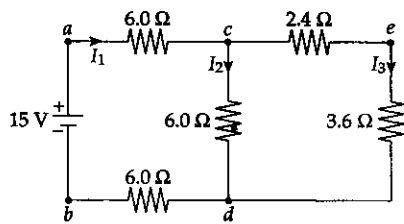


Figure 2

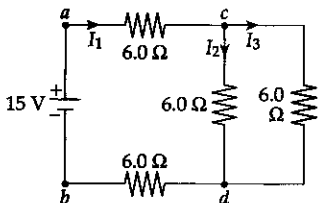


Figure 3

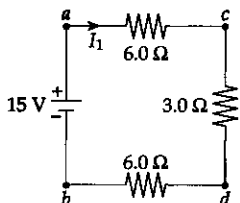


Figure 4

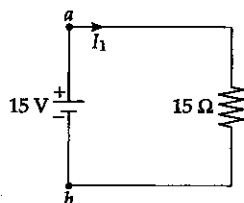


Figure 5

(b) From Figure 5,  $I_1 = \frac{\Delta V_{ab}}{R_{eq}} = \frac{15 \text{ V}}{15 \Omega} = 1.0 \text{ A}$ .

Then, from Figure 4,

$$\Delta V_{ac} = \Delta V_{ab} = I_1 (6.0 \Omega) = 6.0 \text{ V} \quad \text{and} \quad \Delta V_{cd} = I_1 (3.0 \Omega) = 3.0 \text{ V}$$

From Figure 3,  $I_2 = I_3 = \frac{\Delta V_{cd}}{6.0 \Omega} = \frac{3.0 \text{ V}}{6.0 \Omega} = 0.50 \text{ A}$

From Figure 2,  $\Delta V_{cd} = I_3 (3.6 \Omega) = 1.8 \text{ V}$

Then, from Figure 1,  $I_4 = \frac{\Delta V_{cd}}{6.0 \Omega} = \frac{1.8 \text{ V}}{6.0 \Omega} = 0.30 \text{ A}$

and  $I_5 = \frac{\Delta V_{fd}}{9.0 \Omega} = \frac{\Delta V_{cd}}{9.0 \Omega} = \frac{1.8 \text{ V}}{9.0 \Omega} = 0.20 \text{ A}$

- (c) From Figure 2,  $\Delta V_{ce} = I_3 (2.4 \Omega) = 1.2 \text{ V}$ . All the other needed potential differences were calculated above in part (b). The results were

$$\Delta V_{ac} = \Delta V_{ab} = 6.0 \text{ V}; \quad \Delta V_{cd} = 3.0 \text{ V}; \quad \text{and} \quad \Delta V_{fd} = \Delta V_{cd} = 1.8 \text{ V}$$

- (d) The power dissipated in each resistor is found from  $\phi = (\Delta V)^2/R$  with the following results:

$$\phi_{ac} = \frac{(\Delta V)_{ac}^2}{R_{ac}} = \frac{(6.0 \text{ V})^2}{6.0 \Omega} = \boxed{6.0 \text{ W}}; \quad \phi_{ce} = \frac{(\Delta V)_{ce}^2}{R_{ce}} = \frac{(1.2 \text{ V})^2}{2.4 \Omega} = \boxed{0.60 \text{ W}};$$

$$\phi_{cd} = \frac{(\Delta V)_{cd}^2}{R_{cd}} = \frac{(1.8 \text{ V})^2}{6.0 \Omega} = \boxed{0.54 \text{ W}}; \quad \phi_{fd} = \frac{(\Delta V)_{fd}^2}{R_{fd}} = \frac{(1.8 \text{ V})^2}{9.0 \Omega} = \boxed{0.36 \text{ W}};$$

$$\phi_{cd} = \frac{(\Delta V)_{cd}^2}{R_{cd}} = \frac{(3.0 \text{ V})^2}{6.0 \Omega} = \boxed{1.5 \text{ W}}; \quad \phi_{db} = \frac{(\Delta V)_{db}^2}{R_{db}} = \frac{(6.0 \text{ V})^2}{6.0 \Omega} = \boxed{6.0 \text{ W}}$$

- 18.48 (a) From  $\phi = (\Delta V)^2/R$ , the resistance of each of the three bulbs is given by

$$R = \frac{(\Delta V)^2}{\phi} = \frac{(120 \text{ V})^2}{60.0 \text{ W}} = 240 \Omega$$

As connected, the parallel combination of  $R_2$  and  $R_3$  is in series with  $R_1$ . Thus, the equivalent resistance of the circuit is

$$R_{eq} = R_1 + \left( \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = 240 \Omega + \left( \frac{1}{240 \Omega} + \frac{1}{240 \Omega} \right)^{-1} = 360 \Omega$$

The total power delivered to the circuit is


$$\phi = \frac{(\Delta V)^2}{R_{eq}} = \frac{(120 \text{ V})^2}{360 \Omega} = \boxed{40.0 \text{ W}}$$

- (b) The current supplied by the source is  $I = \frac{\Delta V}{R_{eq}} = \frac{120 \text{ V}}{360 \Omega} = \frac{1}{3} \text{ A}$ . Thus, the potential difference across  $R_1$  is

$$(\Delta V)_1 = IR_1 = \left( \frac{1}{3} \text{ A} \right) (240 \Omega) = \boxed{80.0 \text{ V}}$$

The potential difference across the parallel combination of  $R_2$  and  $R_3$  is then
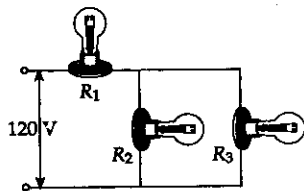
$$(\Delta V)_2 = (\Delta V)_3 = (\Delta V)_{source} - (\Delta V)_1 = 120 \text{ V} - 80.0 \text{ V} = \boxed{40.0 \text{ V}}$$





- 18.49 (a) From  $\mathcal{E} = I(r + R_{\text{load}})$ , the current supplied when the headlights are the entire load is

$$I = \frac{\mathcal{E}}{r + R_{\text{load}}} = \frac{12.6 \text{ V}}{(0.080 + 5.00) \Omega} = 2.48 \text{ A}.$$

The potential difference across the headlights is then

$$\Delta V = IR_{\text{load}} = (2.48 \text{ A})(5.00 \Omega) = \boxed{12.4 \text{ V}}$$

- (b) The starter motor connects in parallel with the headlights. If  $I_H$  is the current supplied to the headlights, the total current delivered by the battery is  $I = I_H + 35.0 \text{ A}$ .

The terminal potential difference of the battery is  $\Delta V = \mathcal{E} - Ir$ , so the total current is  $I = (\mathcal{E} - \Delta V)/r$  while the current to the headlights is  $I_H = \Delta V/5.00 \Omega$ . Thus,  $I = I_H + 35.0 \text{ A}$  becomes

$$\frac{\mathcal{E} - \Delta V}{r} = \frac{\Delta V}{5.00 \Omega} + 35.0 \text{ A},$$

which yields

$$\Delta V = \frac{\mathcal{E} - (35.0 \text{ A})r}{1 + r/(5.00 \Omega)} = \frac{12.6 \text{ V} - (35.0 \text{ A})(0.080 \Omega)}{1 + (0.080 \Omega)/(5.00 \Omega)} = \boxed{9.65 \text{ V}}$$

- 18.50 (a) After steady-state conditions have been reached, there is no current in the branch containing the capacitor.


Thus, for  $R_3$ :

$$\boxed{I_{R_3} = 0 \text{ (steady-state)}}$$

For the other two resistors, the steady-state current is simply determined by the 9.00-V emf across the 12.0-k $\Omega$  and 15.0-k $\Omega$  resistors in series:

For  $R_1$  and  $R_2$ :
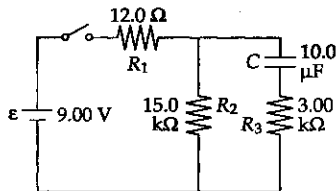
$$I_{(R_1+R_2)} = \frac{\mathcal{E}}{R_1 + R_2} = \frac{9.00 \text{ V}}{(12.0 \text{ k}\Omega + 15.0 \text{ k}\Omega)} = \boxed{333 \mu\text{A} \text{ (steady-state)}}$$



- (b) When the steady-state has been reached, the potential difference across C is the same as the potential difference across  $R_2$  because there is no change in potential across  $R_3$ . Therefore, the charge on the capacitor is

$$Q = C(\Delta V)_{R_2}$$

$$= C(IR_2) = (10.0 \mu\text{F})(333 \times 10^{-6} \text{ A})(15.0 \times 10^3 \Omega) = \boxed{50.0 \mu\text{C}}$$

- 18.51 Applying Kirchhoff's junction rule at junction  $a$  gives

$$I_2 = I_1 + I_3 \quad (1)$$

Applying Kirchhoff's loop rule on the leftmost loop yields

$$+9.0 \text{ V} - (5.0)I_1 - 4.0 \text{ V} - (10)I_2 = 0,$$

or  $I_1 + 2I_2 = 1.0 \text{ A} \quad (2)$


For the rightmost loop,

$$+(10)I_2 + 4.0 \text{ V} + (10)I_3 - 14 \text{ V} = 0,$$


or  $I_2 + I_3 = 1.0 \text{ A} \quad (3)$

Solving equations (1), (2) and (3) simultaneously gives

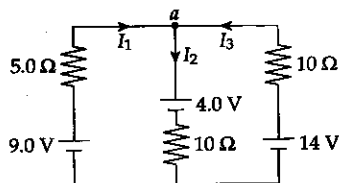
$$\boxed{I_1 = 0, I_2 = I_3 = 0.50 \text{ A}}$$



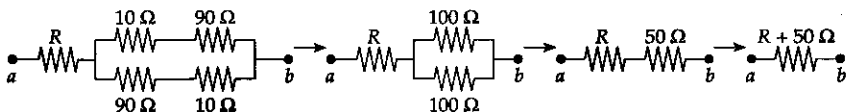18.52 With the switch open, the circuit may be reduced as follows:



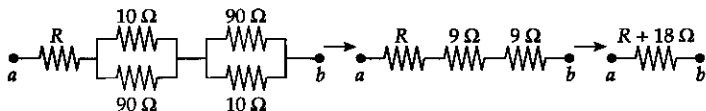With the switch closed, the circuit reduces as shown below:



Since the equivalent resistance with the switch closed is one-half that when the switch is open, we have

$$R + 18 \Omega = \frac{1}{2}(R + 50 \Omega), \text{ which yields } R = \boxed{14 \Omega}$$

18.53 When a generator with emf  $\mathcal{E}$  and internal resistance  $r$  supplies current  $I$ , its terminal voltage is  $\Delta V = \mathcal{E} - Ir$ .

$$\text{If } \Delta V = 110 \text{ V when } I = 10.0 \text{ A, then} \quad 110 \text{ V} = \mathcal{E} - (10.0 \text{ A})r \quad (1)$$

$$\text{Given that } \Delta V = 106 \text{ V when } I = 30.0 \text{ A, yields} \quad 106 \text{ V} = \mathcal{E} - (30.0 \text{ A})r \quad (2)$$

Solving equations (1) and (2) simultaneously gives

$$\boxed{\mathcal{E} = 112 \text{ V and } r = 0.200 \Omega}$$

18.54 At time  $t$ , the charge on the capacitor will be  $Q = Q_{\max}(1 - e^{-t/\tau})$  where

$$\tau = RC = (2.0 \times 10^6 \Omega)(3.0 \times 10^{-6} \text{ F}) = 6.0 \text{ s}$$

When  $Q = 0.90Q_{\max}$ , this gives  $0.90 = 1 - e^{-t/\tau}$ ,

$$\text{or } e^{-t/\tau} = 0.10 \quad \text{Thus, } -\frac{t}{\tau} = \ln(0.10),$$

$$\text{giving } t = -(6.0 \text{ s})\ln(0.10) = \boxed{14 \text{ s}}$$

- 18.55 (a) For the first measurement, the equivalent circuit is as shown in Figure 1. From this,

$$R_{ab} = R_1 = R_y + R_y = 2R_y,$$

$$\text{so } R_y = \frac{1}{2}R_1 \quad (1)$$

For the second measurement, the equivalent circuit is shown in Figure 2. This gives

$$R_{ac} = R_2 = \frac{1}{2}R_y + R_x \quad (2)$$

Substitute (1) into (2) to obtain

$$R_2 = \frac{1}{2}\left(\frac{1}{2}R_1\right) + R_x, \text{ or } R_x = R_2 - \frac{1}{4}R_1$$

- (b) If  $R_1 = 13 \Omega$  and  $R_2 = 6.0 \Omega$ , then  $R_x = 2.8 \Omega$

Since this exceeds the limit of  $2.0 \Omega$ , the antenna is **inadequately grounded**.

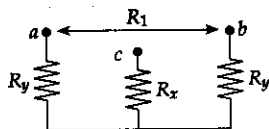


Figure 1

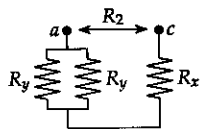


Figure 2

- 18.56 Assume a set of currents as shown in the circuit diagram at the right. Applying Kirchhoff's loop rule to the leftmost loop gives

$$+75 - (5.0)I - (30)(I - I_1) = 0,$$

$$\text{or } 7I - 6I_1 = 15 \quad (1)$$


For the rightmost loop, the loop rule gives

$$-(40 + R)I_1 + (30)(I - I_1) = 0, \text{ or } I = \left(\frac{7}{3} + \frac{R}{30}\right)I_1 \quad (2)$$

Substituting equation (2) into (1) and simplifying gives

$$310I_1 + 7(I_1R) = 450 \quad (3)$$
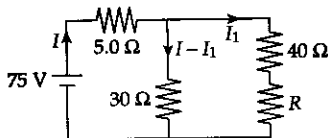
$$\text{Also, it is known that } \rho_R = I_1^2R = 20 \text{ W, so } I_1R = \frac{20 \text{ W}}{I_1} \quad (4)$$



Substitution of equation (4) into (3) yields

$$310I_1 + \frac{140}{I_1} = 450 \text{ or } 310I_1^2 - 450I_1 + 140 = 0$$

Solving this quadratic equation gives two possible values for the current  $I_1$ . These are  $I_1 = 1.0 \text{ A}$  and  $I_1 = 0.452 \text{ A}$ . Then, from  $R = \frac{20 \text{ W}}{I_1^2}$ , we find two possible values for the resistance  $R$ . These are

$$\boxed{R = 20 \Omega \text{ or } R = 98 \Omega}$$

18.57 When connected in series, the equivalent resistance is  $R_{eq} = R_1 + R_2 + \dots + R_n = nR$ .

Thus, the current is  $I_s = (\Delta V)/R_{eq} = (\Delta V)/nR$ , and the power consumed by the series configuration is

$$\phi_s = I_s^2 R_{eq} = \frac{(\Delta V)^2}{(nR)^2} (nR) = \frac{(\Delta V)^2}{nR}$$

For the parallel connection, the power consumed by each individual resistor is

$\phi_1 = \frac{(\Delta V)^2}{R}$ , and the total power consumption is

$$\phi_p = n\phi_1 = \frac{n(\Delta V)^2}{R}$$

Therefore,  $\frac{\phi_s}{\phi_p} = \frac{(\Delta V)^2}{nR} \cdot \frac{R}{n(\Delta V)^2} = \frac{1}{n^2}$  or  $\boxed{\phi_s = \frac{1}{n^2} \phi_p}$

- 18.58 Consider a battery of emf  $\mathcal{E}$  connected between points  $a$  and  $b$  as shown. Applying Kirchoff's loop rule to loop  $acbea$  gives

$$-(1.0)I_1 - (1.0)(I_1 - I_3) + \mathcal{E} = 0,$$

or  $2I_1 - I_3 = \mathcal{E}$

Applying the loop rule to loop  $adbea$  gives

$$-(3.0)I_2 - (5.0)(I_2 + I_3) + \mathcal{E} = 0$$

or  $8I_2 + 5I_3 = \mathcal{E}$

For loop  $adca$ , the loop rule yields

$$-(3.0)I_2 + (1.0)I_3 + (1.0)I_1 = 0 \text{ or } I_1 + I_3 = 3I_2 \quad (3)$$

Solving equations (1), (2) and (3) simultaneously gives

$$I_1 = \frac{13}{27}\mathcal{E}, \quad I_2 = \frac{4}{27}\mathcal{E}, \quad \text{and } I_3 = -\frac{1}{27}\mathcal{E}$$

Then, applying Kirchoff's junction rule at junction  $a$  gives



$$I = I_1 + I_2 = \frac{13}{27}\mathcal{E} + \frac{4}{27}\mathcal{E} = \frac{17}{27}\mathcal{E}. \text{ Therefore, } R_{ab} = \frac{\mathcal{E}}{I} = \frac{\mathcal{E}}{(17\mathcal{E}/27)} = \boxed{\frac{27}{17} \Omega}$$

- 18.59 (a) and (b) - With  $R$  the value of the load resistor, the current in a series circuit composed of a 12.0 V battery, an internal resistance of 10.0  $\Omega$ , and a load resistor is

$$I = \frac{12.0 \text{ V}}{R + 10.0 \Omega},$$


and the power delivered to the load resistor is
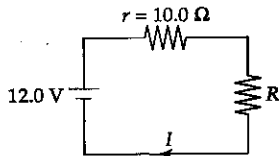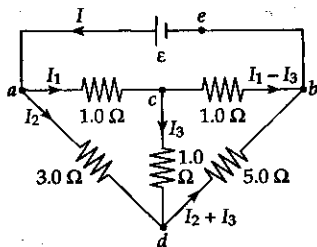
$$\mathcal{P}_L = I^2 R = \boxed{\frac{(144 \text{ V}^2) R}{(R + 10.0 \Omega)^2}}$$



Some typical data values for the graph are

$R (\Omega)$	$\phi_L (W)$
1.00	1.19
5.00	3.20
10.0	3.60
15.0	3.46
20.0	3.20
25.0	2.94
30.0	2.70

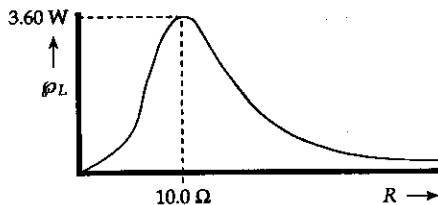

The curve peaks at  $\phi_L = 3.60 \text{ W}$  at a load resistance of  $R = 10.0 \Omega$ .

18.60 The total resistance in the circuit is

$$R = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \left( \frac{1}{2.0 \text{ k}\Omega} + \frac{1}{3.0 \text{ k}\Omega} \right)^{-1} = 1.2 \text{ k}\Omega,$$

and the total capacitance is  $C = C_1 + C_2 = 2.0 \mu\text{F} + 3.0 \mu\text{F} = 5.0 \mu\text{F}$ .

Thus,  $Q_{\max} = C\mathcal{E} = (5.0 \mu\text{F})(120 \text{ V}) = 600 \mu\text{C}$

and  $\tau = RC = (1.2 \times 10^3 \Omega)(5.0 \times 10^{-6} \text{ F}) = 6.0 \times 10^{-3} \text{ s} = \frac{6.0 \text{ s}}{1000}$

The total stored charge at any time  $t$  is then

$$Q = Q_1 + Q_2 = Q_{\max} (1 - e^{-t/\tau}) \text{ or } Q_1 + Q_2 = (600 \mu\text{C}) (1 - e^{-1000t/6.0 \text{ s}}) \quad (1)$$

Since the capacitors are in parallel with each other, the same potential difference exists across both at any time.

Therefore,  $(\Delta V)_C = \frac{Q_1}{C_1} = \frac{Q_2}{C_2}$ , or  $Q_2 = \left( \frac{C_2}{C_1} \right) Q_1 = 1.5 Q_1$  (2)

Solving equations (1) and (2) simultaneously gives

$$Q_1 = \left[ (240 \mu\text{C}) (1 - e^{-1000t/6.0 \text{ s}}) \right],$$

and  $Q_2 = \left[ (360 \mu\text{C}) (1 - e^{-1000t/6.0 \text{ s}}) \right]$