

PHYSICS 1B – Fall 2007



Electricity & Magnetism




Professor Brian Keating
SERF Building, Room 333

Why is the **series law** easy to understand?

- Recall that the resistance of a resistor is

$$R = \rho \frac{L}{A}$$

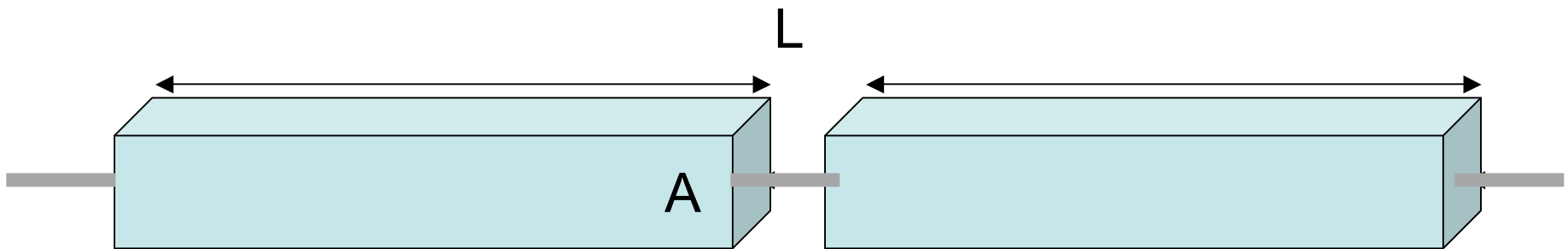


$$R \sim L$$

$$R_{\text{tot}} \sim L_1 + L_2$$

Resistors in Series I same, ΔV different

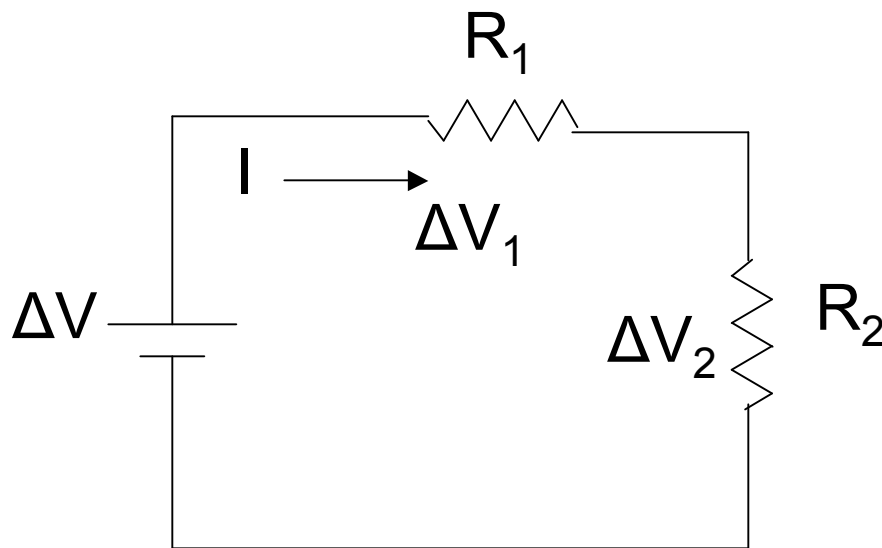What is the equivalent resistance R_{eq} ?



$$\Delta V = \Delta V_1 + \Delta V_2$$

$$\Delta V = IR_{eq} = IR_1 + IR_2$$

$$R_{eq} = R_1 + R_2$$

For N resistors in series

$$R_{eq} = R_1 + R_2 + \dots + R_N$$

R_{eq} is larger
than any R

Why is the **parallel law** easy to understand?

- Recall that the resistance of a resistor is

$$R = \rho \frac{L}{A}$$




$R \sim 1/\text{Area}$

$$A_{\text{tot}} = A_1 + A_2$$

$$A_{\text{tot}} = 1/R_1 + 1/R_2$$

$$R_{\text{tot}} \sim 1/A_{\text{tot}} \sim 1/(1/R_1 + 1/R_2)$$

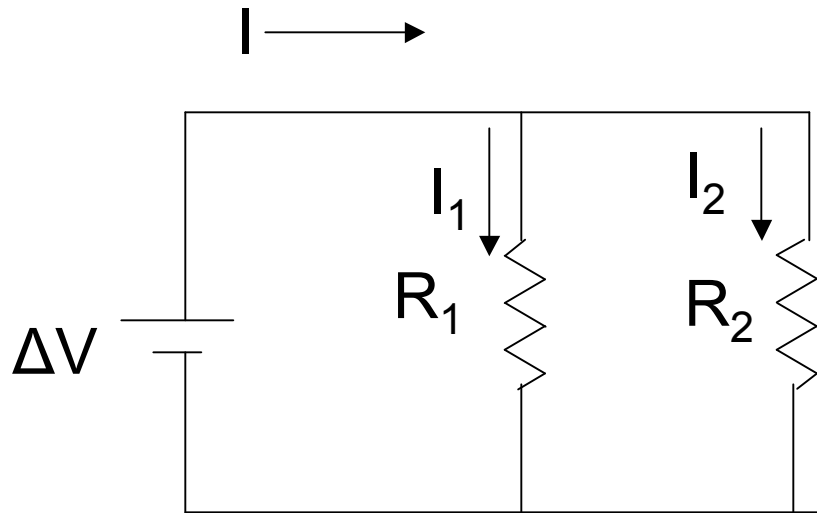Resistors in parallel, ΔV same, I different



$$I = I_1 + I_2$$

$$\frac{\Delta V}{R_{eq}} = I = \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

For N resistors in parallel

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$



R_{eq} is smaller
than any R

Comparisons: Resistors & Capacitors

- Resistors in series are like capacitors in parallel.
- Resistors in parallel are like capacitors in series.
- This is because $R \sim L$ and $C \sim 1/L$
- And because $R \sim 1/A$ and $C \sim A$

Why do we care?

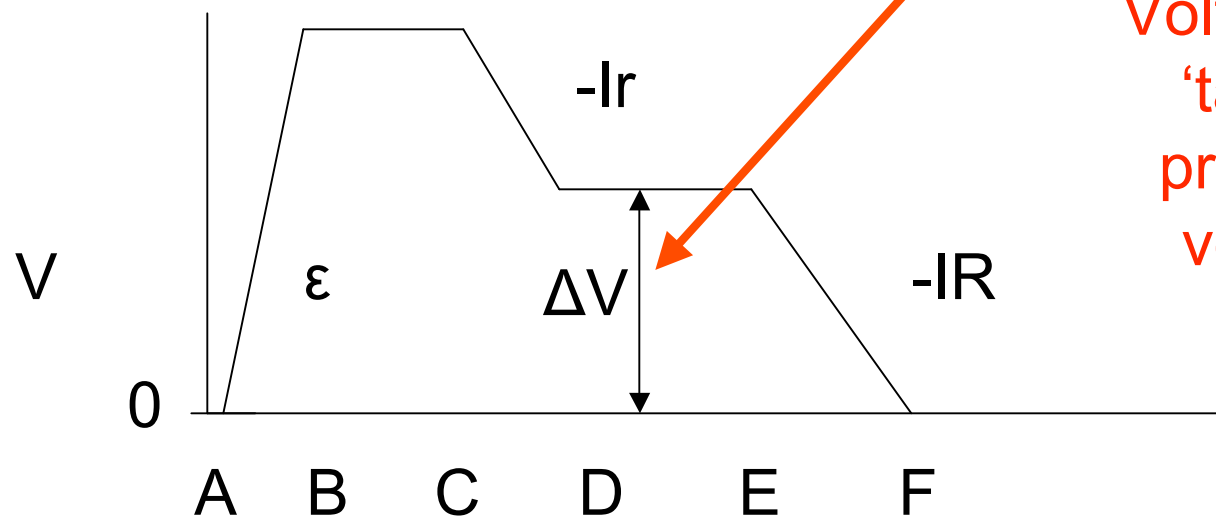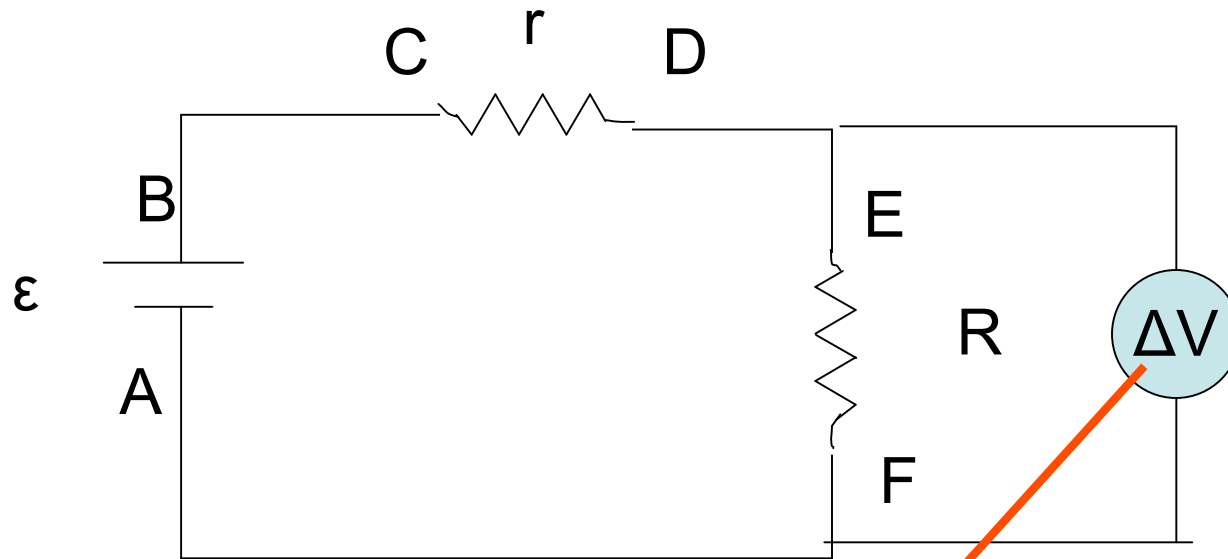Consider Simple Circuit: Two resistors in Series




Voltage can be 'tailored' to produce any voltage we desire!

Ch 18 Kirchoff's 2 Rules

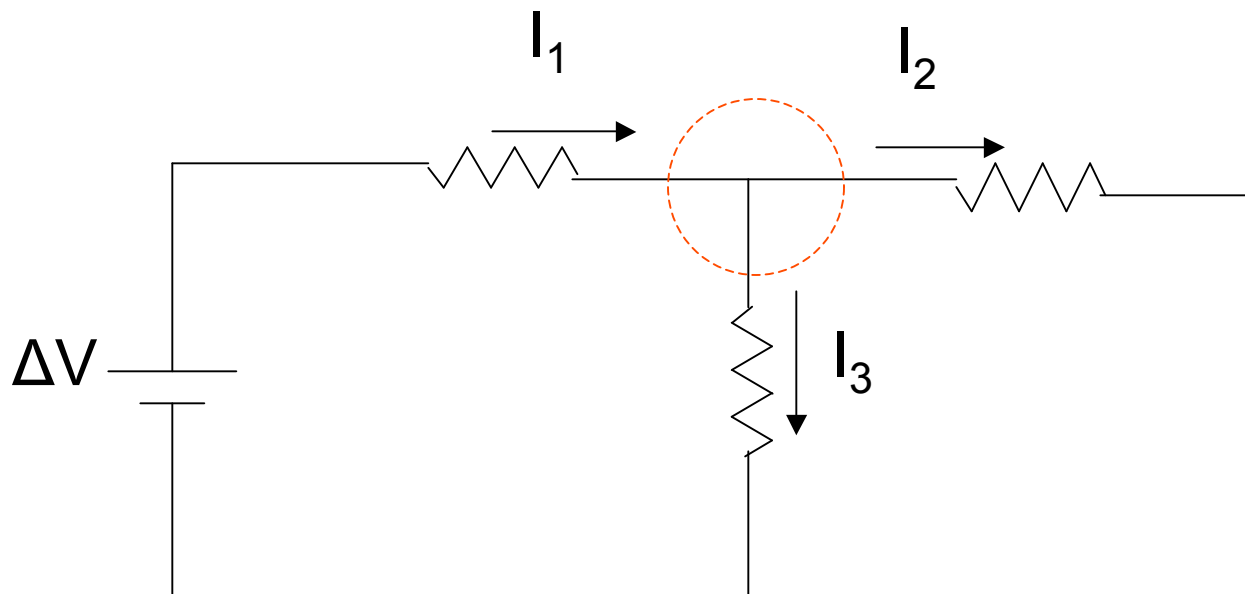1. Junction rule
2. Loop rule

Rule #1. “*Junction rule*”

The current flowing into a junction is equal to the current flowing out.




$$I_1 = I_2 + I_3$$

This comes from ‘conservation of charge’
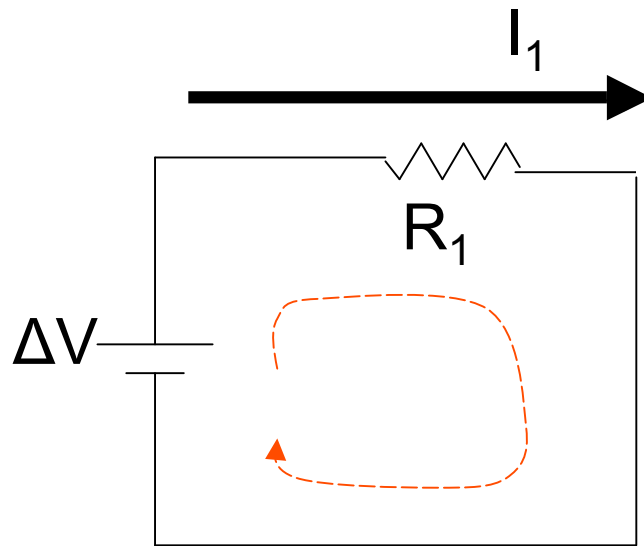
#2. Loop rule


“The sum of voltage differences in going around a closed current loop is equal to zero”



$$\sum_{loop} \Delta V_i = 0$$
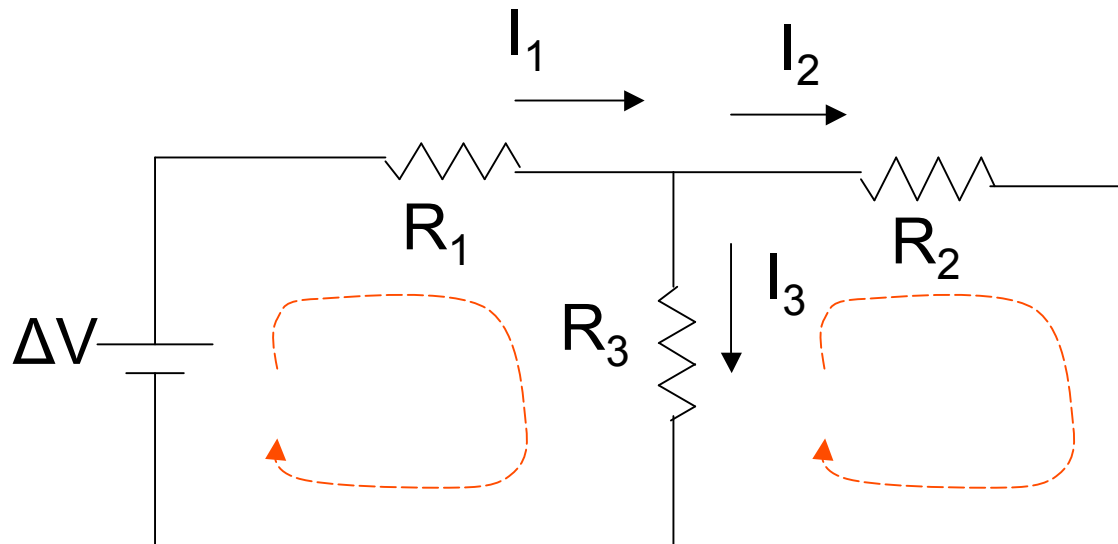
#2. Loop rule

The sum of voltage differences in going around a closed current loop is equal to zero



$$\sum_{loop} \Delta V_i = 0$$

Voltage changes in traversing the loop


Choose a current direction

- IR , current in traversal direction

+ IR current in opposite direction

+ ΔV voltage increases along traversal direction

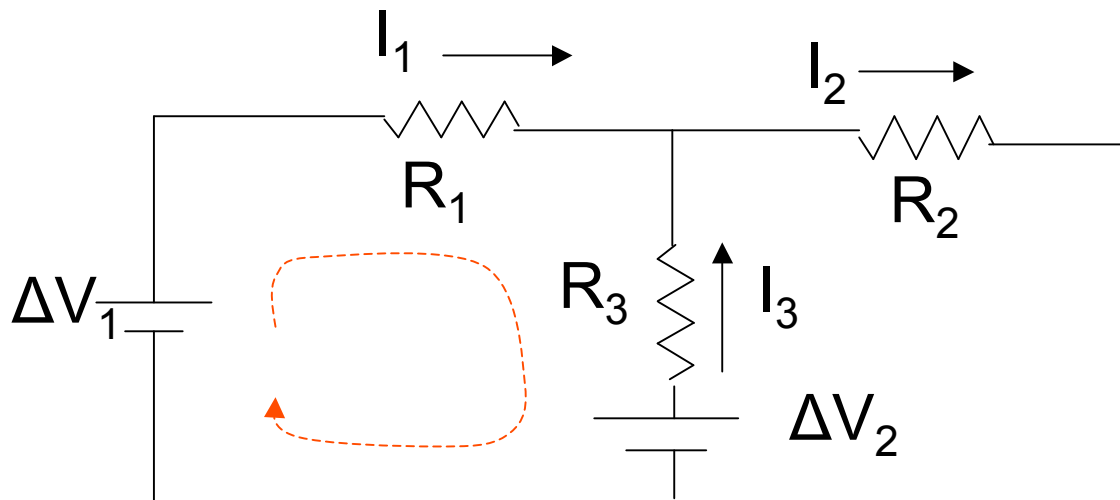
- ΔV voltage decreases along traversal direction



$$\Delta V_1 - I_1 R_1 + I_3 R_3 - \Delta V_2 = 0$$

If I is negative when you solve the equations, the current flows in the opposite direction than you chose.

Not all loop equations are independent

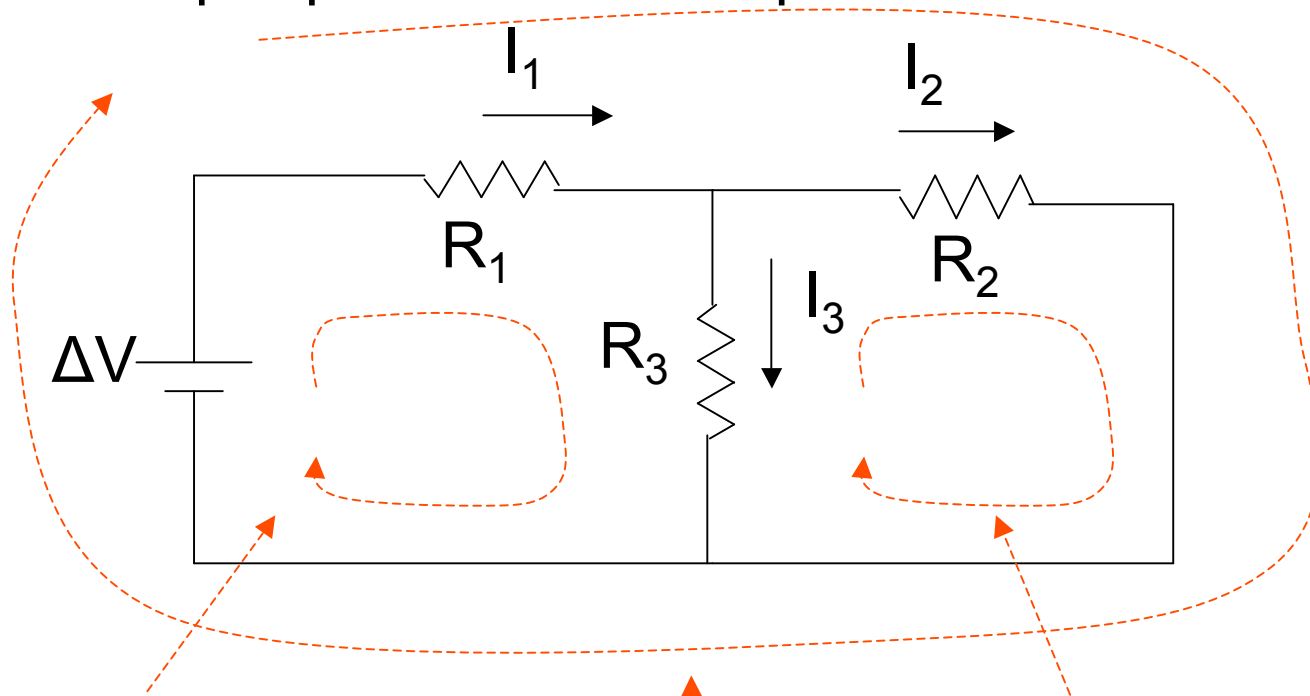

$$\Delta V - I_1 R_1 - I_3 R_3 = 0$$

$$I_3 R_3 - I_2 R_2 = 0$$

$$\Delta V - I_1 R_1 - I_2 R_2 = 0$$

only 2 of these equations are independent

Using Kirchoff's rules


- (1) Write the equations for the junction rule.
- (2) Write the equations for the loop rule. Choose a direction for currents. If the current is negative then it flows in the opposite direction. Use as many equations as necessary to solve for all unknown quantities. (for n unknowns need n equations).
- (3) Solve the set of equations for n unknown quantities.

Find I_1, I_2, I_3

No. equations needed = 3

no. Junction = 1

No. loop = 2

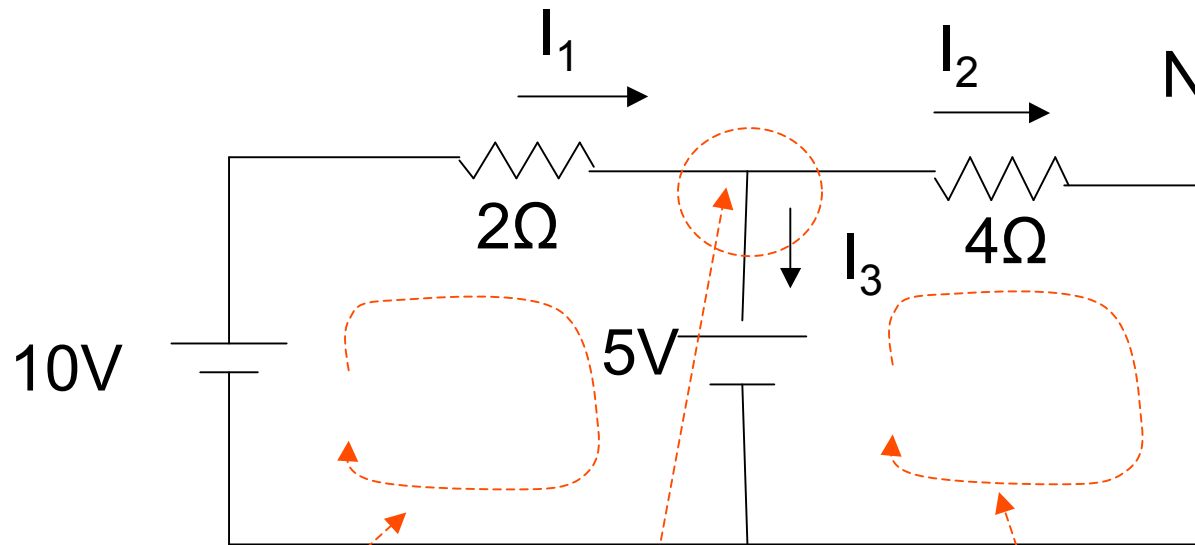

$$V=IR$$

$$10 - 2I_1 - 5 = 0$$

$$I_1 = \frac{10 - 5}{2} = 2.5A$$

$$I_1 = I_2 + I_3$$

$$I_3 = I_1 - I_2$$

$$I_3 = 2.5 - 1.25 = 1.25A$$

$$5 - 4I_2 = 0$$

$$I_2 = \frac{5}{4} = 1.25A$$


Chapter 18.5 RC circuit

Time dependent currents and voltages.

Applications. clocks, timing circuits,
computers.


Time to charge and discharge of a capacitor

RC circuit

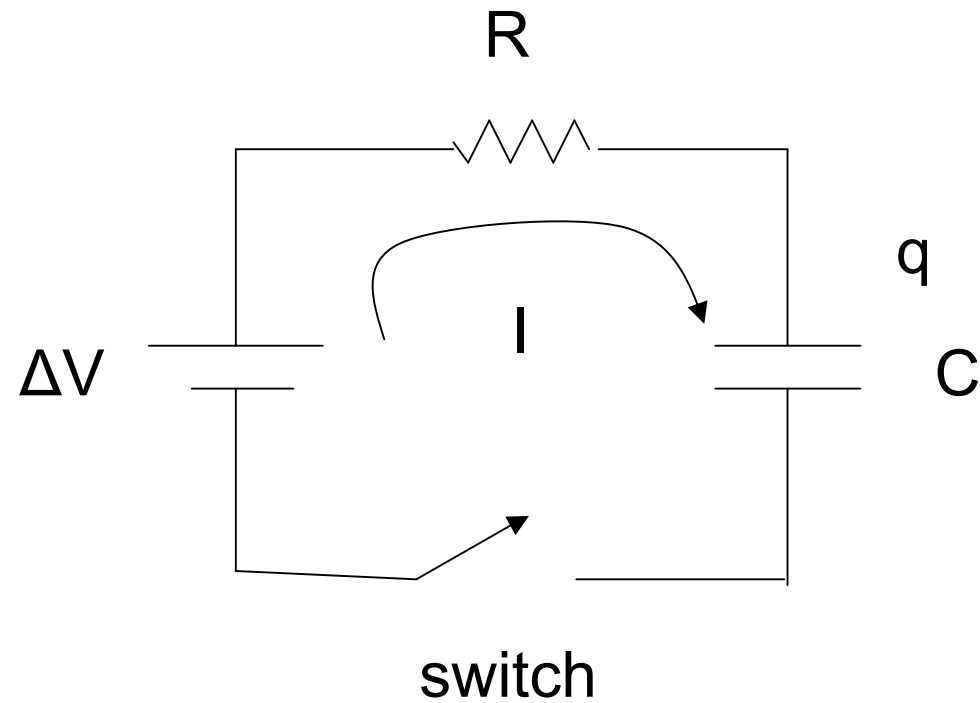

When the switch is closed how does the current and voltage change with time?

RC circuit

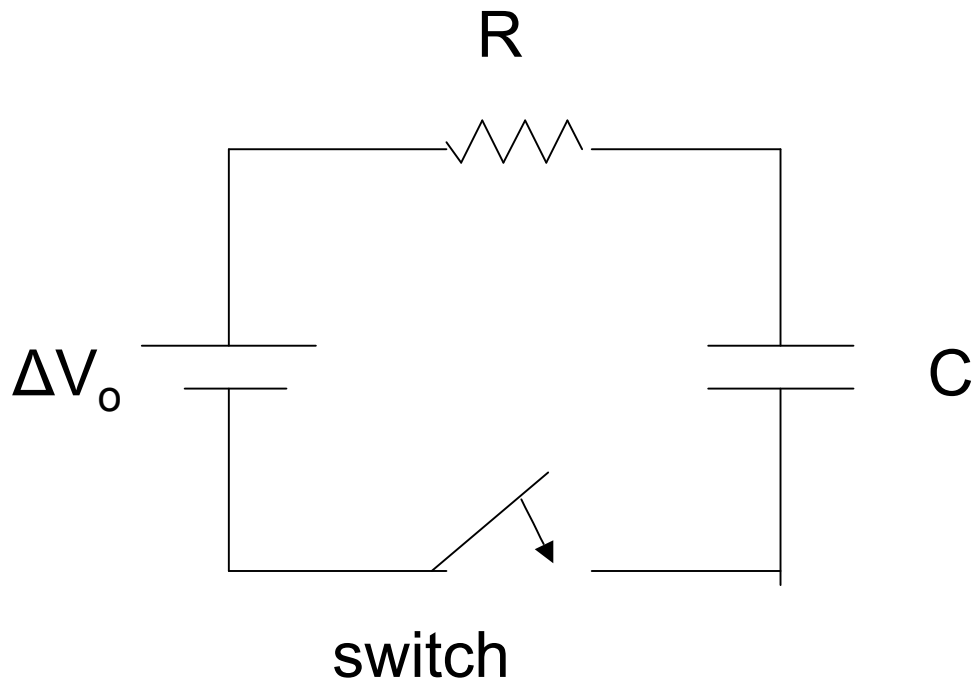


Switch off

Capacitor uncharged

$$\Delta V_c = 0$$

Charging

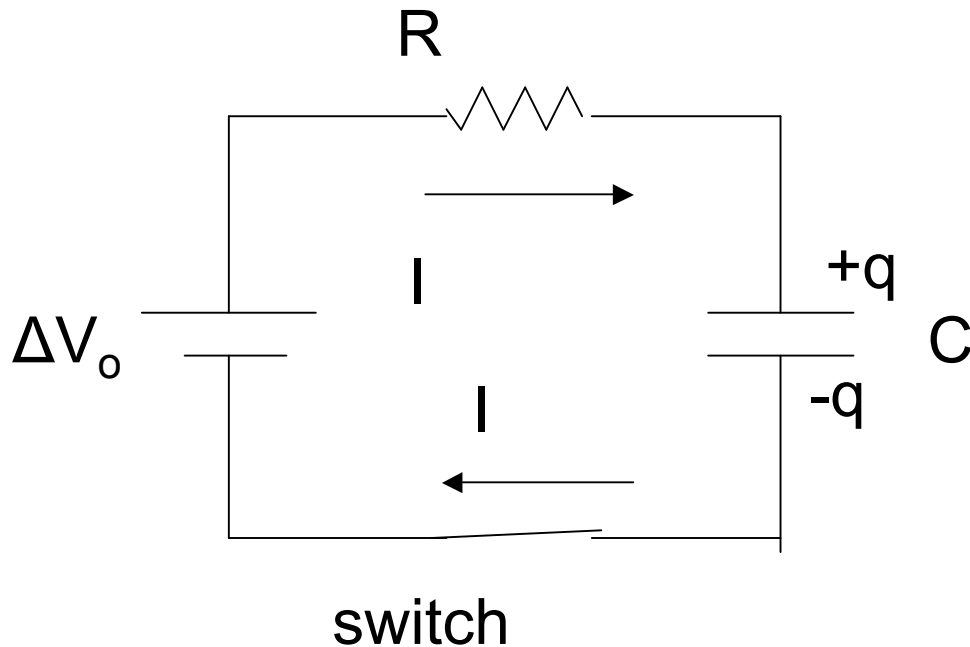

Switch on

$$\Delta V_c = \frac{q}{C}$$



$$\Delta V_0 - IR - \Delta V_c = 0$$

When the switch is initially closed the voltage on the capacitor is zero.

Charge is transferred to the capacitor at a rate $I = dq/dt$.

As the capacitor is charging the charge and voltage on the capacitor increases with time and the current decreases.

Charging Capacitor

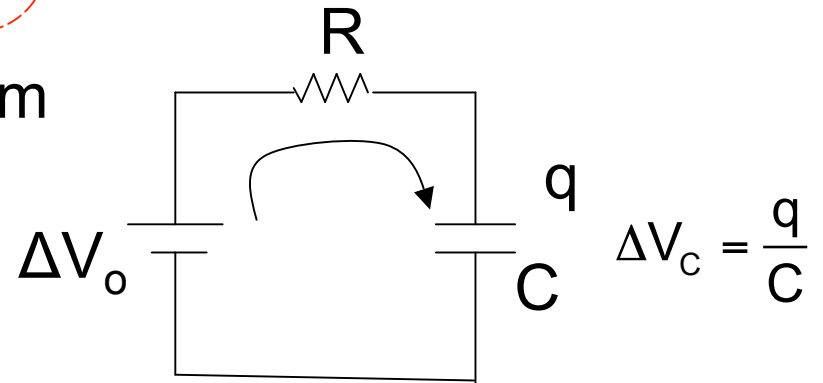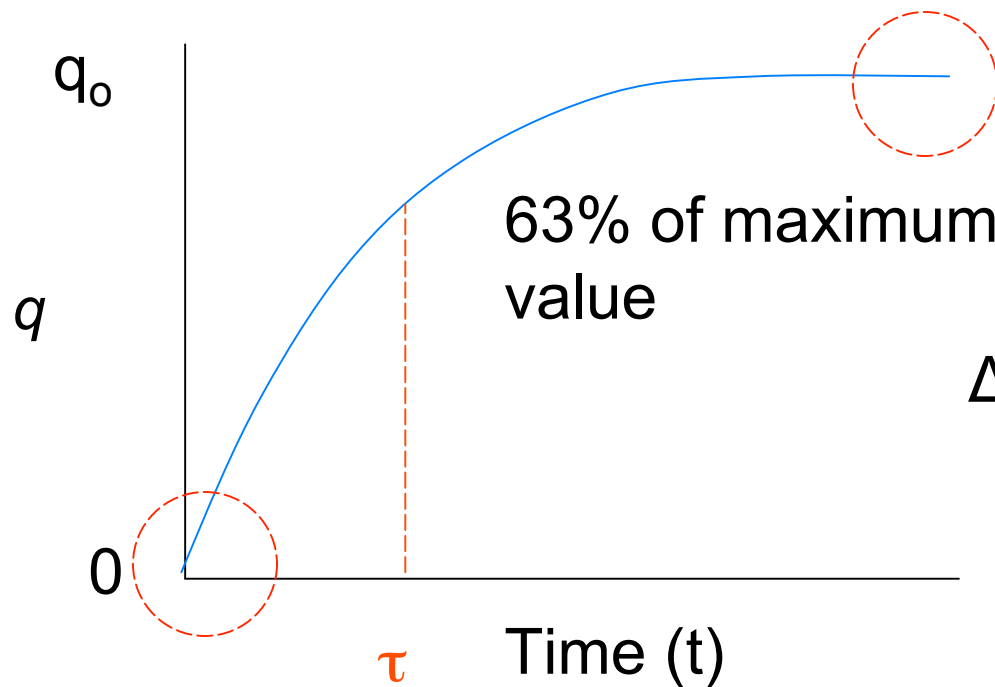

$$\Delta V_C = \frac{q}{C}$$

$$\Delta V_0 = IR + \frac{q}{C}$$

short times

intermediate times

long times

$$q = \sim 0$$

$$q = q_0(1 - e^{-\left(\frac{t}{\tau}\right)})$$

$$q = q_0$$

$$\Delta V_C = \approx 0$$

$$\Delta V_C = V_0(1 - e^{-\left(\frac{t}{\tau}\right)})$$

$$\Delta V_C = \Delta V_0$$

$$I = \approx \frac{\Delta V_0}{R}$$

$$I = \frac{\Delta V_0}{R} e^{-\left(\frac{t}{\tau}\right)}$$

$$\tau = RC$$

$$I = 0$$

Time Constant

$$\tau = RC$$

Dimensional analysis


$$RC = \frac{V}{I} \frac{q}{V} = \frac{q}{I} = \frac{q}{q/t} = t$$

RC has units of time


Time required to charge the capacitor

- increases with R – lower current flow
- Increases with C - more charge on capacitor

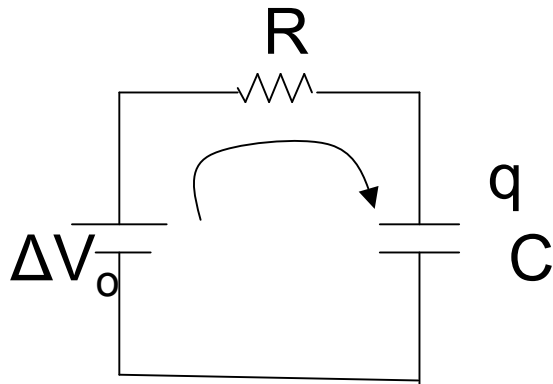
How does the time to charge the capacitor depend on R and C




Charging time τ_0

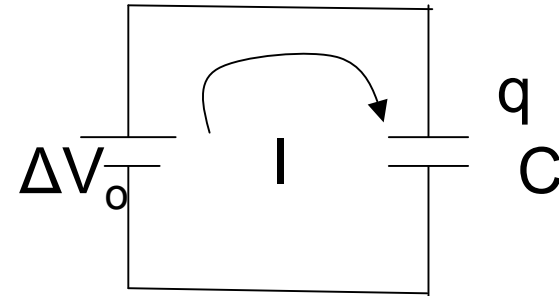

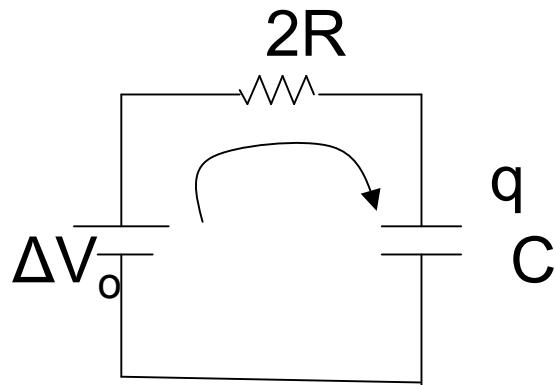shorter than τ_0 because the current is larger




longer than τ_0
the current is smaller

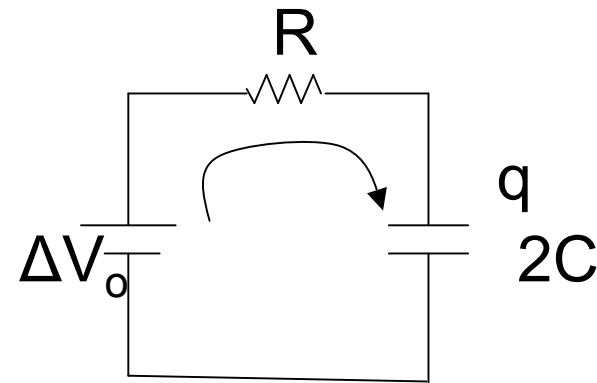

longer than τ_0
more charge is transferred

Discharging

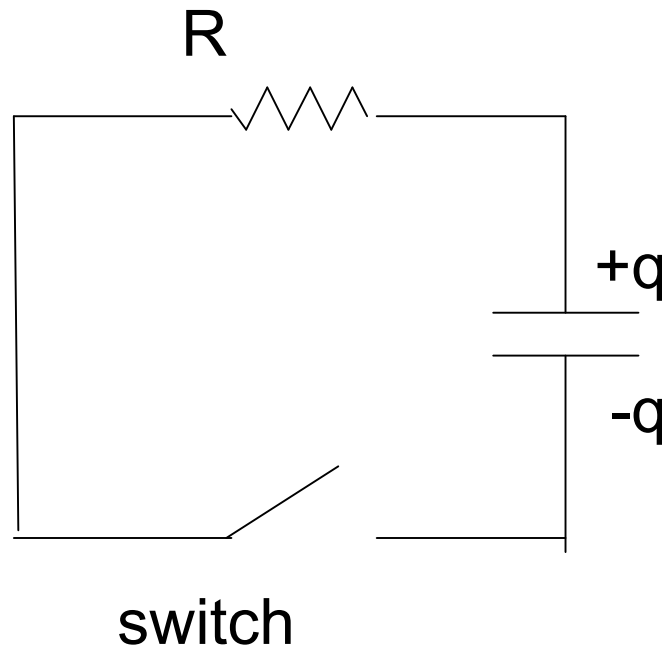

Switch off

Capacitor charged


$$C$$
$$\Delta V_c = \frac{q}{C}$$

When the switch is closed to discharge the capacitor the capacitor has a maximum charge of q_0 and maximum voltage V_0 .

As the capacitor discharges the charge and voltage decrease with time.

The current will also decrease with time.

Discharge

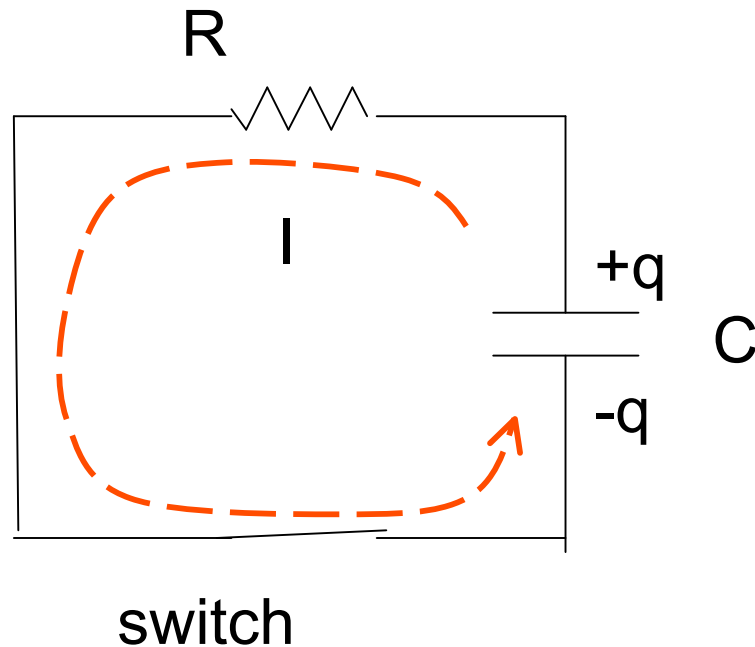

Switch on



Current flows

$$\Delta V_R = IR = \Delta V_C = \frac{q}{C}$$

$$I = -\frac{\Delta q}{\Delta t} = \frac{q}{RC}$$

$$q = q_0 e^{-\left(\frac{t}{\tau}\right)}$$

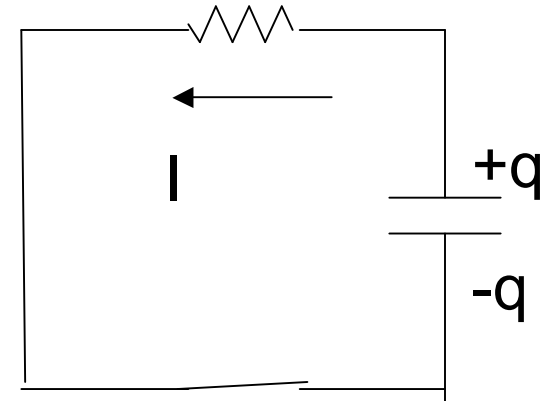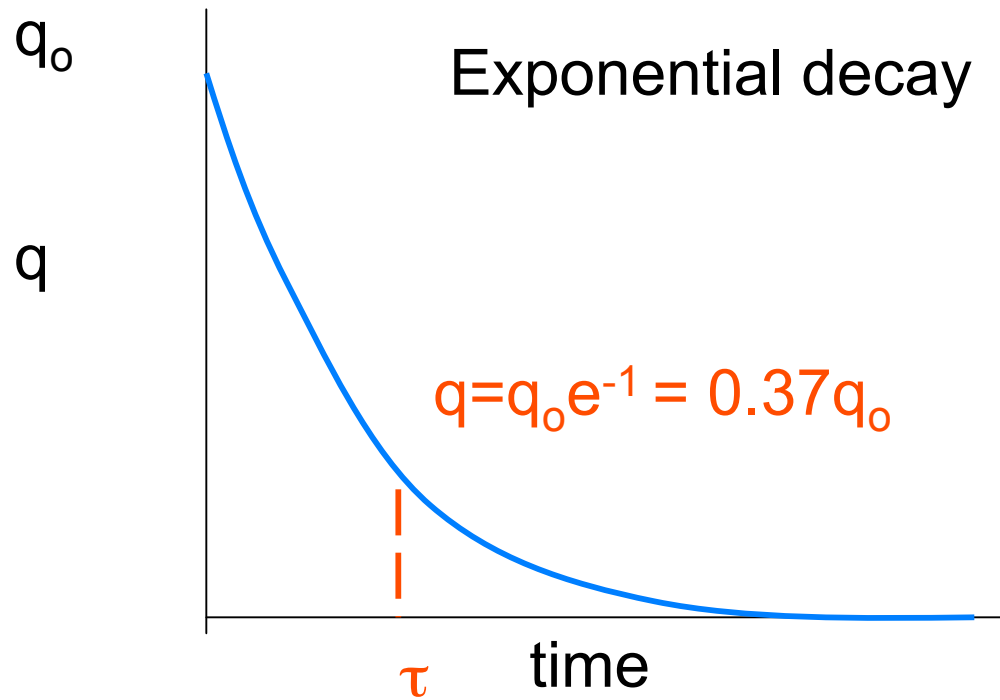The charge decays exponentially with time



$$\Delta V_C - \Delta V_R = 0$$

short times

intermediate
times

long times

$q =$	q_0	$q = q_0 e^{-\left(\frac{t}{\tau}\right)}$	0
-------	-------	--	-----


$\Delta V_C =$	ΔV_0	$\Delta V_C = V_0 e^{-\left(\frac{t}{\tau}\right)}$	0
----------------	--------------	---	-----

$I =$	$\frac{\Delta V_0}{R}$	$I = \frac{\Delta V_0}{R} e^{-\left(\frac{t}{\tau}\right)}$	0
-------	------------------------	---	-----

$$\tau = RC$$

Exponential decay

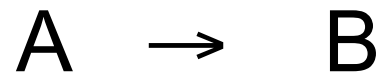Found in many other systems-
Chemical reaction, nuclear decay



When the rate of decay of a species is proportional to the amount of the species

$$\frac{\Delta A}{\Delta t} = -\frac{A}{\tau}$$

The result is exponential decay

$$A = A_0 e^{-\left(\frac{t}{\tau}\right)}$$

τ is a constant

A 12 μ farad capacitor is discharged through a 2 k Ω resistor. How long does it take for the voltage to decay to 5% of the initial voltage.

$$\tau = RC = 2 \times 10^3 (12 \times 10^{-6}) = 24 \times 10^{-3} \text{ s} = 24 \text{ ms}$$


$$V = V_0 e^{-\left(\frac{t}{\tau}\right)}$$

$$\frac{V}{V_0} = e^{-\left(\frac{t}{\tau}\right)}$$

$$\ln\left(\frac{V}{V_0}\right) = -\frac{t}{\tau}$$

$$t = -\tau \ln\frac{V}{V_0} = -24 \times 10^{-3} (\ln(0.05)) = 7.2 \times 10^{-2} \text{ s}$$

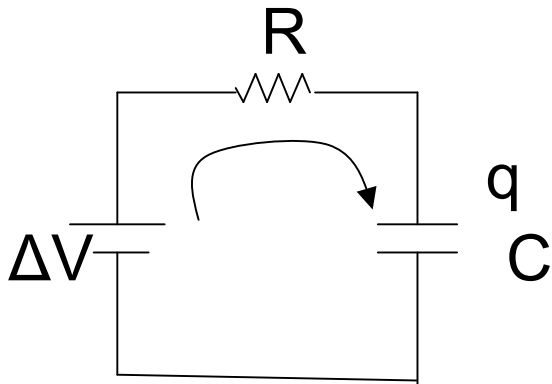33. Consider a series RC circuit for which $R=1.0\text{ M}\Omega$, $C=5.0\text{ }\mu\text{F}$ and $\varepsilon=30\text{ V}$. The capacitor is initially uncharged when the switch is open. (a) Find the charge on the capacitor 10 s after the switch is closed.



$$\tau = RC = 1 \times 10^6 (5 \times 10^{-6}) = 5.0 \text{ s}$$

$$q = q_0 (1 - e^{-\frac{t}{RC}}) = q_0 (1 - e^{-\frac{t}{\tau}})$$


$$C = \frac{q}{\Delta V}$$

$$q_0 = \Delta V C = 30 (5 \times 10^{-6}) = 1.5 \times 10^{-4} \text{ C}$$

$$q = q_0 (1 - e^{-\frac{t}{RC}}) = 1.5 \times 10^{-4} (1 - e^{-\frac{10}{5}})$$

$$q = 1.3 \times 10^{-4} \text{ C}$$

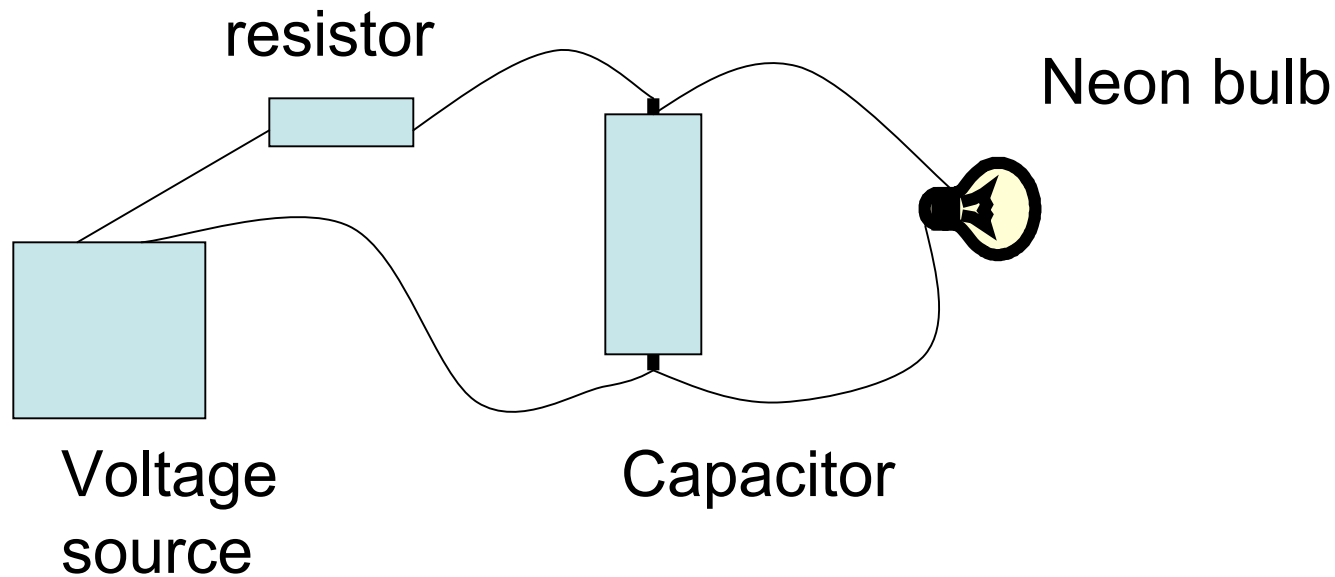You plan to make a flasher circuit that charges a capacitor through a resistor up to a voltage at which a neon bulb discharges (about 100V) about once every 5 sec. If you have a 10 microfarad capacitor what resistor do you need?




$$\tau = RC$$

$$R = \frac{\tau}{C} = \frac{5}{10 \times 10^{-6}} = 0.5 \times 10^6 \Omega$$


About
0.5M Ω

Charging

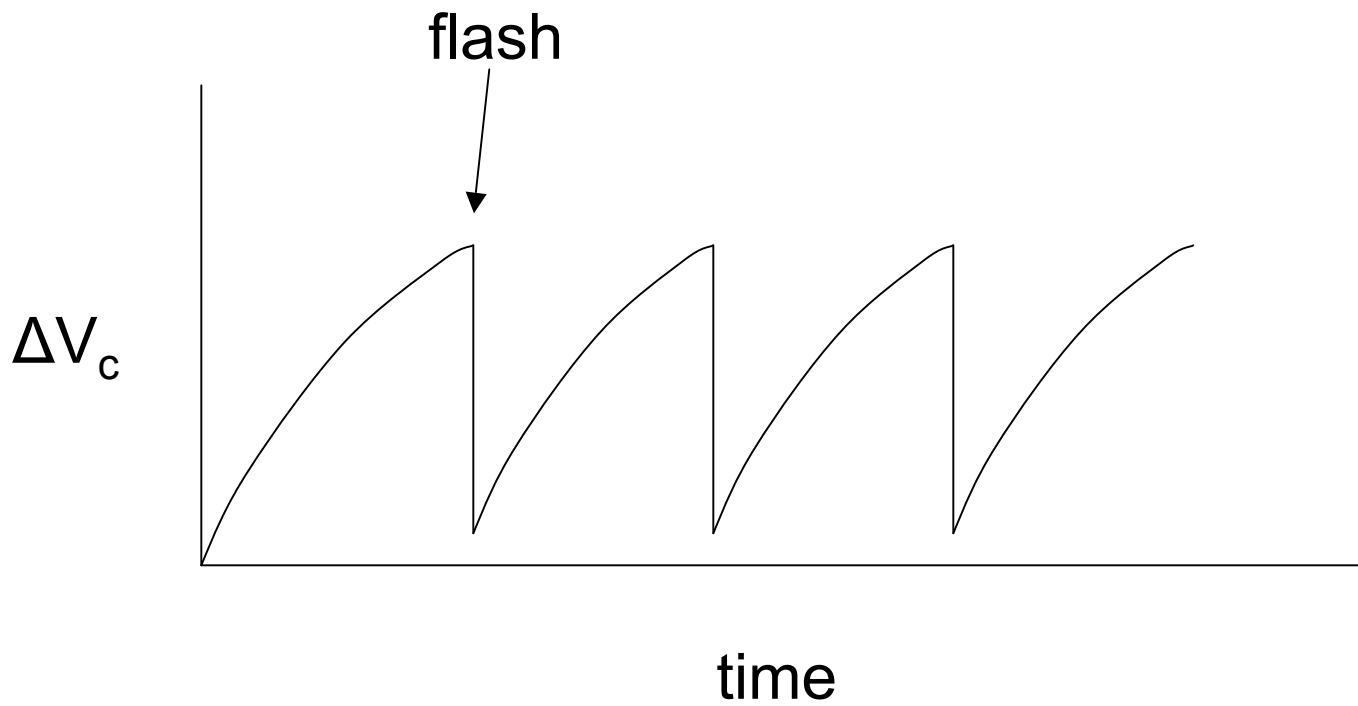

HW – Clickers Out

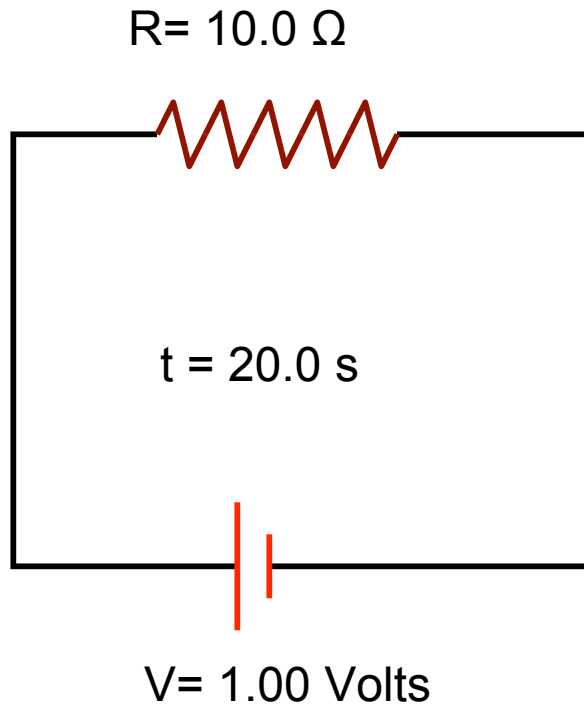
1) From 17.3: A 1.00 V potential difference is maintained across a 10.0 Ω resistor for a period of 20.0 s. What total charge passes through the wire in this time interval?



- A) 4 C
- B) 1 C
- C) can't determine
- D) 2 C



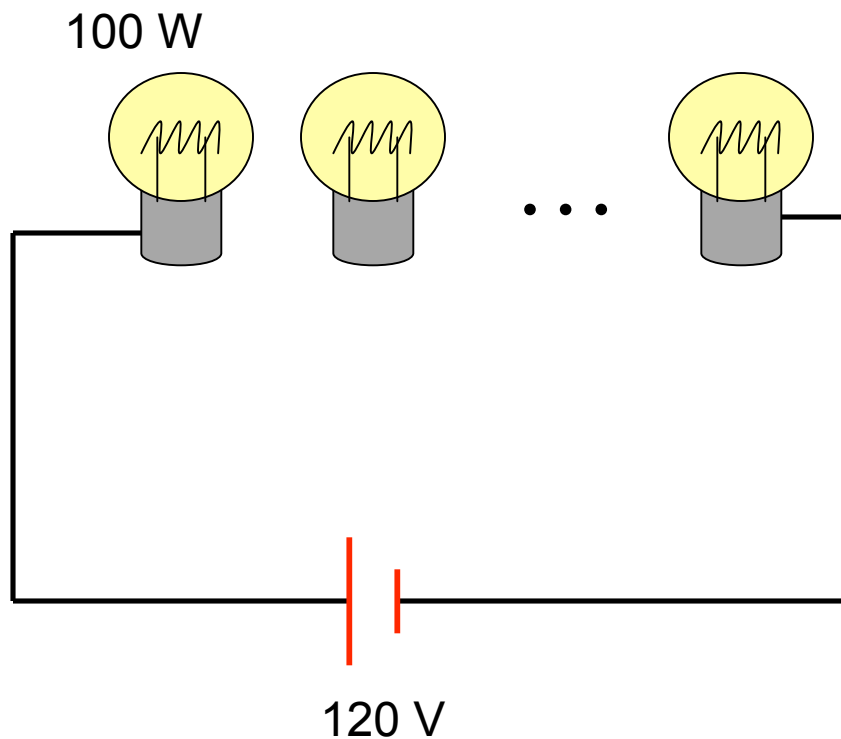2) From 17.33: How many 100 W light bulbs can you use in a 120 V circuit without tripping a 15 A circuit breaker? (the potential difference across each bulb is 120 V.)



- A) 1 bulb
- B) 18 bulbs
- C) 9 bulbs
- C) 10 bulbs




3) From 17.9: If the current carried by a conductor is doubled what happens to the charge carrier density?

- A) doubled
- B) unchanged
- C) halved



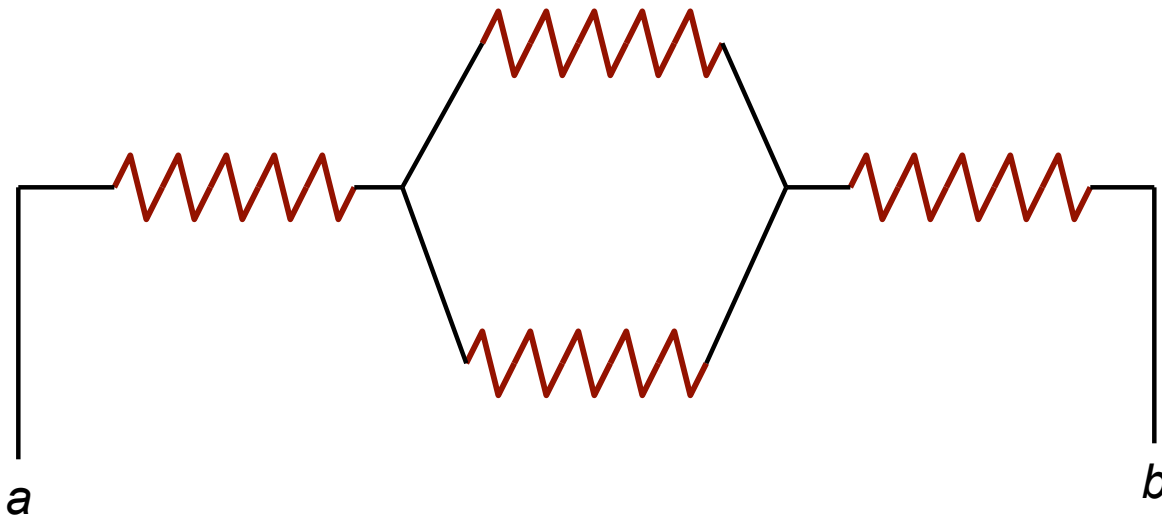
4) From 18.5: Find the equivalent resistance between points a and b in the figure.



- A) 2.4Ω
- B) 17.1Ω
- C) 30Ω
- D) 1.6Ω



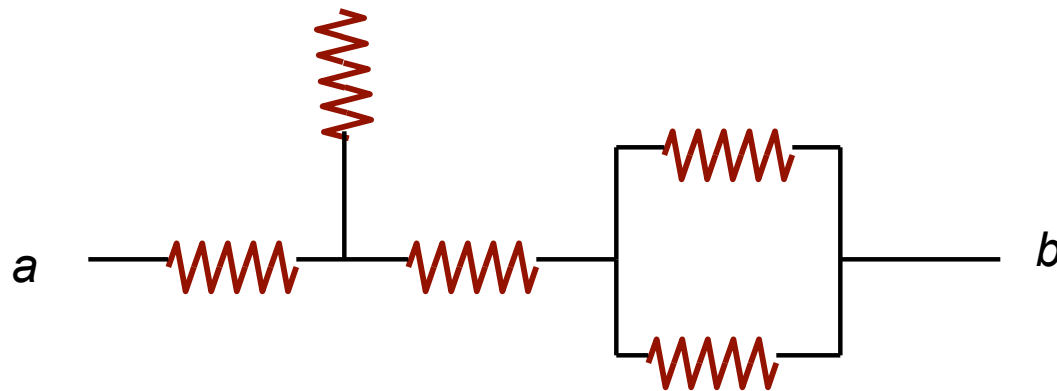
5) From 18.7: Find the equivalent resistance between points a and b in the figure. Each resistor has resistance R .



- A) $2.5 R$
- B) $5 R$
- C) $12.75 R$
- D) R



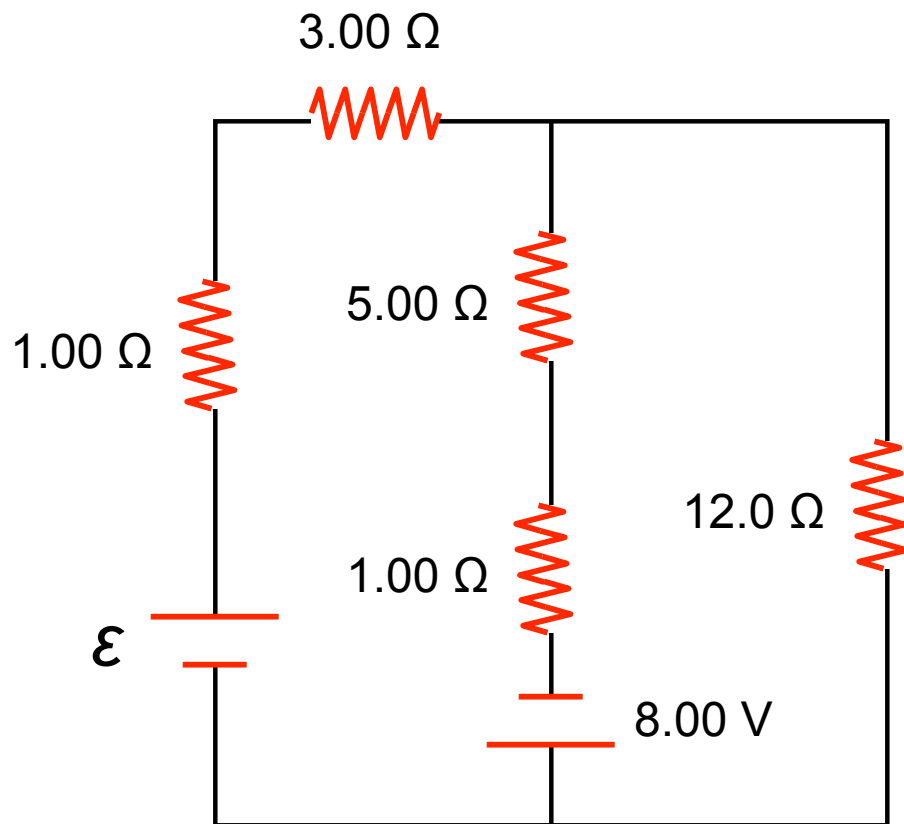6) From 18.21: What is the EMF of the battery in the following figure?



- A) $8.0\ \text{V}$
- B) $14.3\ \text{V}$
- C) $5.8\ \text{V}$
- D) $10.7\ \text{V}$

