

Chapter 18

Direct-Current Circuits

Problem Solutions

18.1 From $\Delta V = I(R + r)$, the internal resistance is

$$r = \frac{\Delta V}{I} - R = \frac{9.00 \text{ V}}{0.117 \text{ A}} - 72.0 \text{ } \Omega = \boxed{4.92 \text{ } \Omega}$$

18.3 For the bulb in use as intended,


$$R_{bulb} = \frac{(\Delta V)^2}{P} = \frac{(120 \text{ V})^2}{75.0 \text{ W}} = 192 \text{ } \Omega$$

Now, presuming the bulb resistance is unchanged, the current in the circuit shown is

$$I = \frac{\Delta V}{R_{eq}} = \frac{120 \text{ V}}{0.800 \text{ } \Omega + 192 \text{ } \Omega + 0.800 \text{ } \Omega} = 0.620 \text{ A}$$


and the actual power dissipated in the bulb is
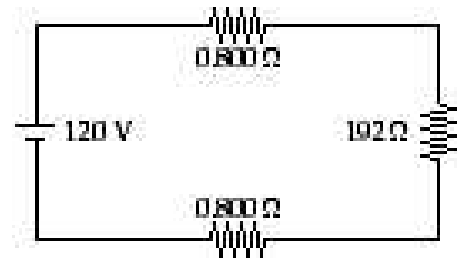
$$P = I^2 R_{bulb} = (0.620 \text{ A})^2 (192 \text{ } \Omega) = \boxed{73.8 \text{ W}}$$



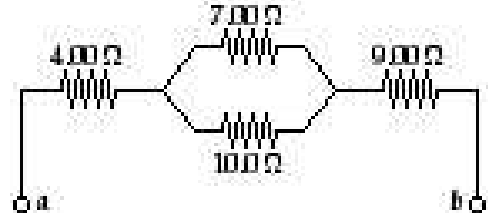- 18.5 (a) The equivalent resistance of the two parallel resistors is

$$R_p = \left(\frac{1}{7.00 \, \Omega} + \frac{1}{10.0 \, \Omega} \right)^{-1} = 4.12 \, \Omega$$



Thus,


$$R_{ab} = R_4 + R_p + R_9 = (4.00 + 4.12 + 9.00) \, \Omega = \boxed{17.1 \, \Omega}$$

(b) $I_{ab} = \frac{(\Delta V)_{ab}}{R_{ab}} = \frac{34.0 \, \text{V}}{17.1 \, \Omega} = 1.99 \, \text{A}$, so $I_4 = I_9 = 1.99 \, \text{A}$


Also, $(\Delta V)_p = I_{ab} R_p = (1.99 \, \text{A})(4.12 \, \Omega) = 8.18 \, \text{V}$

Then, $I_7 = \frac{(\Delta V)_p}{R_7} = \frac{8.18 \, \text{V}}{7.00 \, \Omega} = \boxed{1.17 \, \text{A}}$





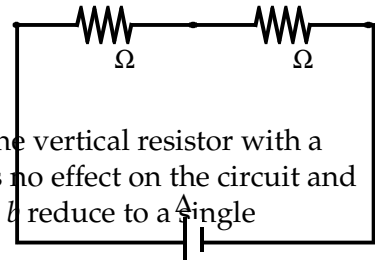
and $I_{10} = \frac{(\Delta V)_p}{R_{10}} = \frac{8.18 \, \text{V}}{10.0 \, \Omega} = \boxed{0.818 \, \text{A}}$



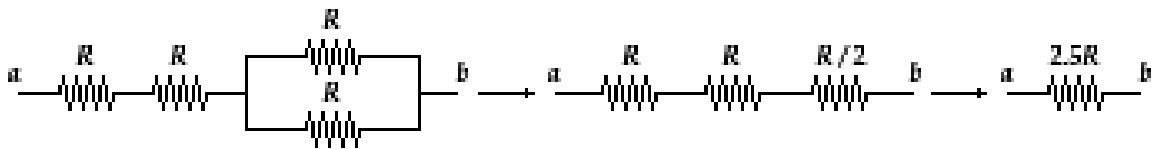- 18.7 If a potential difference is applied between points a and b , the vertical resistor with a free end is not part of any closed current path. Hence, it has no effect on the circuit and can be ignored. The remaining four resistors between a and b reduce to a single equivalent resistor, $R_{eq} = \boxed{2.5R}$, as shown below:



- 18.13 The resistors in the circuit can be combined in the stages shown below to yield an equivalent resistance of $R_{ad} = (63/11) \Omega$.

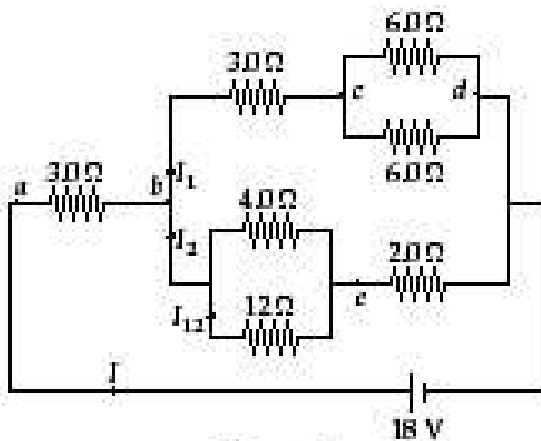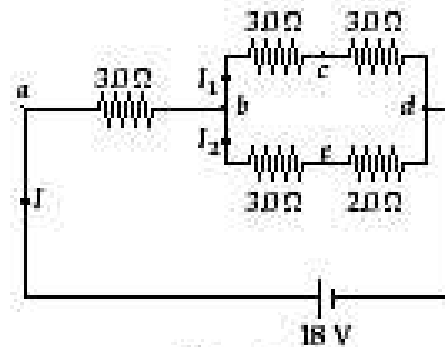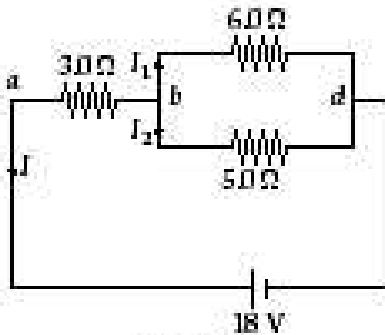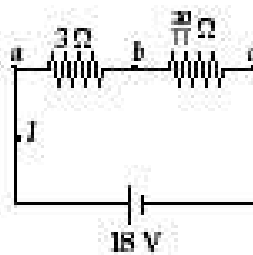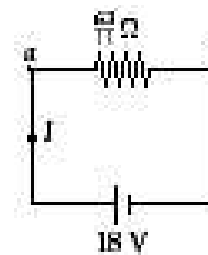
Figure 1

Figure 2

Figure 3

Figure 4

Figure 5

From Figure 5,
$$I = \frac{(\Delta V)_{ad}}{R_{ad}} = \frac{18 \text{ V}}{(63/11) \Omega} = 3.14 \text{ A}$$

Then, from Figure 4, $(\Delta V)_{bd} = IR_{bd} = (3.14 \text{ A})(30/11 \Omega) = 8.57 \text{ V}$

Now, look at Figure 2 and observe that

$$I_2 = \frac{(\Delta V)_{bd}}{3.0 \Omega + 2.0 \Omega} = \frac{8.57 \text{ V}}{5.0 \Omega} = 1.71 \text{ A}$$

so $(\Delta V)_{be} = I_2 R_{be} = (1.71 \text{ A})(3.0 \Omega) = 5.14 \text{ V}$

Finally, from Figure 1,
$$I_{12} = \frac{(\Delta V)_{be}}{R_{12}} = \frac{5.14 \text{ V}}{12 \Omega} = \boxed{0.43 \text{ A}}$$

- 18.17 We name the currents I_1 , I_2 , and I_3 as shown. Using Kirchhoff's loop rule on the rightmost loop gives

$$+12.0 \text{ V} - (1.00 + 3.00) I_3 - (5.00 + 1.00) I_2 - 4.00 \text{ V} = 0$$

or $(2.00) I_3 + (3.00) I_2 = 4.00 \text{ V}$ (1)

Applying the loop rule to the leftmost loop yields

$$+4.00 \text{ V} + (1.00 + 5.00) I_2 - (8.00) I_1 = 0$$

or $(4.00) I_1 - (3.00) I_2 = 2.00 \text{ V}$ (2)

From Kirchhoff's junction rule, $I_1 + I_2 = I_3$ (3)


Solving equations (1), (2) and (3) simultaneously gives

$$I_1 = 0.846 \text{ A}, I_2 = 0.462 \text{ A}, \text{ and } I_3 = 1.31 \text{ A}$$

All currents are in the directions indicated by the arrows in the circuit diagram.

- 18.21 First simplify the circuit by combining the series resistors. Then, apply Kirchhoff's junction rule at point a to find

$$I_1 + I_2 = 2.00 \text{ A}$$

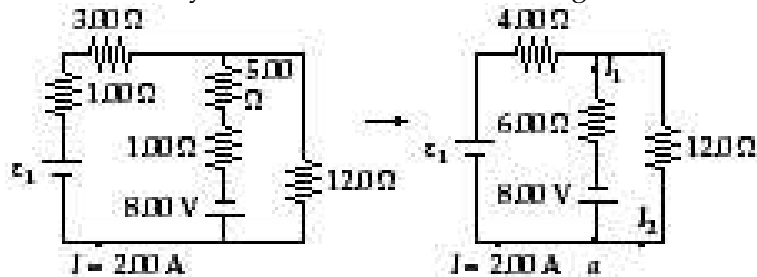

Next, we apply Kirchhoff's loop rule to the rightmost loop to obtain

$$-8.00 \text{ V} + (6.00) I_1 - (12.0) I_2 = 0$$

or $-8.00 \text{ V} + (6.00) I_1 - (12.0)(2.00 \text{ A} - I_1) = 0$ This yields $I_1 = 1.78 \text{ A}$

Finally, apply Kirchhoff's loop rule to the leftmost loop to obtain

$$+\varepsilon_1 - (4.00)(2.00 \text{ A}) - (6.00) I_1 + 8.00 \text{ V} = 0$$

or $\varepsilon_1 = (4.00)(2.00 \text{ A}) + (6.00)(1.78 \text{ A}) - 8.00 \text{ V} = 10.7 \text{ V}$

18.26 Using Kirchhoff's loop rule on the outer perimeter of the circuit gives

$$+12 \text{ V} - (0.01) I_1 - (0.06) I_3 = 0$$

$$\text{or } I_1 + 6I_3 = 1.2 \times 10^3 \text{ A} \quad (1)$$

For the rightmost loop, the loop rule gives

$$+10 \text{ V} + (1.00) I_2 - (0.06) I_3 = 0$$


$$\text{or } I_2 - 0.06I_3 = -10 \text{ A} \quad (2)$$

Applying Kirchhoff's junction rule at either junction gives

$$I_1 = I_2 + I_3 \quad (3)$$

Solving equations (1), (2), and (3) simultaneously yields
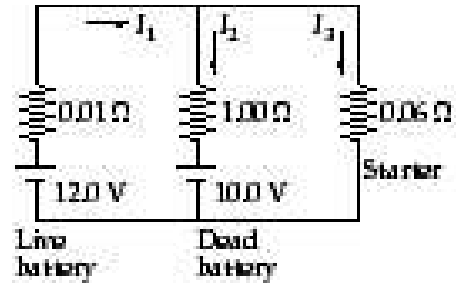
$$I_2 = 0.28 \text{ A (in dead battery)} \text{ and } I_3 = 1.7 \times 10^2 \text{ A (in starter)}$$



18.31 (a) $\tau = RC = (2.0 \times 10^6 \Omega)(6.0 \times 10^{-6} \text{ F}) = \boxed{12 \text{ s}}$

(b) $Q_{\text{max}} = C\varepsilon = (6.0 \times 10^{-6} \text{ F})(20 \text{ V}) = \boxed{1.2 \times 10^{-4} \text{ C}}$

18.33 $Q_{\text{max}} = C\varepsilon = (5.0 \times 10^{-6} \text{ F})(30 \text{ V}) = 1.5 \times 10^{-4} \text{ C}$, and

$$\tau = RC = (1.0 \times 10^6 \Omega)(5.0 \times 10^{-6} \text{ F}) = 5.0 \text{ s}$$

Thus, at $t = 10 \text{ s} = 2\tau$

$$Q = Q_{\text{max}}(1 - e^{-t/\tau}) = (1.5 \times 10^{-4} \text{ C})(1 - e^{-2}) = \boxed{1.3 \times 10^{-4} \text{ C}}$$

18.35 From $Q = Q_{\max}(1 - e^{-t/\tau})$, we have at $t = 0.900 \text{ s}$,

$$\frac{Q}{Q_{\max}} = 1 - e^{-0.900 \text{ s}/\tau} = 0.600$$

Thus, $e^{-0.900 \text{ s}/\tau} = 0.400$, or $-\frac{0.900 \text{ s}}{\tau} = \ln(0.400)$

giving the time constant as $\tau = -\frac{0.900 \text{ s}}{\ln(0.400)} = \boxed{0.982 \text{ s}}$

$R (\Omega)$	$P_L (\text{W})$
1.00	1.19
5.00	3.20
10.0	3.60
15.0	3.46
20.0	3.20
25.0	2.94
30.0	2.70

The curve peaks at $P_L = 3.60 \text{ W}$ at a load resistance of $R = 10.0 \Omega$.