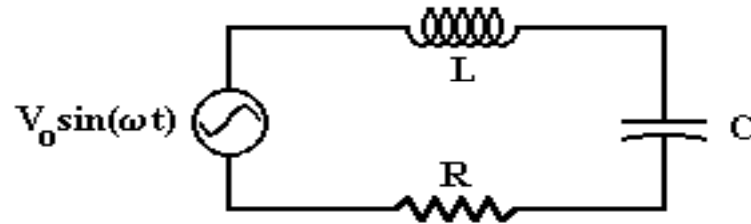


Experiment 3: Resonance in LRC Circuits Driven by Alternating Current

Goal: examine LRC series circuit driven by AC

1. Determine quality factor, resonance frequency, and bandwidth
2. Measure phase shift (extra credit)



Complex Impedance

The complex generalization of resistance is impedance $Z = \frac{\tilde{V}}{\tilde{I}}$

$\tilde{V} = V_0 e^{i\omega t} = Z \tilde{I}$ $\tilde{I} = I_0 e^{i(\omega t + \phi)}$ ϕ is the amount by which \tilde{V} and \tilde{I} are out of phase

a capacitor

$$V_C = \frac{Q}{C} = \frac{1}{C} \int I dt \quad \frac{dV_C}{dt} = \frac{I}{C}$$

$$\begin{aligned} \tilde{I} &= C \frac{d}{dt} (V_{C0} e^{i\omega t}) \\ &= i\omega C (V_{C0} e^{i\omega t}) \\ &= i\omega C (Z_C \tilde{I}) \end{aligned}$$

$$Z_C = \frac{1}{i\omega C}$$

an inductor

$$V_L = L \frac{dI}{dt}$$



$$\begin{aligned} \tilde{V}_L &= L \frac{d}{dt} \left(\frac{\tilde{V}_L}{Z_L} \right) \\ &= \frac{i\omega L}{Z_L} V_{L0} e^{i\omega t} \\ &= \frac{i\omega L}{Z_L} \tilde{V}_L \end{aligned}$$

$$Z_L = i\omega L$$

Complex Numbers

$$c = a + ib$$

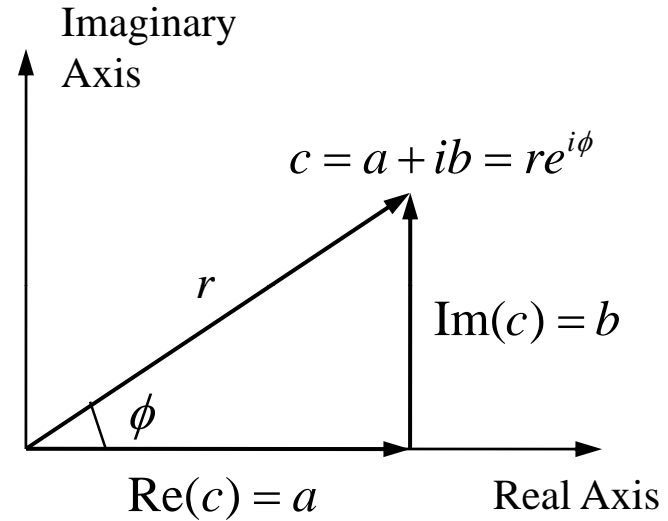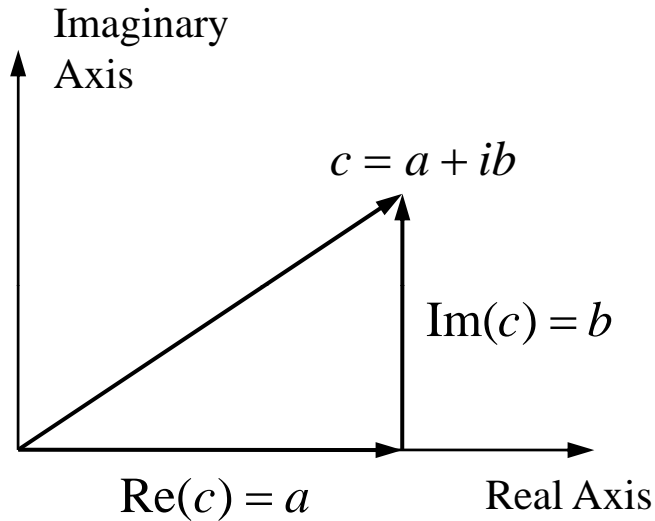a and b are real numbers, $i = \sqrt{-1}$



relationships between Cartesian and polar coordinates


$$r = \sqrt{a^2 + b^2}$$

$$a = r \cos(\theta)$$

$$\theta = \arctan\left(\frac{b}{a}\right)$$

$$b = r \sin(\theta)$$

LRC Series Circuit Driven by AC

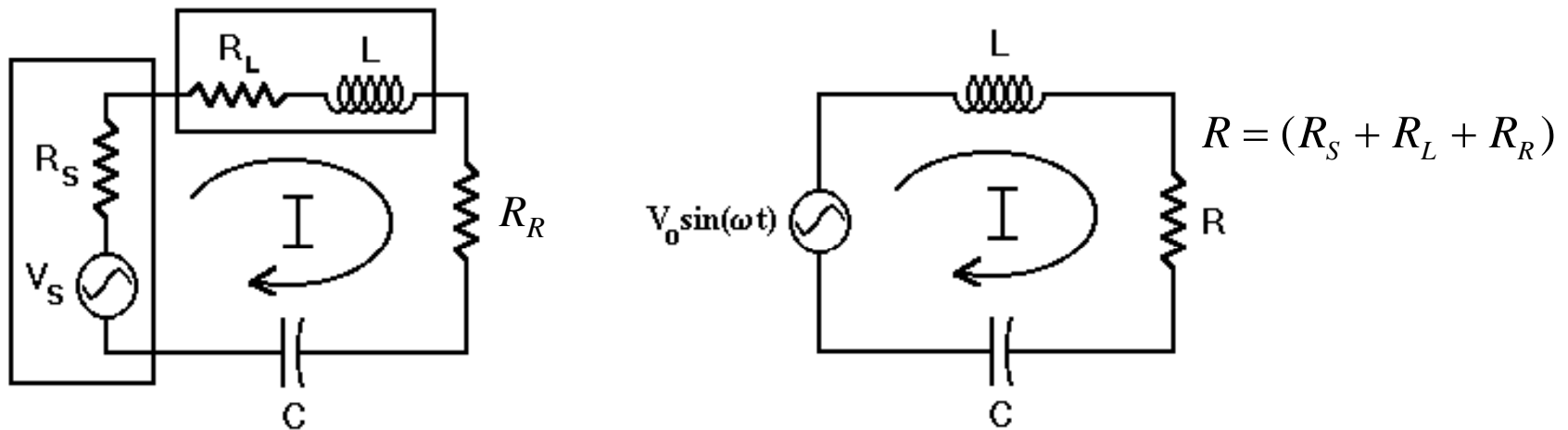

R is the total resistance in the loop
 R_R is the resistance of only the resistor

Kirchhoff's Law $V_S + V_L + V_R + V_C = 0$

$$V_S - I(Z_L + Z_R + Z_C) = 0 \rightarrow V_S = I \left(i\omega L + R + \frac{1}{i\omega C} \right)$$

$$c = a + ib = re^{i\phi}$$

$$r = \sqrt{a^2 + b^2}$$

$$\theta = \arctan\left(\frac{b}{a}\right)$$

$$V_S - I(Z_L + Z_R + Z_C) = 0 \rightarrow V_S = I\left(i\omega L + R + \frac{1}{i\omega C}\right)$$

the total impedance

$$\left[R + i\left(\omega L - \frac{1}{\omega C}\right) \right] = \sqrt{R^2 + L^2\left(\omega - \frac{1}{\omega LC}\right)^2} \exp\left[i \arctan\left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)\right]$$

$$|Z_{Total}| = \sqrt{R^2 + L^2\left(\omega - \frac{1}{\omega LC}\right)^2} = R \sqrt{1 + Q^2\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^2}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}, \text{ and } Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{\omega_0 RC}$$

$$\phi = \arctan\left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right) = \arctan\left[Q\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)\right]$$

$$\tilde{V} = V_0 e^{i\omega t}$$

$$\tilde{V} = \tilde{I} Z$$

$$V_0 e^{i\omega t} = \tilde{I} |Z_{total}| e^{i\phi}$$

$$\tilde{I} = \frac{V_0}{|Z_{total}|} e^{i(\omega t - \phi)}$$

Voltage over the resistor



$$|V_R| = |I||Z_R| = V_0 \frac{|Z_R|}{|Z_{Total}|}$$

$$= \frac{V_0 R_R}{R \sqrt{1 + Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}}$$

V_R is greatest when $\omega = \omega_0$
 ↑
resonance frequency


power $P \propto V^2$

the half power points occur when the voltage decreases to $1/\sqrt{2}$ of its peak value, which happens at $\omega = \omega_1$ and $\omega = \omega_2$

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}} \rightarrow Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2 = 1 \rightarrow \boxed{Q = \frac{\omega_0}{\omega_2 - \omega_1}} \leftarrow \text{bandwidth}$$

↑
way to measure Q

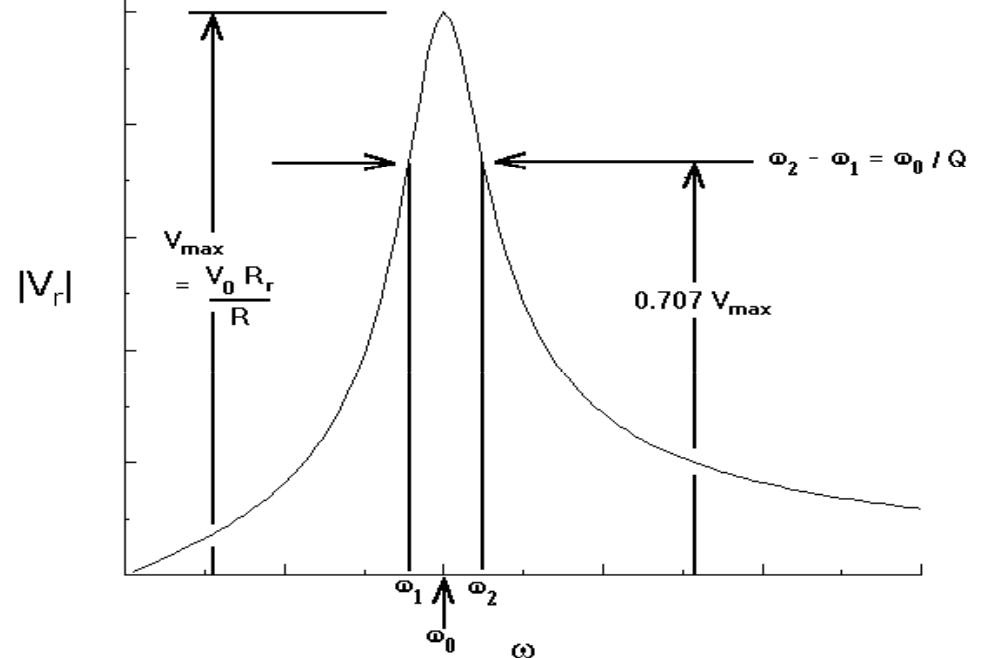the response function of the LRC series circuit



The Q multiplier

$$|Z_{total}| = R \sqrt{1 + Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}$$

$$\underline{|Z_{total}| = R \text{ at } \omega = \omega_0}$$

voltage over the capacitor
at $\omega = \omega_0$


$$V_{C0} \equiv |V_C(\omega_0)| = \frac{V_0}{|Z_{total}|} \frac{1}{\omega_0 C} = \frac{V_0}{R} \frac{1}{\omega_0 C} = \frac{V_0}{R} \sqrt{\frac{L}{C}} = V_0 Q$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{V_{C0}}{V_0}$$

way to measure Q

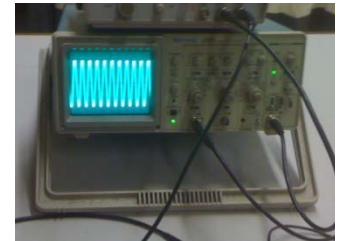


Voltage Phase Offsets of Circuit Elements

for a resistor


$$\tilde{V}_R = \tilde{I}Z_R = \tilde{I}R_R = \frac{V_0}{|Z_{total}|} R_R e^{i(\omega t - \phi)}$$

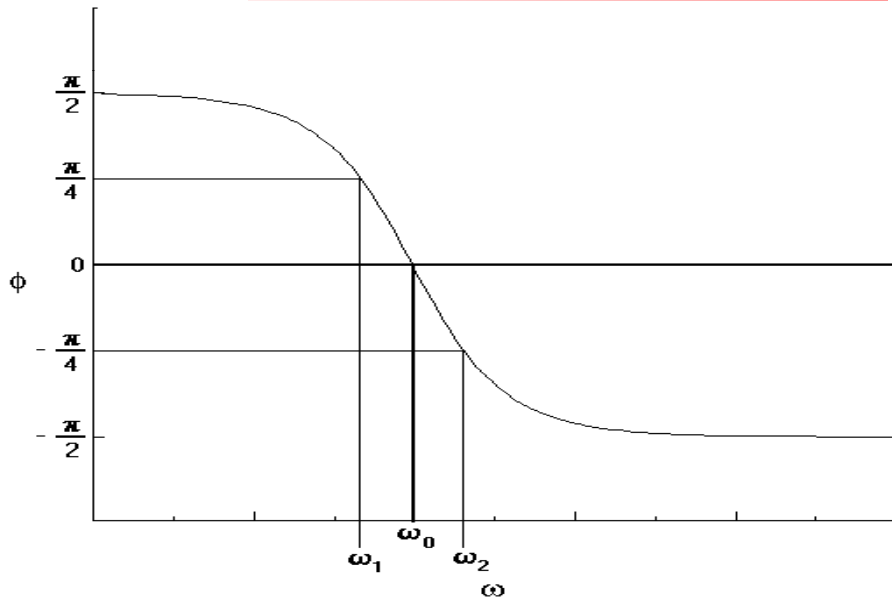where $\phi = \phi_R(\omega) \equiv -\arctan\left(Q\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)\right)$



following same procedure:
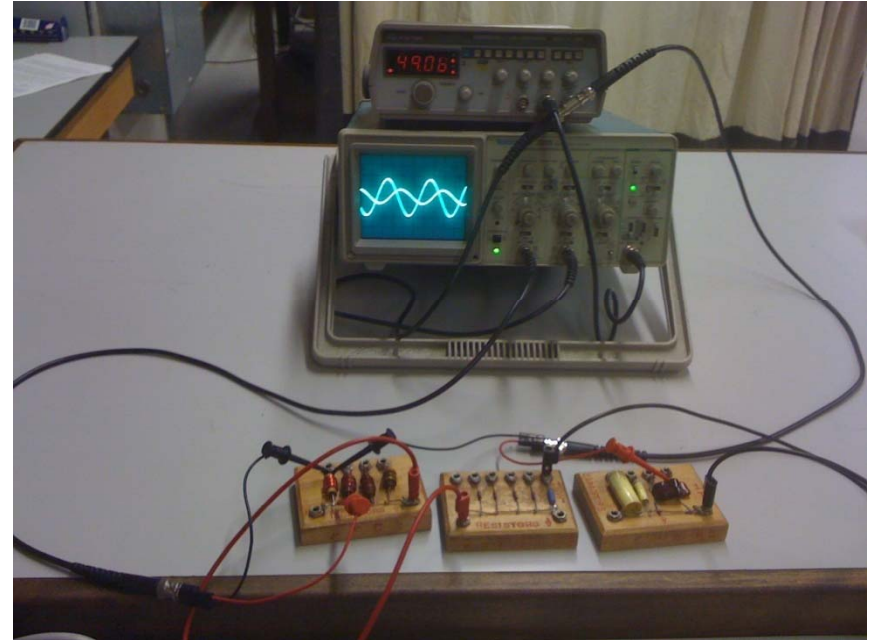
$$\phi_L(\omega) \equiv -\arctan\left(Q\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)\right) + \frac{\pi}{2}$$




$$\phi_R(\omega_1) \equiv -\arctan(-1) = \frac{\pi}{4}$$

$$\phi_R(\omega_0) \equiv 0$$


$$\phi_R(\omega_2) \equiv -\arctan(+1) = -\frac{\pi}{4}$$

$$\phi_C(\omega) \equiv -\arctan\left(Q\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)\right) - \frac{\pi}{2}$$

Limiting Distributions

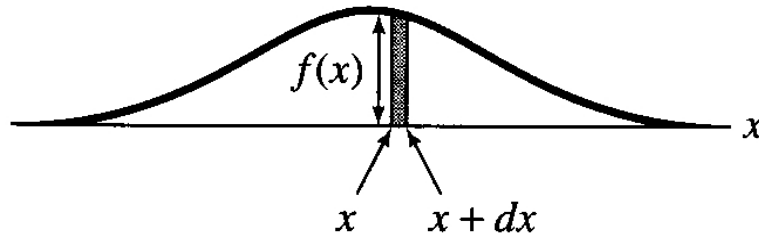

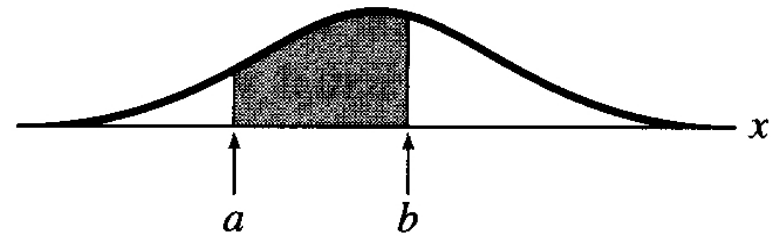
$f(x) dx$ = fraction of measurements
that fall between x and $x+dx$
= probability that any
measurement will give an
answer between x and $x+dx$



$\int_a^b f(x) dx$ = fraction of measurements
that fall between $x=a$ and $x=b$
= probability that any
measurement will give an
answer between $x=a$ and $x=b$


$$\int_{-\infty}^{+\infty} f(x) dx = 1 \quad \text{normalization condition}$$

The Gauss, or Normal Distribution

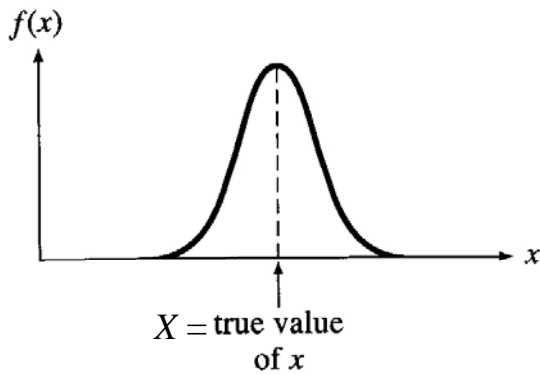

the limiting distribution for a measurement subject to many small random errors is bell shaped and centered on the true value of x

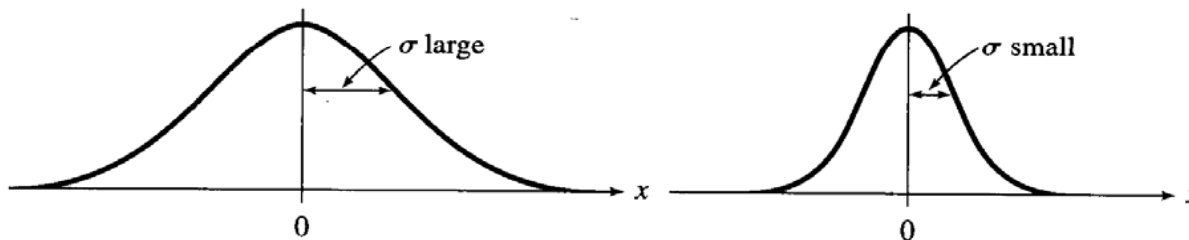the mathematical function that describes the bell-shape curve is called the normal distribution, or Gauss function



prototype function

$$e^{-x^2/2\sigma^2}$$

$$e^{-(x-X)^2/2\sigma^2}$$

σ – width parameter

X – true value of x


The Gauss, or Normal Distribution

normalize $e^{-(x-X)^2/2\sigma^2} \longrightarrow \int_{-\infty}^{+\infty} f(x)dx = 1$


↓

$$G_{X,\sigma}(x) = \frac{1}{\sigma\sqrt{2\pi}} e^{-(x-X)^2/2\sigma^2}$$

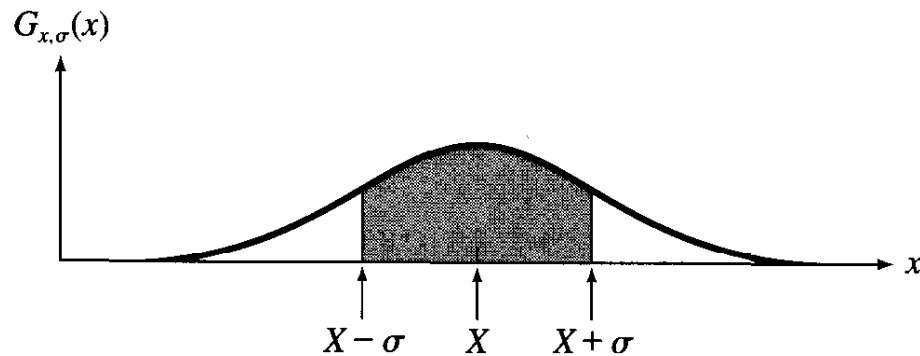standard deviation $\sigma_x =$ width parameter of the Gauss function σ
the mean value of $x =$ true value X



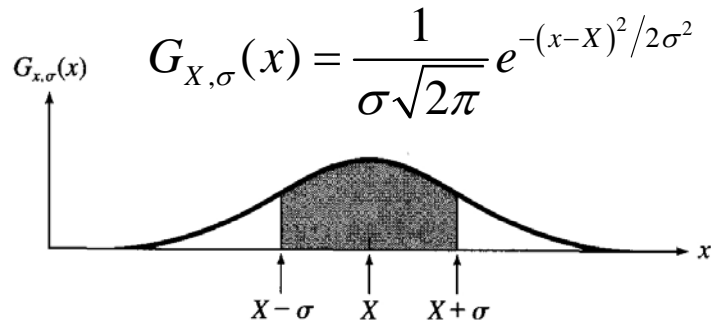
The standard Deviation as 68% Confidence Limit



$$\text{Prob}(\text{within } \sigma) = \int_{X-\sigma}^{X+\sigma} G_{X,\sigma}(x) dx$$

$$= \frac{1}{\sigma\sqrt{2\pi}} \int_{X-\sigma}^{X+\sigma} e^{-(x-X)^2/2\sigma^2} dx$$

$$(x - X) / \sigma = z$$

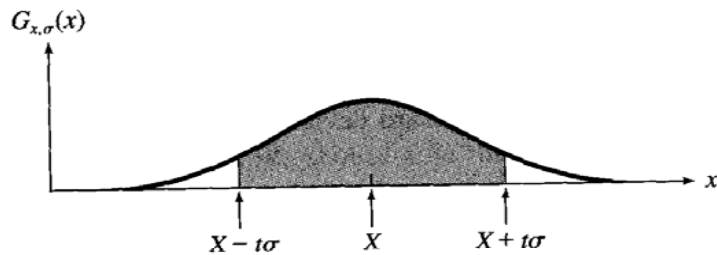

$$\text{Prob}(\text{within } \sigma) = \frac{1}{\sqrt{2\pi}} \int_{-1}^1 e^{-z^2/2} dz$$

$$\text{Prob}(\text{within } t\sigma) = \frac{1}{\sqrt{2\pi}} \int_{-t}^t e^{-z^2/2} dz$$

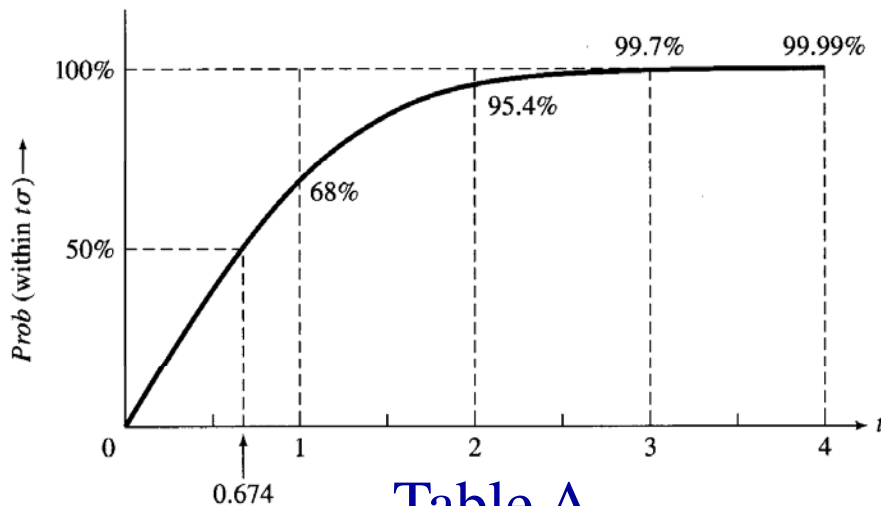


Table A.

← $erf(t)$ – error function

the probability that a measurement will fall within one standard deviation of the true answer is 68 %

$$x = x_{best} \pm \delta x \quad \delta x = \sigma$$