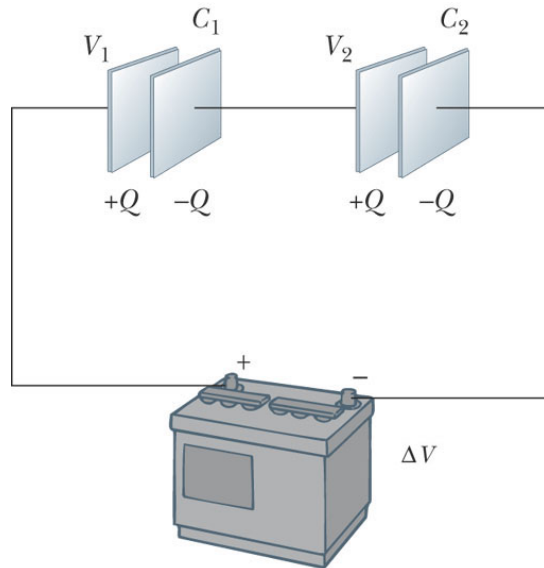



Connecting Capacitors in Series and in Parallel

Goal: find “equivalent” capacitance of a single capacitor (simplifies circuit diagrams and makes it easier to calculate circuit properties)

Find C_{eq} in terms of C_1, C_2, \dots to satisfy $C_{eq} = Q/\Delta V$




(a)

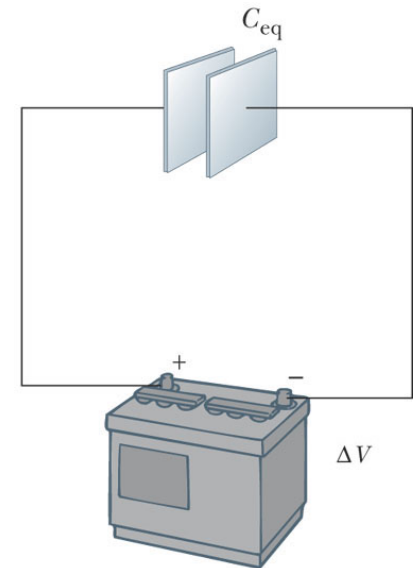


(b)


Capacitors in Parallel

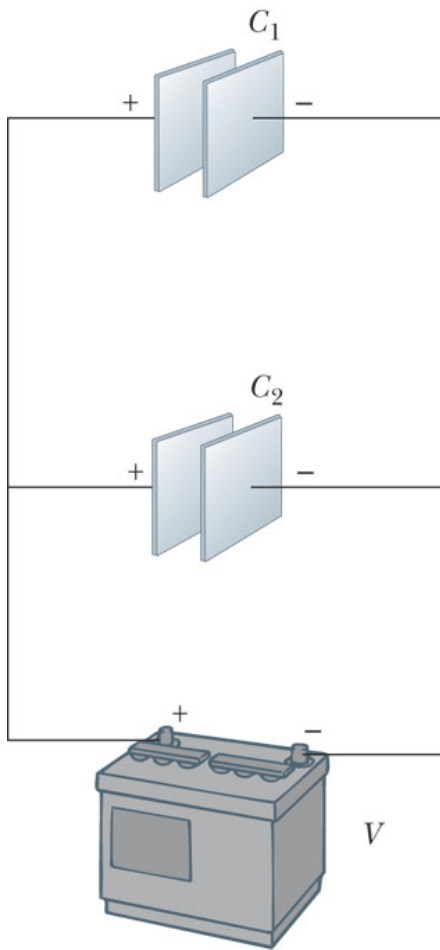

(a)

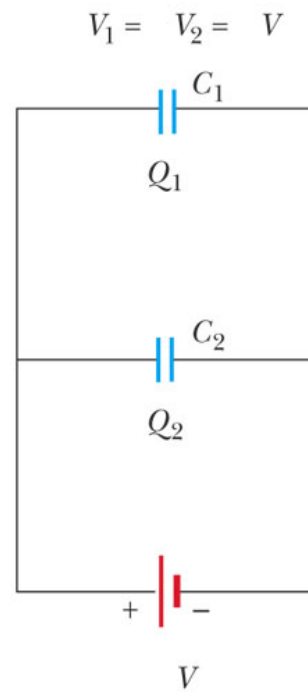


(b)

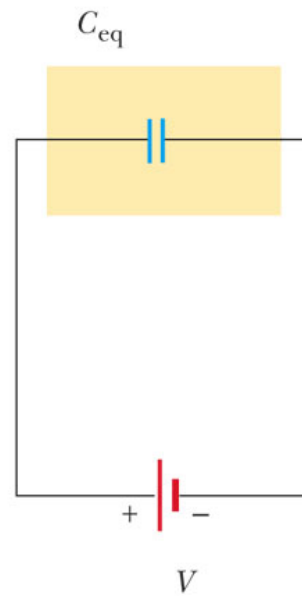

(c)

Capacitors in Parallel

$$\Delta V_1 = \Delta V_2 = \Delta V$$

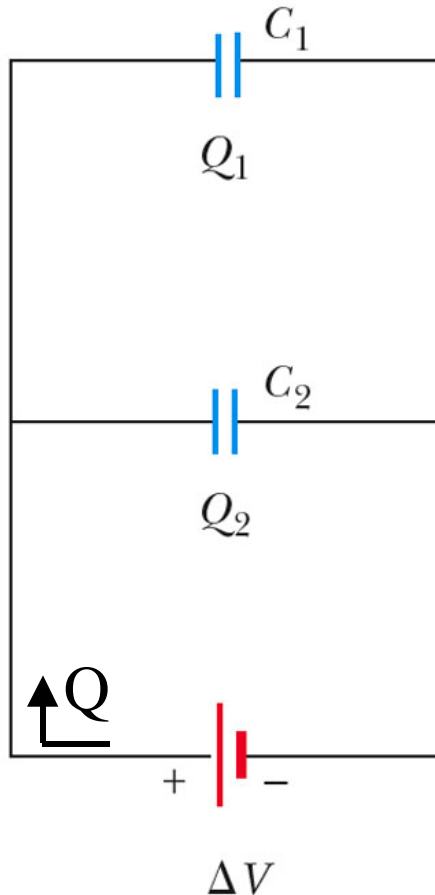

Note that both capacitors are held are same potential difference ΔV :

$$\Delta V_1 = \Delta V_2 = \Delta V$$


$$\text{Total charge } Q = Q_1 + Q_2$$

$$Q = C_1\Delta V + C_2\Delta V$$

$$C_{\text{eq}} = Q/\Delta V = (C_1\Delta V + C_2\Delta V)/\Delta V$$

$$C_{\text{eq}} = C_1 + C_2$$

Capacitors in Parallel

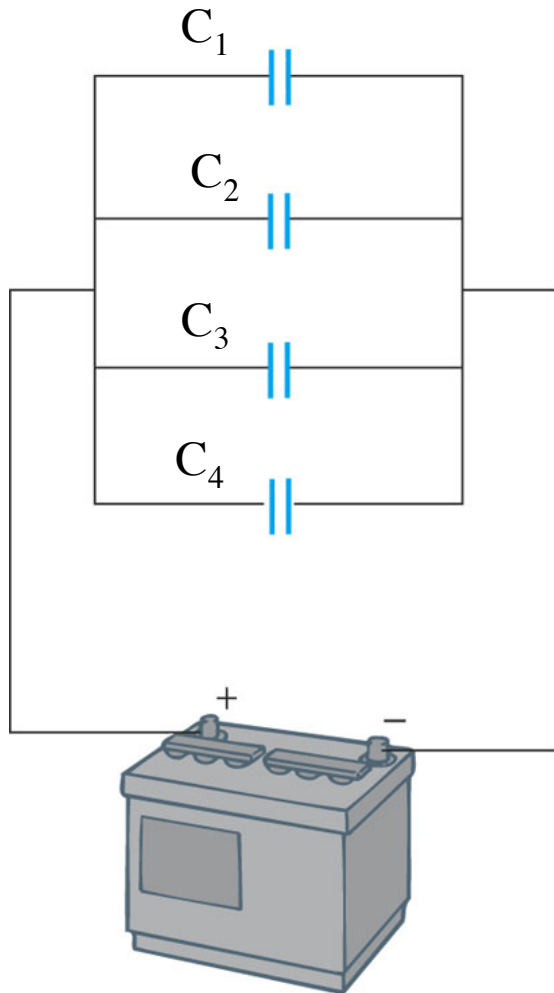

For N capacitors in parallel:


$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

C_{eq} bigger than any individual C

akin to having larger area:

$$\text{Area}(C_{eq}) = \text{Area}_1 + \text{Area}_2 + \dots$$


Capacitors in Parallel

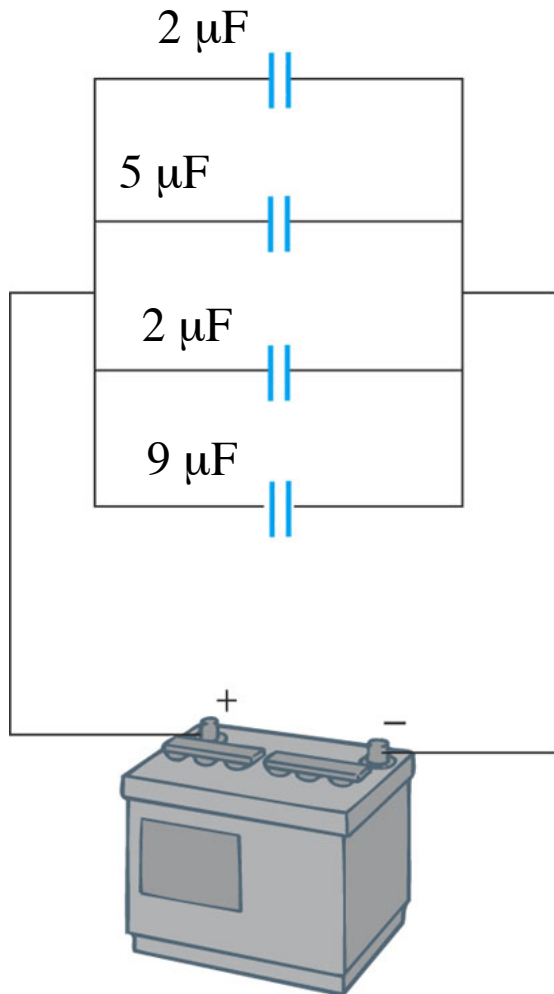


Example: Calculate C_{eq}

$$C_{\text{eq}} = 2+5+2+9\ \mu\text{F} = 18\mu\text{F}$$

Capacitors in Series

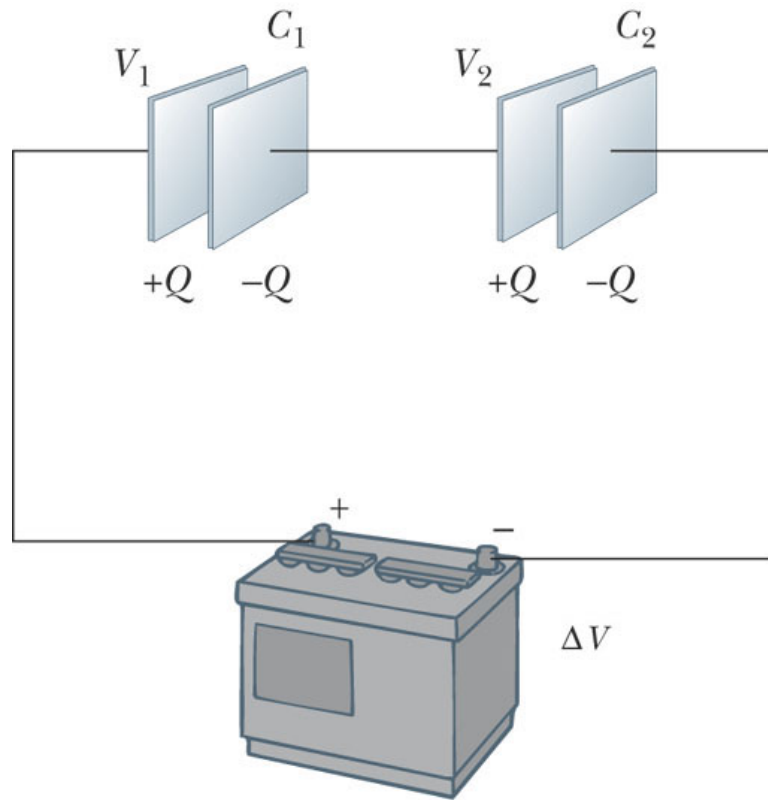


(a)

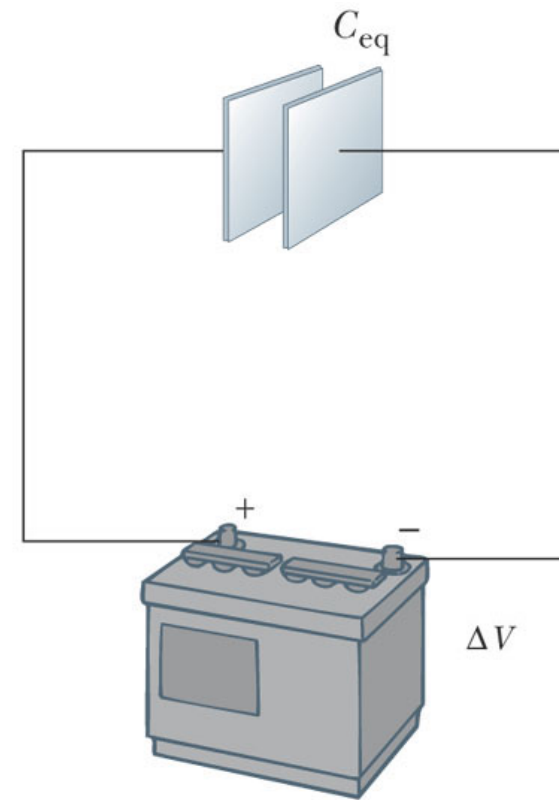

(b)

Capacitors in Series

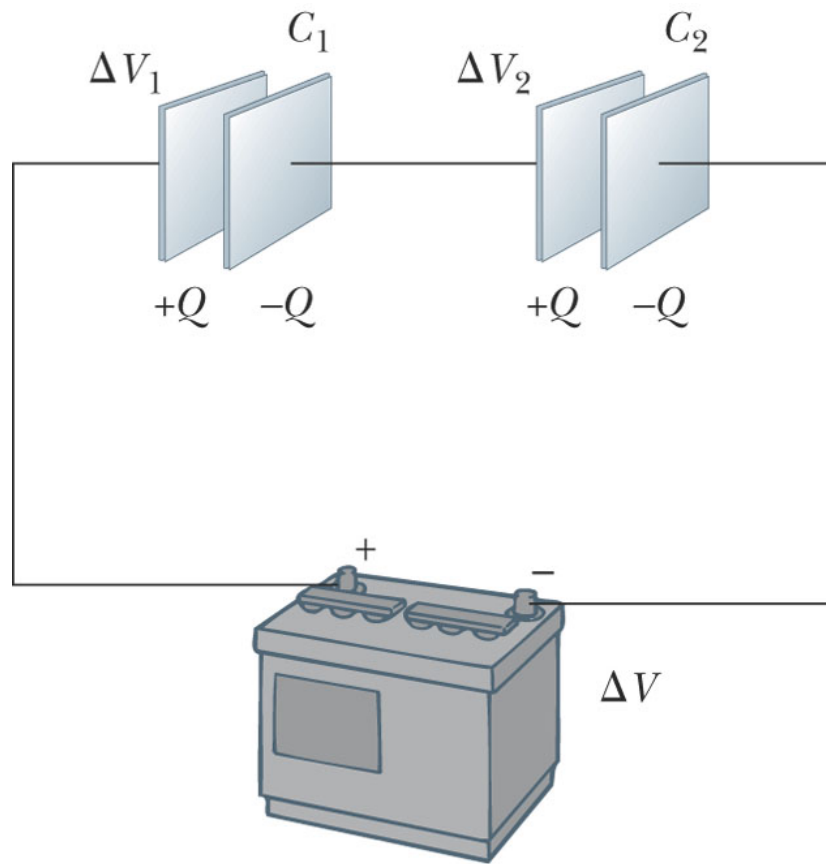

(a)

Note both capacitors' left plates have equal positive charge, $+Q$ (and right plates each have $-Q$)

$$\text{Also: } \Delta V = \Delta V_1 + \Delta V_2$$

$$\Delta V = Q/C_1 + Q/C_2$$

$$C_{\text{eq}} = Q/\Delta V$$

$$1/C_{\text{eq}} = \Delta V/Q$$

$$1/C_{\text{eq}} = (Q/C_1 + Q/C_2)/Q$$

$$\mathbf{1/C_{eq} = 1/C_1 + 1/C_2}$$

Capacitors in Series

For N capacitors in series:

$$1/C_{\text{eq}} = 1/C_1 + 1/C_2 + 1/C_3 + \dots + 1/C_N$$

C_{eq} smaller than any
individual C

Capacitors in Series


Example: Find C_{eq} .

$$\begin{aligned} 1/C_{eq} &= \\ 1/(15\mu\text{F}) + 1/(10\mu\text{F}) + 1/(6\mu\text{F}) + \\ 1/(3\mu\text{F}) &= 0.667/\mu\text{F} \end{aligned}$$

$$C_{eq} = 1.5 \mu\text{F}$$

Find Q on each capacitor:
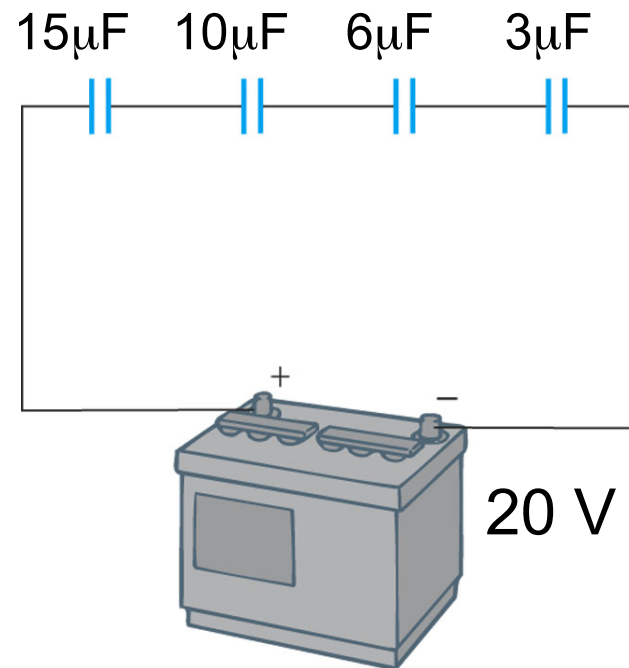
$$\begin{aligned} Q &= C_{eq}\Delta V = \\ (1.5 \times 10^{-6}\text{F})(20\text{V}) &= 30\mu\text{C} \end{aligned}$$



Capacitors in Series

Find the voltage drop across each capacitor:

$$\Delta V_1 = Q/C_1 = 30\mu\text{C}/15\mu\text{F} = 2\text{V}$$


$$\Delta V_2 = Q/C_2 = 30\mu\text{C}/10\mu\text{F} = 3\text{V}$$

$$\Delta V_3 = Q/C_3 = 30\mu\text{C}/6\mu\text{F} = 5\text{V}$$


$$\Delta V_4 = Q/C_4 = 30\mu\text{C}/3\mu\text{F} = 10\text{V}$$

Notice that
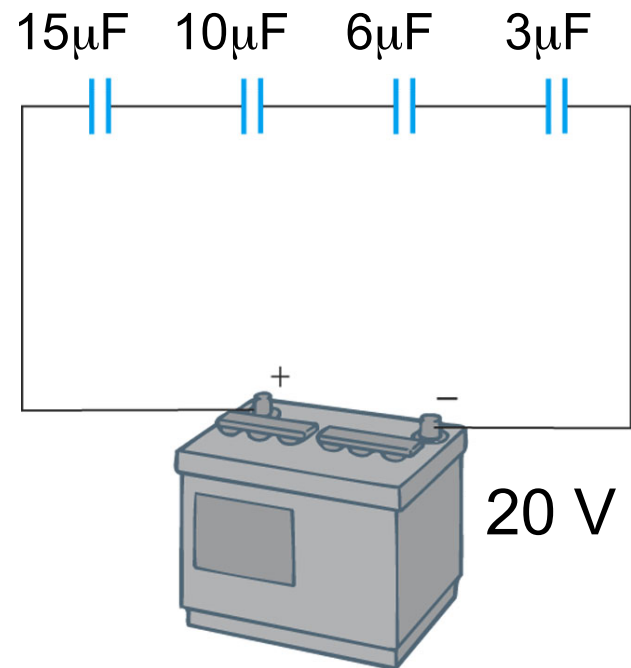
$$\Delta V_1 + \Delta V_2 + \Delta V_3 + \Delta V_4 = \Delta V$$



Capacitors in Parallel AND in SERIES

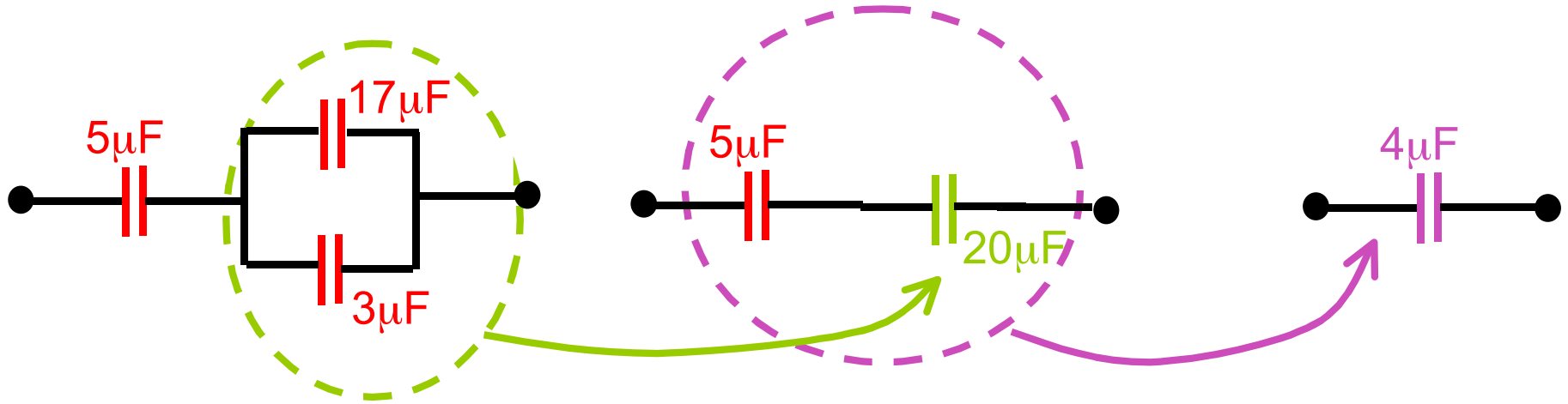


Energy stored in a capacitor


How much work does it take to charge up a capacitor?

Start with neutral plates, transfer a tiny amount of charge, ΔQ : Amount of work you need to do will equal the amount of charge times the potential difference currently across the plates

Energy stored in a capacitor

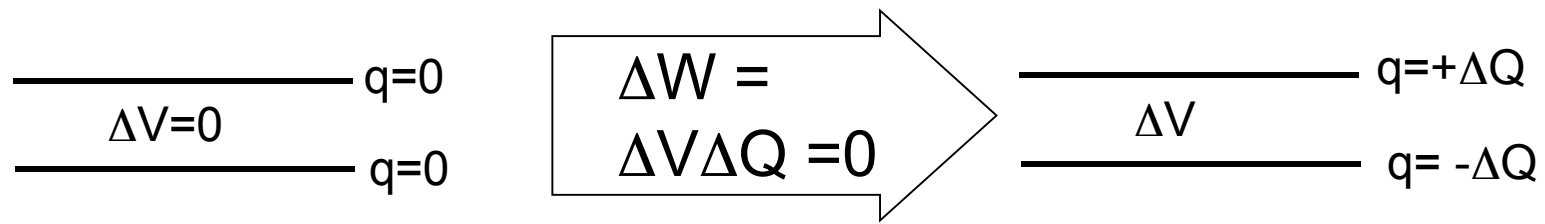


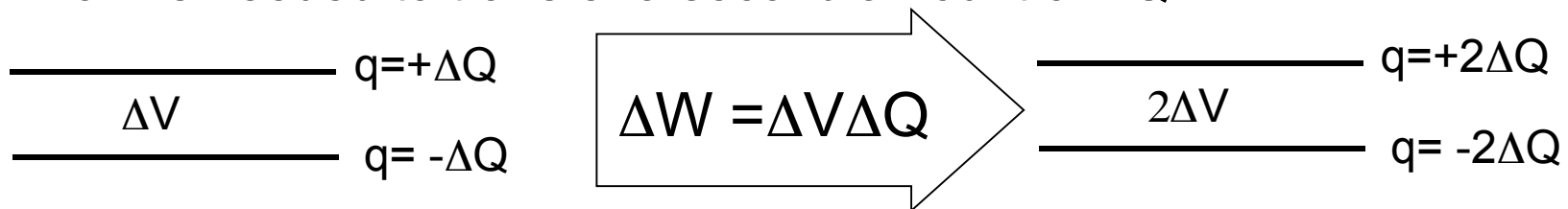Once one ΔQ has been transferred, ΔV has increased, so additional work is needed to transfer a second amount of ΔQ :



To transfer a third ΔQ , you'll need to do work $\Delta W = (2\Delta V)\Delta Q$

Energy stored in a capacitor

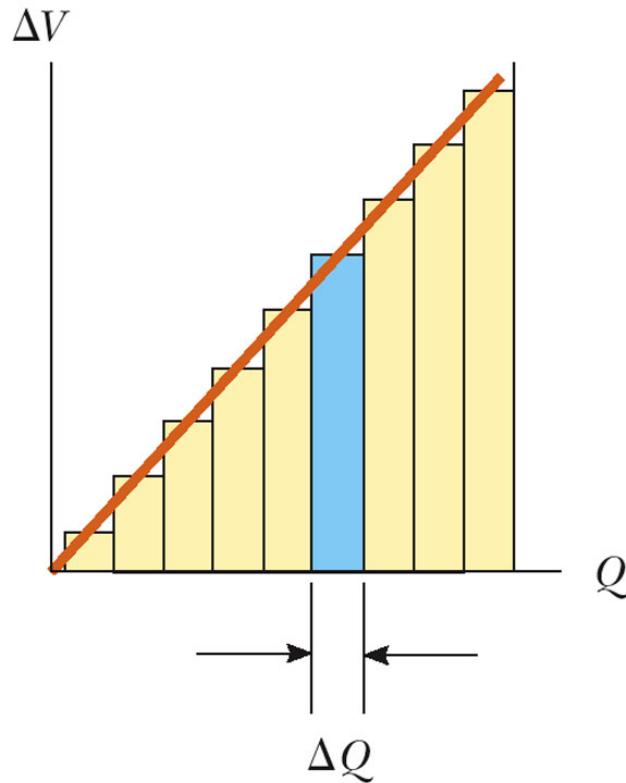

Total work = shaded area

$$W = \int_0^Q \frac{q}{C} dq = \frac{1}{C} \int_0^Q q dq = \frac{1}{C} \frac{Q^2}{2}$$

$$\text{Total Work} = U = \frac{1}{2} (Q \Delta V) = \\ \frac{1}{2} C(\Delta V)^2 = \frac{Q^2}{2C}$$

Energy density

- Energy stored can also be expressed in terms of the energy density (energy per unit volume)

$$u_E = \frac{1}{2} \epsilon_0 E^2$$

Defibrillators

A fully charged defibrillator contains $U = 1.2$ kJ of energy stored in a capacitor with $C = 1.1 \times 10^{-4}$ F. Find the voltage needed to store this amount of energy.

$$U = \frac{1}{2} C (\Delta V)^2$$

$$\Delta V = \sqrt{2 U / C} = \sqrt{(2)(1200\text{J}) / 1.1 \times 10^{-4} \text{ F}} = 4670 \text{ V}$$

In a discharge through a patient, 600 J of electrical energy are delivered in 2.5 ms. What's the average power delivered during this time?


$$\text{Avg. Power} = \text{Energy/time} = 600\text{J}/0.0025\text{sec} = 2.4 \times 10^5 \text{ W}$$

Recap: when d is halved, what happens to the energy stored?

$d \rightarrow d/2$, with battery attached: $\Delta V = \text{same}$; $E = \Delta V/d \rightarrow 2E$; $Q \rightarrow 2Q$; $C \rightarrow 2C$; $U \rightarrow 2U$
 $d \rightarrow d/2$, after battery removed: $Q = \text{same}$; $E = \sigma/\epsilon_0 = \text{same}$; $\Delta V = Ed \rightarrow \Delta V/2$; $C = Q/\Delta V = \frac{\epsilon_0 A}{d} \rightarrow 2C$; $U \rightarrow U/2$.

Dielectrics

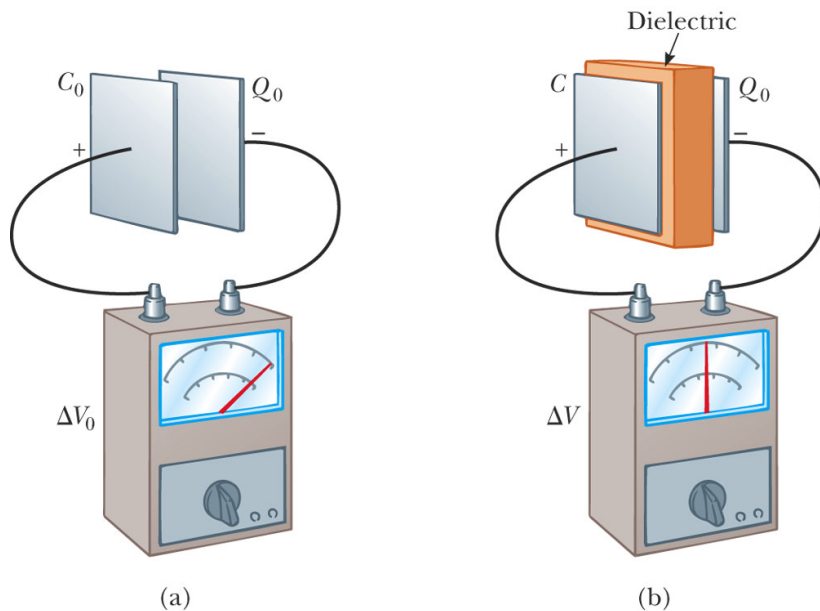Insulators placed in the gap to increase capacitance by a factor κ : ceramic, paper, glass, plastic, water, teflon,...



When you insert a dielectric (no battery attached), the voltage is observed to drop

$$\Delta V = \Delta V_0 / \kappa$$

κ always > 1 ($\kappa=1$ for vacuum)

Q_0 remains the same (charge can't flow anywhere)

$$C = Q / \Delta V = Q / (\Delta V_0 / \kappa) = \kappa Q / \Delta V_0$$

$$\mathbf{C = \kappa C_0}$$

Originally:
 $\Delta V_0, C_0, Q_0$

Dielectrics

TABLE 20.1

Dielectric Constants and Dielectric Strengths of Various Materials at Room Temperature

Material	Dielectric Constant κ	Dielectric Strength (V/m)
Vacuum	1.000 00	—
Air	1.000 59	3×10^6
Bakelite [®]	4.9	24×10^6
Fused quartz	3.78	8×10^6
Pyrex [®] glass	5.6	14×10^6
Polystyrene	2.56	24×10^6
Teflon [®]	2.1	60×10^6
Neoprene rubber	6.7	12×10^6
Nylon	3.4	14×10^6
Paper	3.7	16×10^6
Strontium titanate	233	8×10^6
Water	80	—
Silicone oil	2.5	15×10^6


Dielectrics

$$C = \kappa \epsilon_0 (A/d)$$

For any given d , there's a maximum electric field that can occur inside the dielectric above which conduction will occur.


“Dielectric strength”

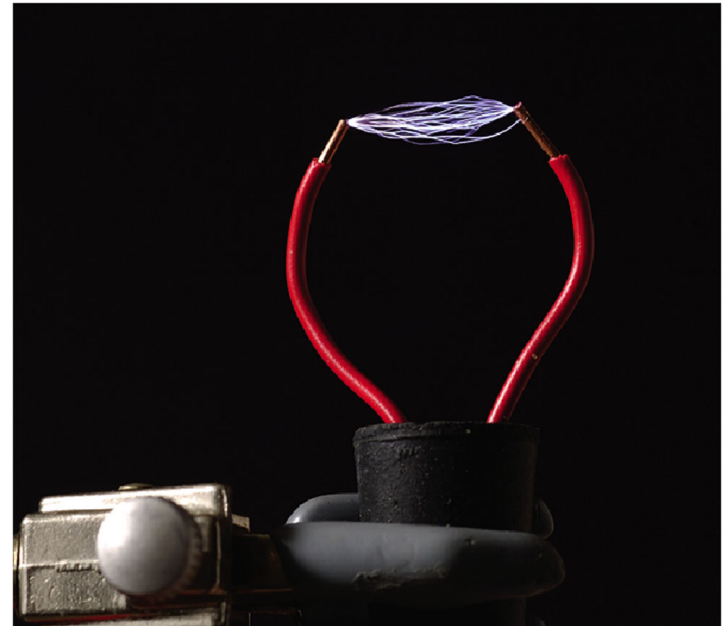For air ($\kappa = 1.00059$),
this is $E = 3 \times 10^6 \text{ V/m}$



Permittivity of a dielectric

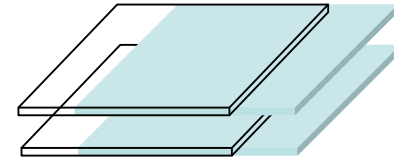Consider a capacitor not connected to a battery: $E_0 = \Delta V_0/d$



Add dielectric $E = \Delta V/d = (\Delta V/\kappa)/d$


$$E = E_0/\kappa$$

For a capac., $E_0 = \sigma/\epsilon_0$

$$E = (\sigma/\epsilon_0)/\kappa = \sigma/\epsilon$$

$$\epsilon = \kappa\epsilon_0$$

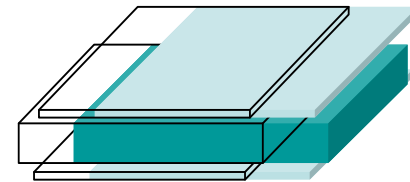Permittivity is increased compared to vacuum



Example:

You have a capacitor with plates of area = 20 cm², separated by a 1mm-thick layer of teflon. Find the capacitance and the maximum voltage & charge that can be placed on the capacitor.

Find κ from Table 20.1: For teflon, $\kappa=2.1$

$$C = \kappa \epsilon_0 (A/d)$$

$$C = 2.1(8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2)(20 \times 10^{-4} \text{ m}^2)/(10^{-3} \text{ m}) = 3.7 \times 10^{-11} \text{ F} \\ = 37 \text{ pF}$$


Diel. Strength is also found in Table 20.1: $E_{\text{max}} = 6 \times 10^7 \text{ V/m}$

$$\Delta V_{\text{max}} = E_{\text{max}} d = (6 \times 10^7 \text{ V/m})(0.001 \text{ m}) = 6 \times 10^4 \text{ V}$$

$$Q_{\text{max}} = C \Delta V_{\text{max}} = (37 \times 10^{-12} \text{ F})(6 \times 10^4 \text{ V}) = 2.2 \times 10^6 \text{ C}$$


Molecular basis for dielectric constant

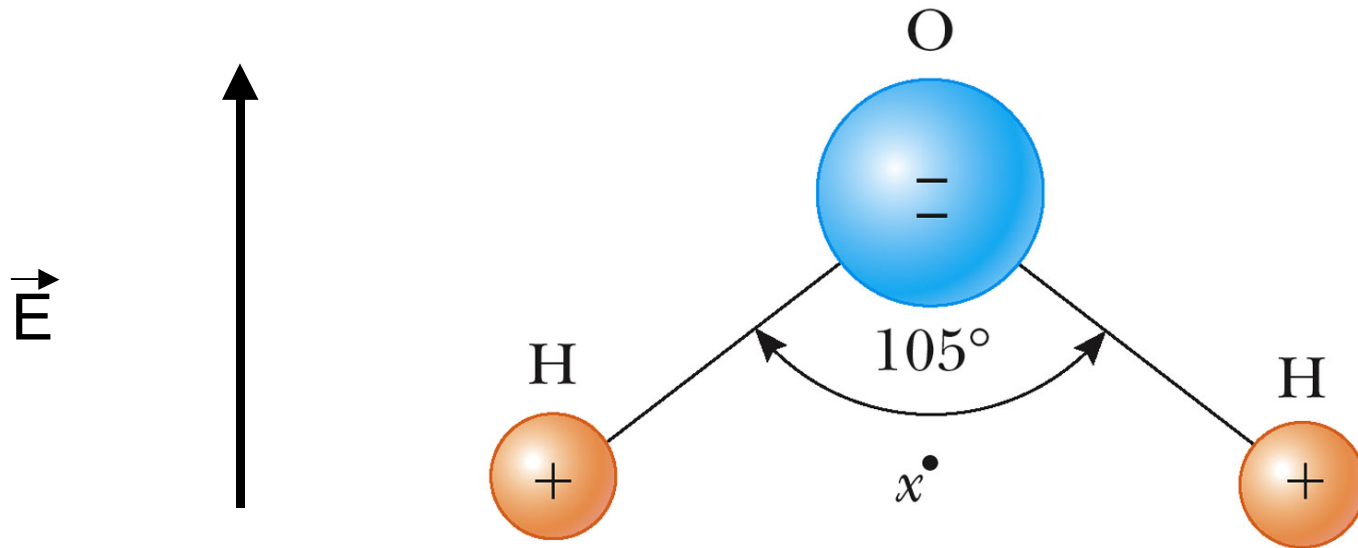Relies on POLARIZATION: In some molecules, there's a separation between average positions of + and - charges



Molecular basis for dielectric constant

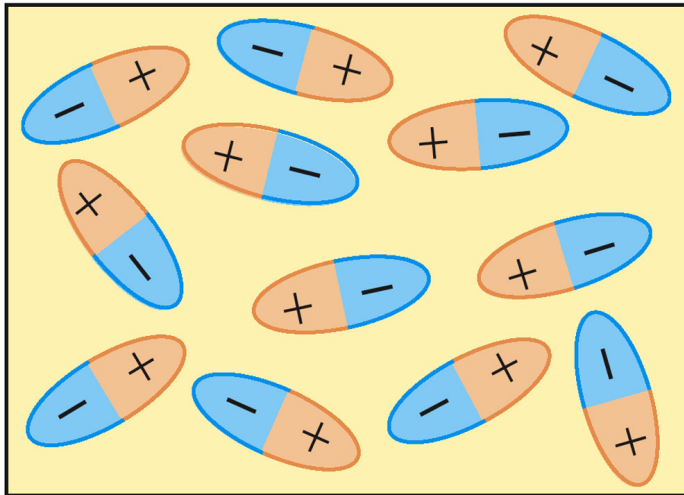
No external E-field: Molecules are randomly oriented




Molecular basis for dielectric constant

No external E-field: Molecules are randomly oriented

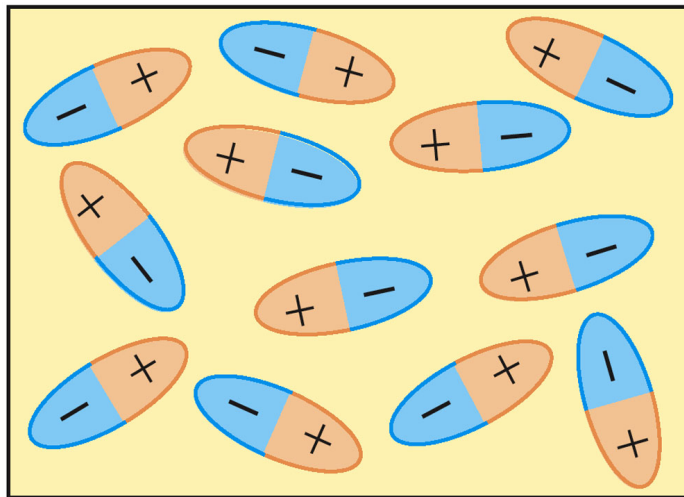Apply external E-field: molecules orient themselves to partially align with the field



© 2006 Brooks/Cole - Thomson

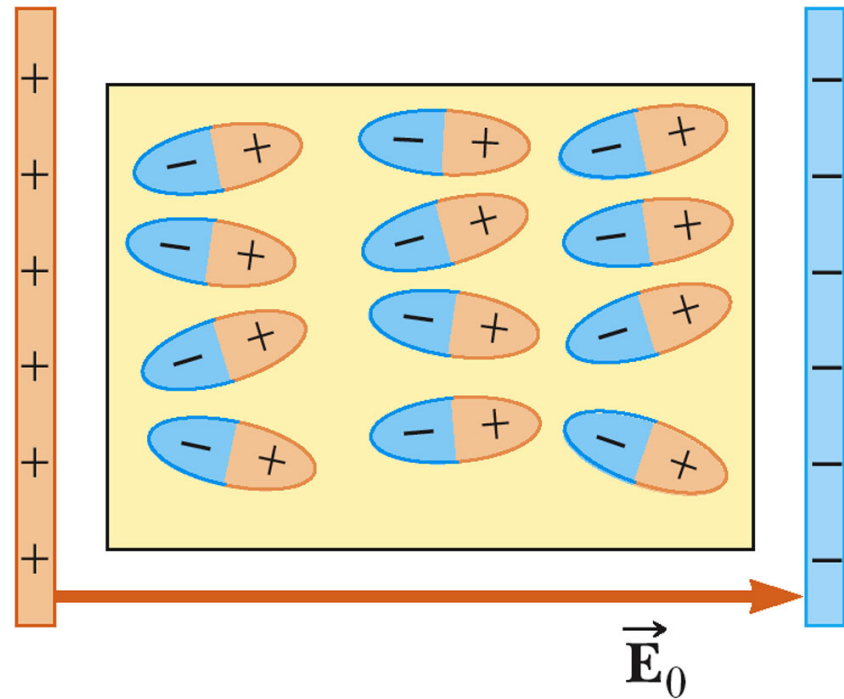


© 2006 Brooks/Cole - Thomson


Molecular basis for dielectric constant

No external E-field: Molecules are randomly oriented

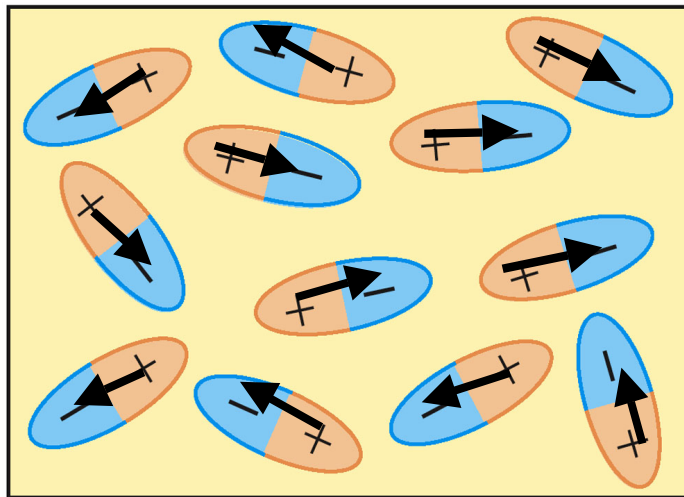Apply external E-field: molecules orient themselves to partially align with the field



© 2006 Brooks/Cole - Thomson

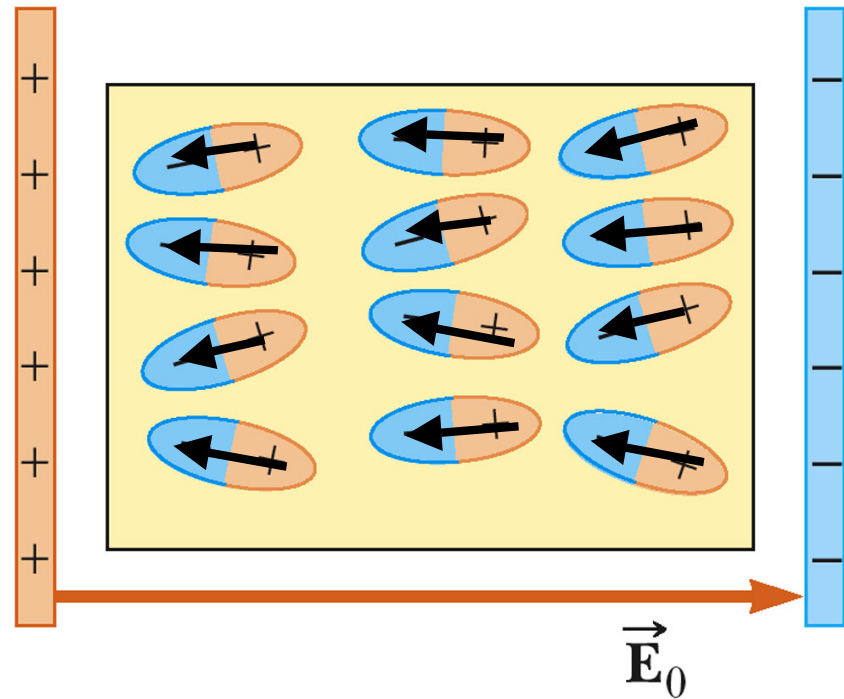

© 2006 Brooks/Cole - Thomson


Molecular basis for dielectric constant

Dielectric produces its own E-field (E_{induced})

$$E_{\text{net}} = E_0 - E_{\text{induced}}$$

Negative poles of molecules attract more +Q onto positive plate, etc.... so capacitor can hold more charge

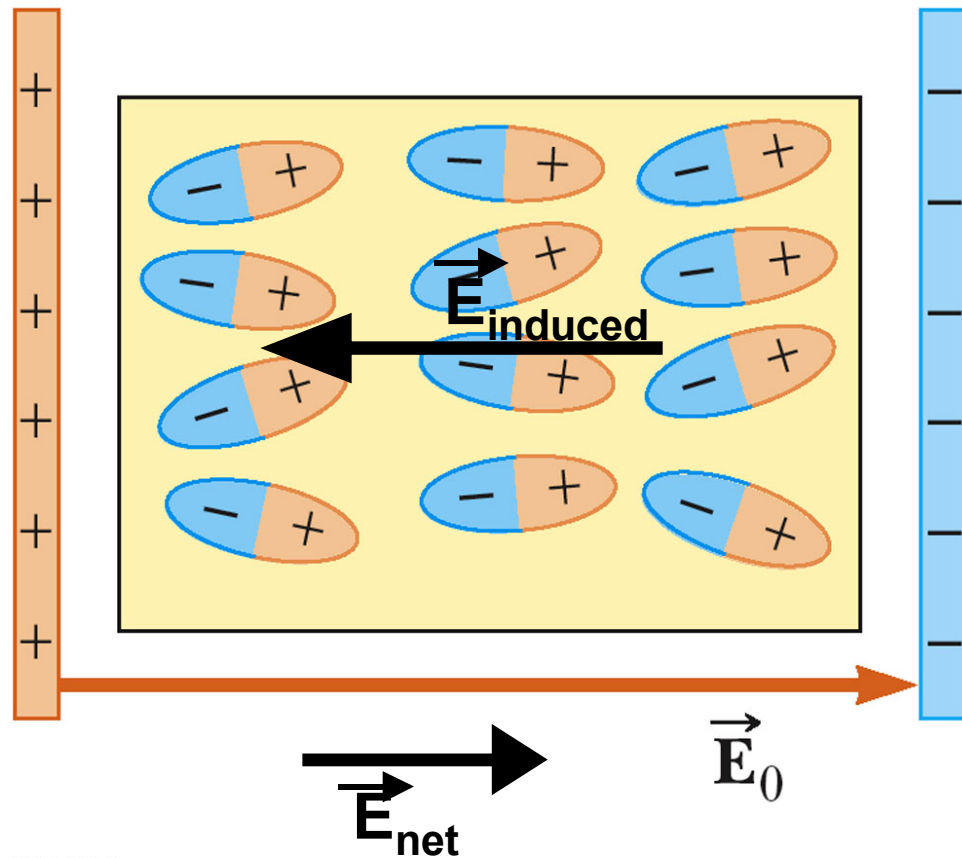(and if a battery's attached, more charge CAN be added)



Dielectric Example 1

Example: You have a capacitor with capacitance C_0 , charge it up via a battery so the charge is $\pm Q_0$, with ΔV_0 across the plates and E_0 inside. Initially $U_0 = 1/2 C_0 (\Delta V_0)^2 = Q_0^2 / 2 C_0$. Then, disconnect the battery, and then insert a dielectric with dielectric constant κ .

What are C_f , U_f , Q_f , E_f , and ΔV_f ?

Isolated system, so $Q_f = Q_0$.

$$\Delta V_f = \Delta V_0 / \kappa$$

$$E_f = E_0 / \kappa$$

$$C_f = Q_f / \Delta V_f = \kappa C_0$$

$$U_f = 1/2 C_f (\Delta V_f)^2 = U_0 / \kappa$$

Dielectric Example 2

Example: You have a capacitor with capacitance C_0 , charge it up via a battery so the charge is $\pm Q_0$, with ΔV_0 across the plates and E_0 inside. Initially $U_0 = 1/2 C_0 (\Delta V_0)^2 = Q_0^2 / 2 C_0$. Then, while keeping the connection to the battery, insert a dielectric with dielectric constant κ .

What are C_f , U_f , Q_f , E_f , and ΔV_f ?

Battery maintains a constant potential diff.: $\Delta V_f = \Delta V_0$

$$E_f = E_0 \quad (E_0 = \sigma_0 / \epsilon_0; E_f = \sigma_f / \epsilon = \kappa \sigma_0 / \kappa \epsilon_0)$$

$$Q_f = \kappa Q_0.$$

$$C_f = Q_f / \Delta V_f = \kappa C_0$$

$$U_f = 1/2 C_f (\Delta V_f)^2 = \kappa U_0$$


Capacitance of Biological Membranes

Neurons:

Outside: Na^+ , Cl^-


Inside: K^+ , neg.
organics

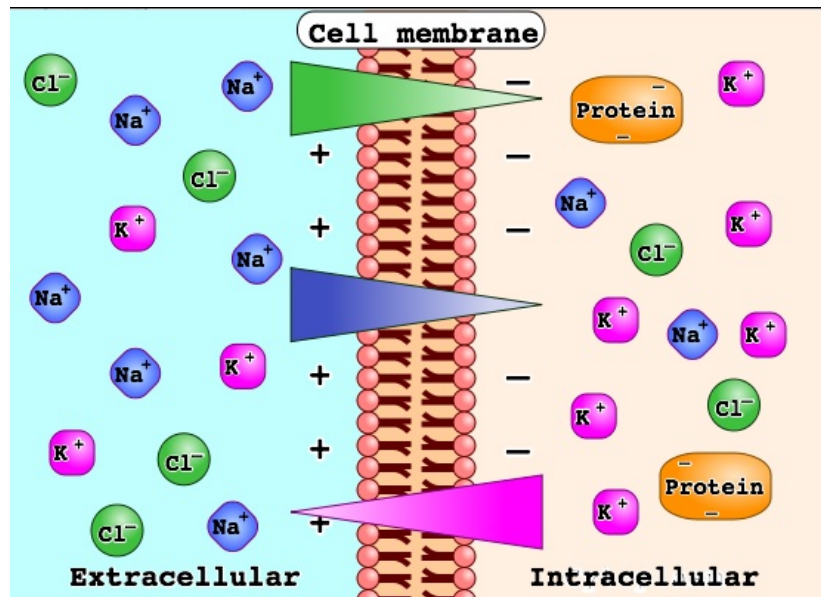No electric pulse:
equal amounts of
 Na^+ and K^+ on
either side



Capacitance of Biological Membranes

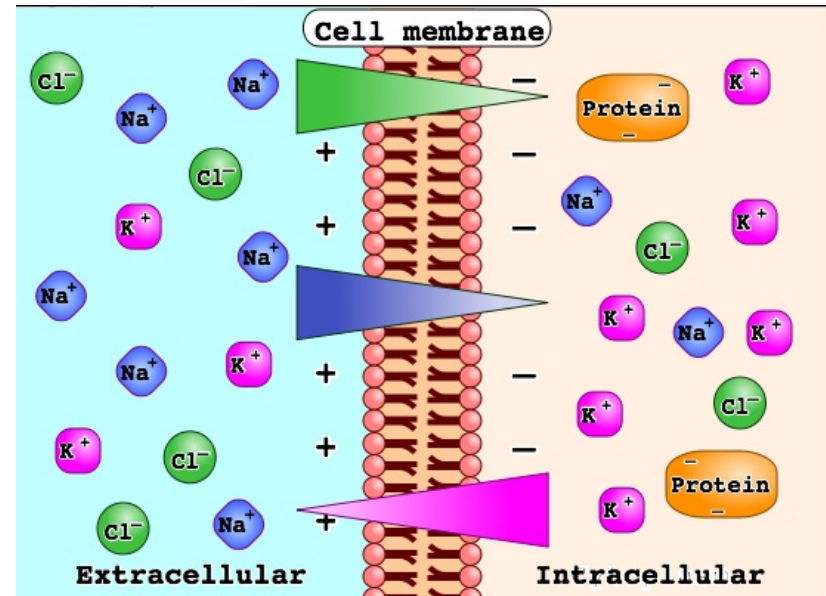Electric pulse: K^+ ions leave the semi-permeable membrane and migrate outside (for every 3 K^+ 's that leave, 2 Na^+ 's enter). Neg. proteins are too big to go anywhere.



Creates net positive charge outside, net negative inside: ΔV can be as high as $\sim 0.05 - 0.10V$

Capacitance of Biological Membranes

Typical d is a few nm.

Typical Capacitance is ~ 2 μF per square cm of membrane.

Estimate κ , assuming $d = 3\text{nm}$:

$$C = \epsilon_0 \kappa (A/d) \quad \rightarrow \quad C/A = \epsilon_0 \kappa / d$$

$$\kappa = (C/A)d / \epsilon_0 = (2 \times 10^{-6} \text{ F/cm}^2)(10^4 \text{ cm}^2/\text{m}^2)(3 \times 10^{-9} \text{ m}) / (8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2) = 6.8$$

Compare to the teflon ($\kappa=2.1$) capacitor, where C/A was $37\text{pF}/20\text{cm}^2 = 1.9\text{pF}/\text{cm}^2$. Here we have much smaller d (and higher κ).

