

CHAPTER 21

1. $I = 30.0 \mu\text{A} = 3 \cdot 10^{-5} \text{A}$
 $\Delta t = 40 \text{s}$

$$\Delta Q = I \Delta t = 1.2 \cdot 10^{-3} \text{C}$$

$$\text{Number of electrons} = \frac{\Delta Q}{e} = \underline{7.5 \cdot 10^{15}}$$

5. $A = 4 \cdot 10^{-6} \text{m}^2$

$$I = 5 \text{A}$$

$$\rho = 2.7 \text{g/cm}^3 = 2.7 \cdot 10^6 \text{g/m}^3$$

$$\text{Molar mass} = 24 \text{g/mol}$$

$$\text{Mass of one atom} = \frac{\text{Molar mass}}{N_A}$$

$$\text{Number density of atoms} = \frac{\rho}{\text{mass of one atom}} =$$

$$= \frac{\rho}{\text{Molar mass}} \cdot N_A = 6.02 \cdot 10^{28} \text{m}^{-3}$$

One electron per atom, so

$$n = 6.02 \cdot 10^{28} \text{m}^{-3}$$

$$I = n e v_d A$$

$$v_d = \frac{I}{n e A} = \underline{1.3 \cdot 10^{-4} \text{ m/s}}$$

6. $R = 240 \Omega$

$$\Delta V = 120 \text{ V}$$

$$I = \frac{\Delta V}{R} = \underline{0.5 \text{ A}}$$

7. $\Delta V = 0.9 \text{ V}$

$$l = 1.5 \text{ m}$$

$$A = 0.6 \text{ mm}^2 = 0.6 \cdot 10^{-6} \text{ m}^2$$

$$\rho = 5.6 \cdot 10^{-8} \Omega \cdot \text{m} \text{ (Table 21.1, page 689)}$$

$$R = \frac{\rho l}{A} = 0.14 \Omega$$

$$I = \frac{\Delta V}{R} = \underline{6.43 \text{ A}}$$

8. $m = 1 \text{ g} = 10^{-3} \text{ kg}$

$$R = 0.5 \Omega$$

$$\text{density} = 8.92 \cdot 10^3 \text{ kg/m}^3$$

$$\rho = 1.7 \cdot 10^{-8} \Omega \cdot \text{m}$$

$$m = \text{density} \cdot \text{volume} = \text{density} \cdot A \cdot l \quad (1)$$

$$R = \frac{\rho l}{A} \quad (2)$$

a) multiply (1) and (2):

$$mR = \text{density} \cdot A \cdot l \cdot \frac{\rho l}{A} = \text{density} \cdot \rho l^2$$

$$l = \sqrt{\frac{mR}{\text{density} \cdot \rho}} = \underline{1.82 \text{ m}}$$

(B) From (1):

$$A = \frac{m}{\text{density} \cdot l} = 6.17 \cdot 10^{-8} \text{ m}^2 = \pi r^2$$

$$r = 1.4 \cdot 10^{-4} \text{ m}$$

$$\text{diameter} = 2r = \underline{2.8 \cdot 10^{-4} \text{ m}}$$

9 (a) $\rho_0 = 2.82 \cdot 10^{-8} \Omega \cdot \text{m}$ at $T_0 = 20^\circ \text{C}$

$$T = 50^\circ \text{C}, \quad \alpha = 3.9 \cdot 10^{-3} (\text{C})^{-1}$$

$$\rho = \rho_0 (1 + \alpha(T - T_0)) = \underline{3.15 \cdot 10^{-8} \Omega \cdot \text{m}}$$

(B) $E = 0.2 \text{ V/m}$

$$J = \frac{E}{\rho} = \underline{6.35 \cdot 10^6 \text{ A/m}^2}$$

(c) $d = 0.1 \text{ mm}$

$$r = \frac{d}{2} = 0.05 \text{ mm} = 5 \cdot 10^{-5} \text{ m}$$

$$A = \pi r^2 = 7.85 \cdot 10^{-9} \text{ m}^2$$

$$I = JA = \underline{49.9 \cdot 10^{-3} \text{ A}}$$

(d) density = $2.7 \cdot 10^6 \text{ g/m}^3$

$$\text{Molar mass} = 27 \text{ g/mol}$$

$$\text{Mass of one atom} = \frac{\text{Molar mass}}{N_A}$$

$$\begin{aligned} \text{Number density of atoms} &= \frac{\text{density}}{\text{mass of one atom}} \\ &= \frac{\text{density}}{\text{molar mass}} \cdot N_A = 6.02 \cdot 10^{28} \text{ m}^{-3} \end{aligned}$$

One electron per atom, so

$$n = 6.02 \cdot 10^{28} \text{ m}^{-3}$$

$$J = neV_d$$

$$V_d = \frac{J}{ne} = \underline{6.59 \cdot 10^{-3} \text{ m/s}}$$

(e) $l = 2 \text{ m}$

$$\Delta V = E \cdot l = \underline{0.4 \text{ V}}$$

LO $T_1 = 58^\circ\text{C}$ (Death Valley)

$$I_1 = 1\text{A}$$

$$T_2 = -88^\circ\text{C}$$
 (Antarctica)

$$\alpha = 3.9 \cdot 10^{-3} (\text{C})^{-1}$$

$$R_1 = R_0(1 + \alpha(T_1 - T_0))$$

$$T_0 = 20^\circ\text{C}$$

$$R_2 = R_0(1 + \alpha(T_2 - T_0))$$

$$\Delta V_1 = \Delta V_2 \quad \text{so}$$

$$I_1 R_1 = I_2 R_2$$

$$I_2 = I_1 \frac{R_1}{R_2} = I_1 \frac{R_0(1 + \alpha(T_1 - T_0))}{R_0(1 + \alpha(T_2 - T_0))} =$$

$$= 1\text{A} \cdot \frac{1.15}{0.58} = \underline{\underline{2\text{A}}}$$

12 (a) Charge carrier density is a property of the material, so it does not change.

(b) $J = \frac{I}{A}$, A does not change, I doubles, so J doubles.

(c) $J = ne v_d$

$v_d = \frac{J}{ne}$ doubles

(d) $\rho = \frac{m_e}{ne^2 \tau}$

$\tau = \frac{m_e}{ne^2 \rho}$ does not change.

16 $P = 600W$
 $\Delta V = 120V$

$P = \Delta V \cdot I$

$I = \frac{P}{\Delta V} = \underline{5A}$

$R = \frac{\Delta V}{I} = \underline{24\Omega}$

17 $\Delta V' = 140V$
 $\Delta V = 120V$

$R' = R$

$P = \frac{(\Delta V)^2}{R}$

$\frac{P'}{P} = \frac{(\Delta V')^2 / R}{(\Delta V)^2 / R} = \left(\frac{\Delta V'}{\Delta V}\right)^2 = 1.36$

$P' - P = 0.36P$

$$\frac{P' - P}{P} \cdot 100\% = \underline{36\%}$$

18. $P_1 = 11W$
 $P_2 = 40W$
 $t = 100h$

$$\text{cost} = \$ 0.08 / \text{kW}\cdot\text{h} = \$ 8 \cdot 10^{-5} / \text{Wh}$$

$$\text{energy difference} = (P_2 - P_1) \cdot t = 29 \cdot 10^2 \text{Wh}$$

$$\text{money saved} = 29 \cdot 10^2 \text{Wh} \cdot \$ 8 \cdot 10^{-5} / \text{Wh} =$$
$$= \underline{\$ 0.232}$$

19. $\Delta V = 120V$
 $T_i = 20^\circ C$
 $I_i = 1.8A$
 $I_f = 1.53A$

(a) $P_f = \Delta V \cdot I_f = 184W$

(b) $R_i = \frac{\Delta V}{I_i}$

also $R_i = R_0 [1 + \alpha (T_i - T_0)] = R_0$

since $T_i = T_0 = 20^\circ C$

$$R_f = \frac{\Delta V}{I_f} = R_0(1 + \alpha(T_f - T_0)) = \frac{\Delta V}{I_i}(1 + \alpha(T_f - T_0))$$

$$1 + \alpha(T_f - T_0) = \frac{I_i}{I_f} = 1.18$$

$$\alpha(T_f - T_0) = 0.18$$

$$T_f - T_0 = \frac{0.18}{\alpha} = \frac{0.18}{0.4 \cdot 10^{-3} (\text{C}^{-1})} = 450 \text{ } ^\circ\text{C}$$

$$T_f = T_0 + 450 \text{ } ^\circ\text{C} = \underline{461 \text{ } ^\circ\text{C}}$$

21 cost = \$0.12/kWh = \$0.12 · 10⁻³/Wh

(a) P = 40W

t = 2 weeks = 2 · 7 · 24h = 336h

money = cost · Pt = \$1.61

(b) P = 970W

t = 3 min = 0.05h

money = cost · Pt = \$5.82 · 10⁻³

(c) P = 5200W

t = 40 min = 0.67h

money = cost · Pt = \$0.916

$$\underline{\underline{23}} \quad \Delta V = 12 \text{ V}$$

$$E = 2 \cdot 10^7 \text{ J}$$

$$\underline{\underline{(a)}} \quad P = 8 \text{ kW} = 8 \cdot 10^3 \text{ W}$$

$$P = \Delta V \cdot I$$

$$I = \frac{P}{\Delta V} = \underline{\underline{667 \text{ A}}}$$

$$\underline{\underline{(b)}} \quad v = 20 \text{ m/s}$$

$$t = \frac{E}{P} = 2500 \text{ s}$$

$$d = vt = 5 \cdot 10^4 \text{ m} = \underline{\underline{50 \text{ km}}}$$

$$\underline{\underline{49}} \quad P_1 = 25 \text{ W}$$

$$P_2 = 100 \text{ W}$$

$$\Delta V = 120 \text{ V}$$

$$\underline{\underline{(a)}} \quad P = \frac{(\Delta V)^2}{R}$$

$$R = \frac{(\Delta V)^2}{P}$$

$$\underline{\underline{R_1 = 576 \Omega}}$$

$$\underline{\underline{R_2 = 144 \Omega}}$$

$$\underline{\underline{(b)}} \quad P_1 = \Delta V \cdot I_1$$

$$I_1 = \frac{P_1}{\Delta V} = 0.21 \text{ A} = \frac{Q}{\Delta t}$$

$$\Delta t = \frac{Q}{0.21 A} = \frac{1 C}{0.21 A} = \underline{4.8 S}$$

The charge does not change, its potential energy does.

$$\underline{(c)} \quad \Delta t = \frac{1 J}{P_1} = \underline{0.04 S}$$

The energy enters as the potential energy of the charges, exits as heat and light.

$$\underline{(d)} \quad \text{cost} = \$0.07 / \text{kWh} = \$0.07 \cdot 10^{-3} / \text{Wh} =$$

$$= \$0.07 \cdot 10^{-3} / \text{Wh} \cdot 3600 \text{ s} = \underline{\$1.94 \cdot 10^{-8} / \text{J}}$$

The company sells energy with the cost of $\$1.94 \cdot 10^{-8}$ per Joule.

$$t = 30 \text{ days} = 30 \cdot 24 \cdot 3600 \text{ s} = 2.6 \cdot 10^6 \text{ s}$$

$$\text{money} = \text{cost} \cdot Pt = \underline{\$1.26}$$

53 $P_1 = 1500 \text{ W}$
 $P_2 = 750 \text{ W}$
 $P_3 = 1000 \text{ W}$
 $\Delta V = 120 \text{ V}$

(a) $P = \Delta V \cdot I$
 $I = \frac{P}{\Delta V}$

$$I_1 = \underline{12.5 \text{ A}}$$

$$I_2 = \underline{6.25 \text{ A}}$$

$$I_3 = \underline{8.33 \text{ A}}$$

(b) $I_1 + I_2 + I_3 = 27.1 \text{ A} > 25 \text{ A}$

so it is not sufficient.

55 Batteries in series:

$$\Delta V = 4 \cdot 1.5 \text{ V} = 6 \text{ V}$$

$$Q = 240 \text{ C}$$

$$R = 200 \Omega$$

$$I = \frac{\Delta V}{R} = 0.03 \text{ A}$$

$$\Delta t = \frac{Q}{I} = \underline{8000 \text{ s}}$$

26 Batteries in series:

$$\Delta V = 2 \cdot 1.5 \text{ V} = 3 \text{ V}$$

$$R_1 = 0.255 \Omega$$

$$R_2 = 0.153 \Omega$$

$$I = 600 \text{ mA} = 0.6 \text{ A}$$

$$(a) \underline{R_{\text{total}}} = \frac{\Delta V}{I} = 5 \Omega = R_1 + R_2 + R_{\text{lamp}}$$

$$R_{\text{lamp}} = \underline{4.592 \Omega}$$


$$(b) P = I \cdot R^2$$

$$P_{\text{internal}} = I^2 (R_1 + R_2)$$

$$P_{\text{total}} = I^2 R_{\text{total}}$$

$$\frac{P_{\text{internal}}}{P_{\text{total}}} = \frac{I^2 (R_1 + R_2)}{I^2 R_{\text{total}}} = \left(\frac{R_1 + R_2}{R_{\text{total}}} \right) = \underline{0.0816}$$

27

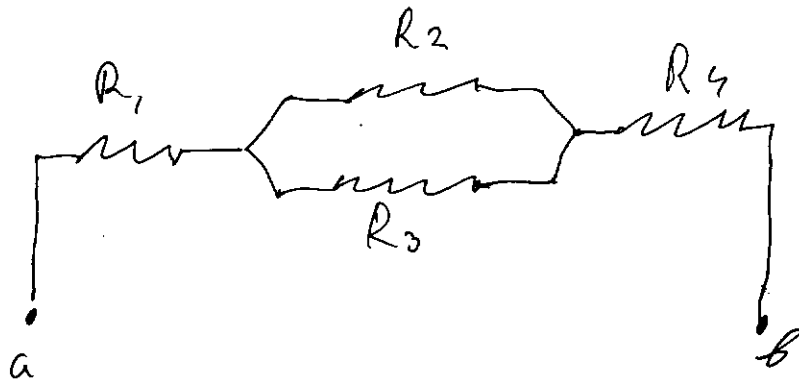

$$R_1 = 4 \Omega$$

$$R_2 = 7 \Omega$$

$$R_3 = 10 \Omega$$

$$R_4 = 9 \Omega$$

(a) 2 and 3 in parallel:

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{23} = \frac{R_2 \cdot R_3}{R_2 + R_3} = 4.12 \Omega$$

1, 23, 4 in series

$$R_{\text{total}} = R_1 + R_{23} + R_4 = \underline{17.12 \Omega}$$

(b) $\Delta V = 34 \text{ V}$

$$I_{\text{total}} = \frac{\Delta V}{R_{\text{total}}} = 2 \text{ A}$$

1, 23, 4 in series so


$$\underline{I_1 = I_4 = I_{23} = I_{\text{total}} = 2 \text{ A}}$$

$$\Delta V_{23} = I_{23} \cdot R_{23} = 8.18 \text{ V} = \Delta V_2 = \Delta V_3$$

$$I_2 = \frac{\Delta V_2}{R_2} = \underline{1.17 \text{ A}}$$

$$I_3 = \frac{\Delta V_3}{R_3} = \underline{0.818 \text{ A}}$$

30

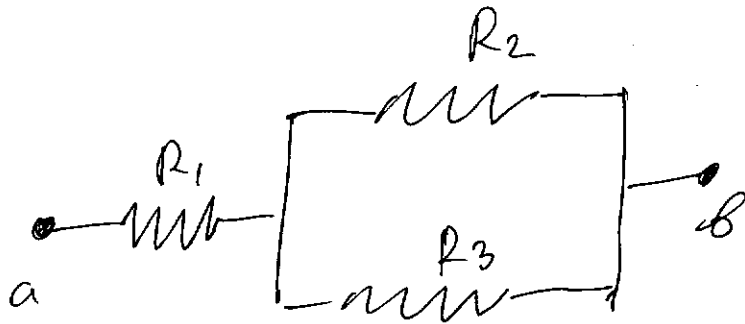

$$R = R_1 = R_2 = R_3 = 100 \Omega$$

$$R_{23} = \frac{R_2 \cdot R_3}{R_2 + R_3} = \frac{R^2}{2R} = \frac{R}{2} \quad (\text{parallel})$$

$$R_{\text{total}} = R_1 + R_{23} = \frac{3R}{2} \quad (\text{series})$$

$$\bar{I}_{\text{total}} = \frac{\Delta V}{R_{\text{total}}} = \frac{2}{3} \frac{\Delta V}{R} = \bar{I}_1 = \bar{I}_{23}$$

$$\Delta V_{23} = \bar{I}_{23} \cdot R_{23} = \frac{2}{3} \Delta V = \Delta V_2 = \Delta V_3$$

$$\bar{I}_2 = \frac{\Delta V_2}{R_2} = \frac{1}{3} \frac{\Delta V}{R}$$

$$\bar{I}_3 = \frac{\Delta V_3}{R_3} = \frac{1}{3} \frac{\Delta V}{R}$$

$$P_1 = \bar{I}_1^2 \cdot R_1 = \frac{4}{9} \frac{(\Delta V)^2}{R}$$

$$P_2 = \bar{I}_2^2 \cdot R_2 = \frac{1}{9} \frac{(\Delta V)^2}{R}$$

$$P_3 = \bar{I}_3^2 \cdot R_3 = \frac{1}{9} \frac{(\Delta V)^2}{R}$$

Cal Biggest power is delivered to R_1 which cannot exceed 25W so

$$25\text{W} = \frac{4}{9} \frac{(\Delta V_{\max})^2}{R}$$


$$\Delta V_{\max} = \underline{75\text{V}}$$

(B) $\Delta V = \Delta V_{\max}$

$$P_1 = \underline{25\text{W}}$$

$$P_2 = P_3 = \frac{1}{9} \frac{(\Delta V)^2}{R} = \frac{P_1}{4} = \underline{6.25\text{W}}$$
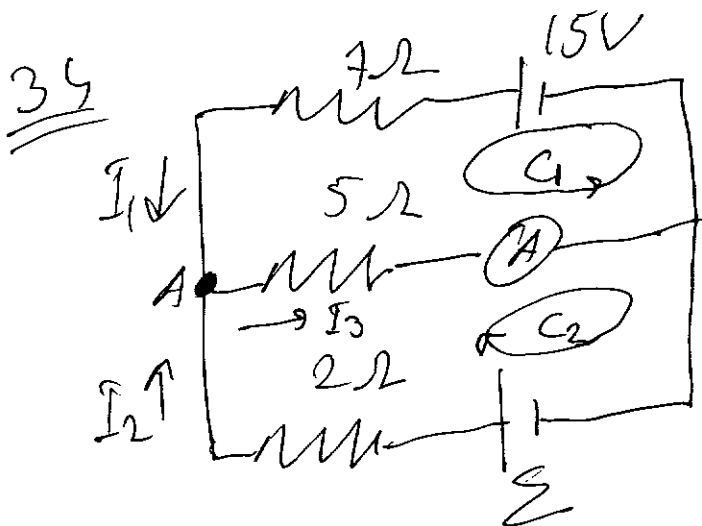
$$P_{\text{total}} = P_1 + P_2 + P_3 = \underline{37.5\text{W}}$$



$$I_3 = 2\text{A}$$

consider loop C_1 :

$$15\text{V} - 7\Omega \cdot I_1 - 5\Omega \cdot I_2 = 0$$

$$15\text{V} - 7\Omega \cdot I_1 - 10\text{V} = 0$$

$$7 \Omega \cdot I_1 = 5V$$

$$\underline{I_1 \approx 0,714 A}$$

consider junction A:

$$I_1 + I_2 = I_3$$

$$\underline{I_2 = I_3 - I_1 \approx 1,286 A}$$

consider loop C₂

$$\Sigma - I_2 \cdot 2 \Omega - I_3 \cdot 5 \Omega = 0$$

$$\underline{\Sigma = I_2 \cdot 2 \Omega + I_3 \cdot 5 \Omega = 12,57V}$$

$$\underline{41} \quad R = 1 M\Omega = 10^6 \Omega$$

$$C = 5 \mu F = 5 \cdot 10^{-6} F$$

$$\Sigma = 30V$$

$$\underline{(a)} \quad \tau = RC = \underline{5s}$$

$$\underline{(b)} \quad Q = C\Sigma = \underline{1,5 \cdot 10^{-4} C}$$

$$\underline{(c)} \quad I(t) = \frac{\Sigma}{R} e^{-t/\tau} = \frac{30}{10^6} A e^{-\frac{10s}{5s}} = \underline{4,06 \cdot 10^{-6} A}$$

$$\underline{42} \quad C = 2 \text{ nF} = 2 \cdot 10^{-9} \text{ F}$$

$$Q_0 = 5.1 \mu\text{C} = 5.1 \cdot 10^{-6} \text{ C}$$

$$R = 1.3 \text{ k}\Omega = 1.3 \cdot 10^3 \Omega$$

$$\underline{(a)} \quad t = 9 \mu\text{s} = 9 \cdot 10^{-6} \text{ s}$$

$$\tau = RC = 2.6 \cdot 10^{-6} \text{ s}$$

$$I(t) = -I_0 e^{-t/\tau} = -\frac{Q_0}{RC}$$

$$I_0 = \frac{\Delta V}{R} = \frac{Q_0/C}{R} = \frac{Q_0}{RC}$$

$$I(t) = -\frac{5.1 \cdot 10^{-6}}{2.6 \cdot 10^{-6}} \text{ A} e^{-\frac{9 \cdot 10^{-6} \text{ s}}{2.6 \cdot 10^{-6} \text{ s}}} = \underline{-6.16 \cdot 10^{-2} \text{ A}}$$


$$\underline{(b)} \quad t = 8 \mu\text{s} = 8 \cdot 10^{-6} \text{ s}$$

$$q(t) = Q_0 e^{-t/\tau} = 5.1 \cdot 10^{-6} \text{ C} e^{-\frac{8 \cdot 10^{-6} \text{ s}}{2.6 \cdot 10^{-6} \text{ s}}} = \underline{2.35 \cdot 10^{-7} \text{ C}}$$

$$\underline{(c)} \quad I_{\text{max}} = I_0 = \frac{Q_0}{RC} = \underline{1.96 \text{ A}}$$

since the current decreases with time,

43

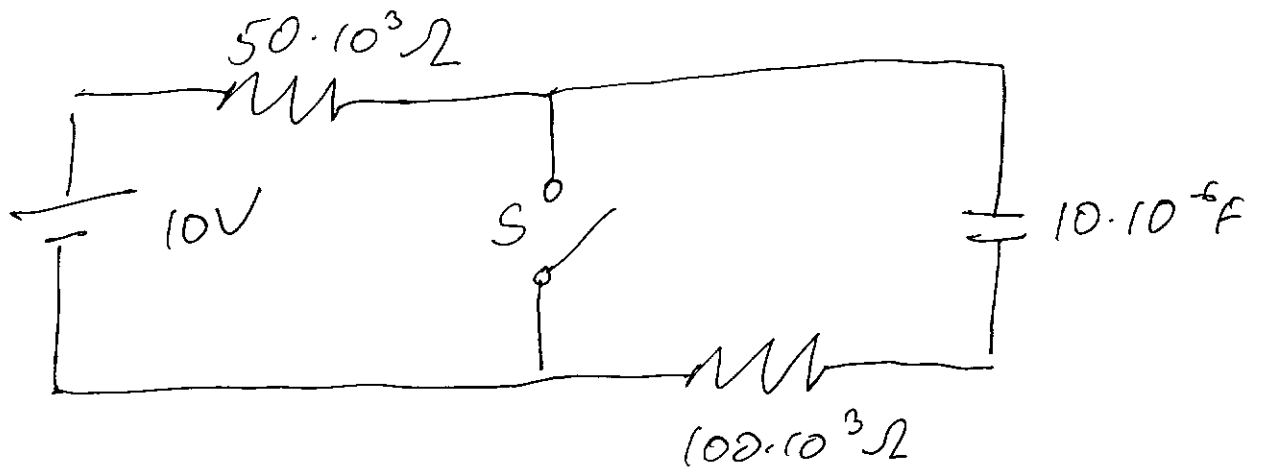


(a) Before the switch is closed

$$R = R_1 + R_2 = 150 \cdot 10^3 \Omega$$

$$\tau = RC = \underline{1.5 \text{ s}}$$

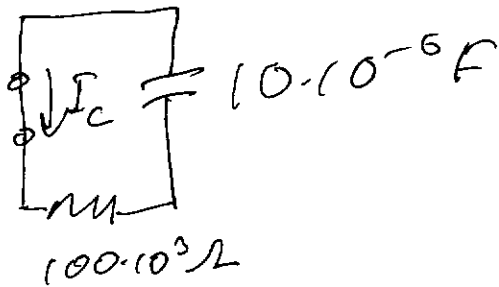(b) After the switch is closed the capacitor discharges through the circuit



so $\tau = R_2 C = \underline{1 \text{ s}}$

(c) Before the switch is closed the capacitor has charge

$$Q_0 = \Delta V \cdot C$$


so as the capacitor begins to discharge

$$I_c(t) = I_0 e^{-t/\tau}$$

$$\text{where } I_0 = \frac{Q_0}{R_2 C} = \frac{\Delta V \epsilon}{R_2 \epsilon} = 10^{-9} \text{ A}$$

$$\tau = R_2 C = 1 \text{ s}$$

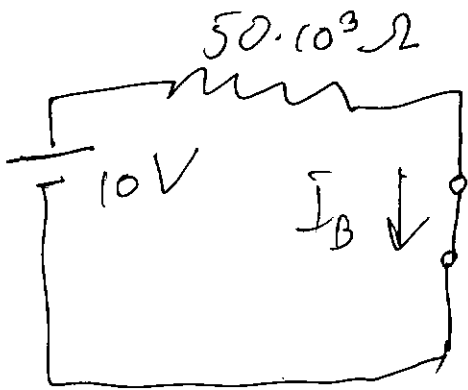but there is also another current through the switch from the other part of the circuit:



$$I_B = \frac{\Delta V}{R_1} = 2 \cdot 10^{-9} \text{ A}$$

so the total current is

$$I(t) = I_B + I_c(t) = \underline{2 \cdot 10^{-9} \text{ A} + 1 \cdot 10^{-9} \text{ A} \cdot e^{-t/1 \text{ s}}}$$

46

$$C = 10 \mu\text{F} = 10^{-5} \text{F}$$

$$\Delta V_0 = 10 \text{V}$$

$$\Delta V(3.5 \text{s}) = 4 \text{V}$$

$$\Delta V(t) = \Delta V_0 (1 - e^{-t/\tau})$$

$$4 \text{V} = 10 \text{V} (1 - e^{-3.5/\tau})$$

$$1 - e^{-3.5/\tau} = 0.4$$

$$e^{-3.5/\tau} = 0.6$$

$$\frac{3.5}{\tau} = 0.511$$

$$\tau = 5.87 \text{s} = RC$$

$$R = \underline{5.87 \cdot 10^5 \Omega}$$

47

$$J = 6 \cdot 10^{-13} \text{A/m}^2$$

$$E = 100 \text{V/m}$$

$$J = \frac{E}{\rho} = \sigma E$$

$$\sigma = \underline{\underline{\frac{J}{E} = 6 \cdot 10^{-15} (\Omega\text{m})^{-1}}}}$$