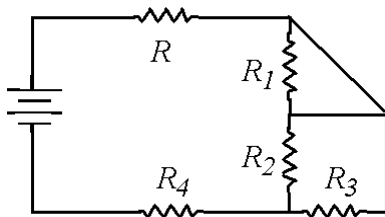


quiz3-1bw10


Multiple Choice

Identify the letter of the choice that best completes the statement or answers the question.

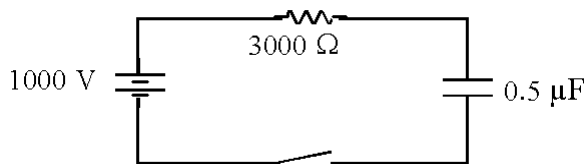- _____ 1. A nichrome wire has a radius of 0.50 mm and a resistivity of $1.5 \times 10^{-6} \Omega \cdot m$. If the wire carries a current of 0.50 A, what is the potential difference per unit length along this wire?
- 0.003 V/m
 - 0.95 V/m
 - 1.6 V/m
 - 1.9 V/m
 - 7.4 V/m
- _____ 2. Which resistor is in series with resistor R?




- R1
 - R2
 - R3
 - R4
 - None of the four resistors above is valid.
- _____ 3. An electric toaster requires 1 100 W at 110 V. What is the resistance of the heating coil?
- 7.5 Ω
 - 9.0 Ω
 - 10.0 Ω
 - 11.0 Ω
 - 13.0 Ω
- _____ 4. A 1 000-V battery, a 3 000- Ω resistor and a 0.50- μ F capacitor are connected in series with a switch. The capacitor is initially uncharged. What is the value of the current the moment after the switch is closed?




- 0.39 A
- 0.33 A
- 0.84 A
- 2 000 A
- 1.0 A

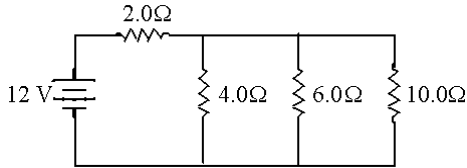- _____ 5. Three resistors connected in parallel have individual values of 4.0, 6.0 and 10.0 Ω , respectively. If this combination is connected in series with a 12-V battery and a 2.0- Ω resistor, what is the current in the 10- Ω resistor?



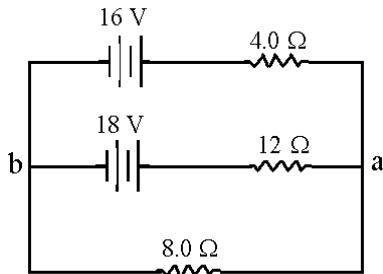- a. 0.59 A
 b. 1.0 A
 c. 11 A
 d. 16 A
 e. 23 A
- _____ 6. What is the potential difference between points a and b?



- a. 6 V
 b. 8 V
 c. 12 V
 d. 24 V
 e. 27 V
- _____ 7. If a metallic wire of cross sectional area $3.0 \times 10^{-6} \text{ m}^2$ carries a current of 6.0 A and has a mobile charge density of $4.24 \times 10^{28} \text{ carriers/m}^3$, what is the average drift velocity of the mobile charge carriers? (charge value = $1.6 \times 10^{-19} \text{ C}$)
- a. $3.4 \times 10^3 \text{ m/s}$
 b. $1.7 \times 10^3 \text{ m/s}$
 c. $1.5 \times 10^{-4} \text{ m/s}$
 d. $2.9 \times 10^{-4} \text{ m/s}$
 e. $1.2 \times 10^{-1} \text{ m/s}$
- _____ 8. How long is a wire made from a volume 100 cm^3 of copper if its resistance is 8.5 ohms? The resistivity of copper is $1.7 \times 10^{-5} \Omega \cdot \text{m}$.
- a. 7.1 m
 b. $1.7 \times 10^2 \text{ m}$
 c. $2.2 \times 10^2 \text{ m}$
 d. $3.0 \times 10^3 \text{ m}$
 e. $4.7 \times 10^3 \text{ m}$

quiz3-1bw10
Answer Section**MULTIPLE CHOICE**

1. ANS: B DIF: 2 TOP: 17.5 Resistivity
2. ANS: D DIF: 2
TOP: 18.1 Sources of emf, 18.2 Resistors in Series, 18.3 Resistors in Parallel
3. ANS: D DIF: 2 TOP: 17.8 Electrical Energy and Power
4. ANS: B DIF: 2 TOP: 18.5 RC Circuits
5. ANS: A DIF: 3
TOP: 18.1 Sources of emf, 18.2 Resistors in Series, 18.3 Resistors in Parallel
6. ANS: C DIF: 3
TOP: 18.4 Kirchhoff's Rules and Complex DC Circuits
7. ANS: D DIF: 2
TOP: 17.2 A Microscopic View: Current and Drift Speed
8. ANS: A DIF: 3 TOP: 17.5 Resistivity