

PHY 1B(b) Chapter 18 Solutions

⑤

a) For parallel resistors,

$$R_{eq,p} = \left(\frac{1}{7.00\Omega} + \frac{1}{10.0\Omega} \right)^{-1} = 4.12\Omega$$

$$\Rightarrow R_{ab} = R_4 + R_{eq,p} + R_9 = 4.00\Omega + 4.12\Omega + 9.00\Omega = \boxed{17.1\Omega}$$

$$b) I_{ab} = \frac{(\Delta V)_{ab}}{R_{ab}} = \frac{34.0\text{V}}{17.1\Omega} = 1.99\text{A}$$

$$\Rightarrow I_4 = I_9 = 1.99\text{A}$$

$$\text{Also, } (\Delta V)_p = I_{ab} R_{eq,p} = (1.99\text{A})(4.12\Omega) = \boxed{8.18\text{V}}$$

$$\Rightarrow I_7 = \frac{(\Delta V)_p}{R_7} = \frac{8.18\text{V}}{7.00\Omega} = \boxed{1.17\text{A}}$$

$$\Rightarrow I_{10} = \frac{(\Delta V)_p}{R_{10}} = \frac{8.18\text{V}}{10.0\Omega} = \boxed{0.818\text{A}}$$

$$\textcircled{8} \quad a) R_{p,10,5} = \frac{(10\Omega)(5\Omega)}{10\Omega + 5\Omega} = \frac{10}{3}\Omega$$

$$R_{s, \frac{10}{3}, 4} = \frac{10}{3}\Omega + 4\Omega = 7.33\Omega$$

$$R_{p, 7.33, 3} = \frac{(7.33\Omega)(3\Omega)}{7.33\Omega + 3\Omega} \approx 2.13\Omega$$

$$R_{eq} = 3\Omega + 2.13\Omega = 5.13\Omega$$

$$b) P = \frac{(\Delta V)^2}{R_{eq}} \Rightarrow \Delta V = \sqrt{P \cdot R_{eq}}$$

$$\Rightarrow \Delta V = \sqrt{(4\text{ W})(5.13\Omega)} = \boxed{4.53\text{ V}}$$


$\textcircled{14}$ Parallel combo of 3Ω and 1Ω has resistance

$$R_p = \frac{(3\Omega)(1\Omega)}{3\Omega + 1\Omega} = .75\Omega$$

$$R_{eq, T} = 2\Omega + 0.75\Omega + 4\Omega = 6.75\Omega$$

\Rightarrow current supplied by battery is
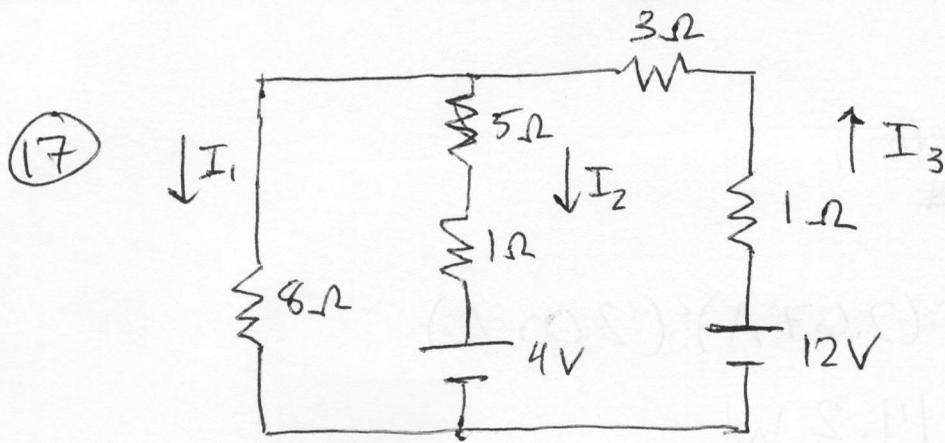
$$I = \frac{\Delta V}{R_{eq}} = \frac{18\text{ V}}{6.75\Omega} = 2.67\text{ A}$$



Kirchhoff's loop rule on right most loop.

$$+12.0\text{V} - (1\Omega + 3\Omega)I_3 - (5\Omega + 1\Omega)I_2 - 4.0\text{V} = 0$$

$$\Rightarrow (2\Omega)I_3 + (3\Omega)I_2 = 4\text{V}$$

On leftmost loop,

$$+4\text{V} + (1\Omega + 5\Omega)I_2 - (8\Omega)I_1 = 0$$

$$\Rightarrow (4\Omega)I_1 - (3\Omega)I_2 = 2\text{V}$$

Also, from Kirchhoff's junction rule,

$$I_3 = I_1 + I_2$$

Three equations and three unknowns, so we can solve this to give

$$I_1 = 0.846\text{A}$$

$$I_2 = 0.462\text{A}$$

$$I_3 = 1.31\text{A}$$

⑭ In $2\ \Omega$ resistor,

$$P_2 = I^2 R^2 = (2.67\text{ A})^2 (2.00\ \Omega) \\ = 14.2\text{ W}$$

In $4\ \Omega$ resistor,

$$P_4 = I^2 R_4 = (2.67\text{ A})^2 (4.00\ \Omega) \\ = 28.4\text{ W}$$


Potential difference across parallel combo of $3+1\ \Omega$ resistors,

$$(\Delta V)_p = IR_p = (2.67\text{ A})(0.75\ \Omega) = 2.00\text{ V}$$

$$\Rightarrow P_3 = \frac{(\Delta V)_p^2}{R_3} = \frac{(2.00\text{ V})^2}{3.00\ \Omega} = \boxed{1.33\text{ W}}$$

$$\text{and } P_1 = \frac{(\Delta V)_p^2}{R_1} = \frac{(2.00\text{ V})^2}{1.00\ \Omega} = \boxed{4.00\text{ W}}$$

26

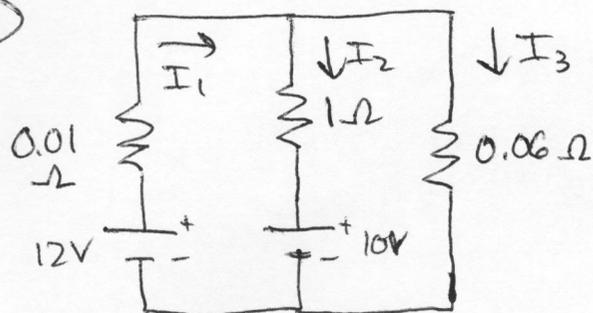

Outer perimeter:

$$+12V - (0.01\Omega)I_1 - (0.06\Omega)I_3 = 0$$

$$\Rightarrow I_1 + 6I_3 = 1.2 \times 10^3 \text{ A}$$

For rightmost loop,

$$+10V + (1\Omega)I_2 - (0.06\Omega)I_3 = 0$$

$$\Rightarrow I_2 - 0.06I_3 = -10 \text{ A}$$

Kirchhoff's junction rule,


$$I_1 = I_2 + I_3$$

Using these equations,

$$I_2 = 0.28 \text{ A (in dead battery)}$$

$$I_3 = 1.7 \times 10^2 \text{ A (in starter)}$$

34

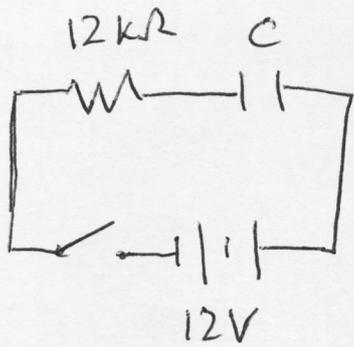

Charge on capacitor at time t is

$$Q = Q_{\max} (1 - e^{-t/\tau})$$

$$Q = C(\Delta V) \text{ and } Q_{\max} = C\varepsilon$$

$$\Rightarrow C(\Delta V) = C\varepsilon (1 - e^{-1s/\tau})$$

$$10V = 12V (1 - e^{-1s/\tau})$$

$$\Rightarrow \frac{1}{6} = e^{-1s/\tau} \Rightarrow e^{1s/\tau} = 6$$

$$\Rightarrow \frac{1s}{\tau} = \ln 6 \Rightarrow \tau = \frac{1s}{\ln 6} \approx 0.56s.$$

Since $\tau = RC$,

$$C = \frac{\tau}{R} = \frac{0.56s}{12 \times 10^3 \Omega} = 4.7 \times 10^{-5} F = \boxed{47 \mu F}$$

48 From $P = \frac{(\Delta V)^2}{R}$

$$\Rightarrow R = \frac{(\Delta V)^2}{P} = \frac{(120\text{V})^2}{60\text{W}} = 240\ \Omega$$

for each bulb, assuming resistance is constant...

$$R_{\text{eq, total}} = R_1 + \frac{R_2 R_3}{R_2 + R_3} = 240\ \Omega + \frac{(240\ \Omega)(240\ \Omega)}{480\ \Omega}$$

$$= 360\ \Omega.$$

Therefore, total power delivered to the circuit is

$$P = \frac{(\Delta V)^2}{R_{\text{eq}}} = \frac{(120\text{V})^2}{360\ \Omega} = \boxed{40\ \text{W}}$$

54 $Q = Q_{\text{max}}(1 - e^{-t/\tau})$

and $\tau = RC = (2.0 \times 10^6\ \Omega)(3.0 \times 10^{-6}\ \text{F}) = 6.0\ \text{s}$

Want $Q = .90 Q_{\text{max}}$, which gives $0.90 = 1 - e^{-t/\tau}$

$$\Rightarrow e^{-t/\tau} = 0.10 \Rightarrow -\frac{t}{\tau} = \ln(0.10)$$

$$\Rightarrow t = -(6.0\ \text{s})(\ln(0.10)) = \boxed{14\ \text{s}}$$

(18) From $P = \frac{(\Delta V)^2}{R}$

$\Rightarrow R = \frac{(\Delta V)^2}{P} = \frac{(150V)^2}{210W} = 107.14 \Omega$

Find the maximum average power

Power = $P_1 + P_2 = 210W = \frac{(210V)^2}{R} + \frac{(210V)^2}{R}$

$= 300W$

Therefore, total power delivered to the circuit is

$P = \frac{(\Delta V)^2}{R} = \frac{(150V)^2}{300\Omega} = 75W$

(19) $G = G_m(1 - e^{-\alpha})$

and $e = RC = (0.0 \times 10^{-6}) \times (3 \times 10^4) = 0.003$

Want $G = 0.99G_m$ with given $0.003 = e^{-\alpha}$

$\Rightarrow e^{-\alpha} = 0.01 \Rightarrow -\alpha = \ln(0.01)$

$\Rightarrow \alpha = -\ln(0.01) = 4.605$