

ANSWER KEY

Physics 1B(b) Quiz 3

Winter 2010



Version B

Reff in series > Reff in parallel

$\Rightarrow \tau_{series} > \tau_{parallel} \Rightarrow B \text{ charges up faster than A}$

Problem 1: I charge up a capacitor C in the following configurations. Which configuration charges the capacitor faster?

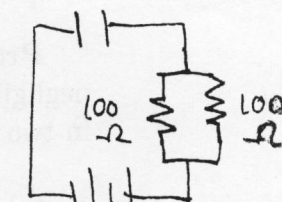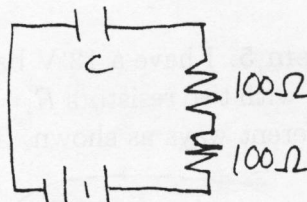- (a) A charges up faster than B
- (b) B charges up faster than A
- (c) Both A and B charge up at the same rate



• Time constant = $\tau = RC$

• Bigger time constant means longer time to charge up A

Problem 2: The resistivity of tungsten is 5.6×10^{-8} ohms-m. If I make a light bulb filament from tungsten wire that has a radius of .01 mm designed for a 100 W light bulb with 120 V, what is the length of the wire I need in the filament?

- (a) 0.340 m
- (b) 0.100 m
- (c) 0.679 m
- (d) 0.808 m


$$R = \frac{\rho L}{A} \text{ and } P = \frac{(\Delta V)^2}{R} \Rightarrow R = \frac{(\Delta V)^2}{P}$$

$$\Rightarrow \frac{(\Delta V)^2}{P} = \frac{\rho L}{A} \Rightarrow L = \frac{A(\Delta V)^2}{\rho P} = \frac{\pi(10^{-5} \text{ m})^2 \cdot (120 \text{ V})^2}{(5.6 \times 10^{-8} \text{ } \Omega \cdot \text{m})(100 \text{ W})}$$

Problem 3: When I close the switch in the circuit shown, the capacitor begins to charge. What is the current in the resistor after 50 milliseconds? .808 mA

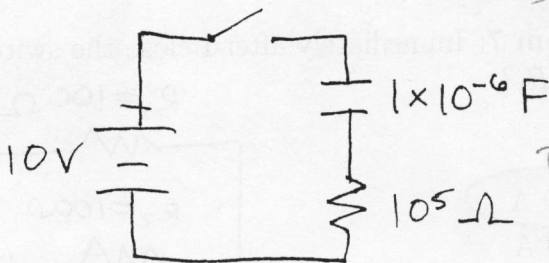- (a) 1.21×10^{-4} A
- (b) 6.07×10^{-3} A
- (c) 6.07×10^{-5} A
- (d) Zero

$\rightarrow t = 50 \text{ ms} = 5 \times 10^{-2} \text{ s}$



$$\tau = RC = (10^{-6} \text{ F})(10^5 \text{ } \Omega) = 0.1 \text{ s}$$

Capacitor charge-up eqn:

$$Q = Q_{max}(1 - e^{-t/\tau})$$

$$= \epsilon C(1 - e^{-5 \times 10^{-2} / 0.1}) = \epsilon C(1 - e^{-0.5})$$

$$= (10 \text{ V})(10^{-6} \text{ F})(.393) = 3.93 \times 10^{-6} \text{ C}$$

Kirchhoff's Loop Rule:

$$\epsilon - IR - \frac{Q}{C} = 0$$

At Q_{max} , $I = 0$

$$\Rightarrow \epsilon - IR - \frac{Q_{max}}{C} = 0$$

$$\Rightarrow Q_{max} = \epsilon C$$

Back to Loop Rule, $10 \text{ V} - I(10^5 \text{ } \Omega) - \frac{3.93 \times 10^{-6} \text{ C}}{10^{-6} \text{ F}} = 0$

$$\Rightarrow I = 6.07 \times 10^{-5} \text{ A}$$

Version B

Problem 4: Referring to the previous problem, what is the charge on the capacitor after 100 milliseconds?

After 100 ms,



- (a) $5.18 \times 10^{-5} \text{ C}$
- (b) $6.32 \times 10^{-6} \text{ C}$
- (c) $3.68 \times 10^{-8} \text{ C}$
- (d) Zero

$$Q = Q_{\max} (1 - e^{-t/\tau})$$

$$\Rightarrow Q = (10\text{V} \times 10^{-6}\text{F}) (1 - e^{-0.15/0.15}) = 6.32 \times 10^{-6} \text{ C}$$

Problem 5: I have a 12 V battery with an internal resistance that is low (i.e., $r = \text{negligible}$) with two resistors $R_1 = 100 \text{ ohms}$ and $R_2 = 50 \text{ ohms}$. I wire up the components in two different ways as shown. The power dissipated in the circuits is

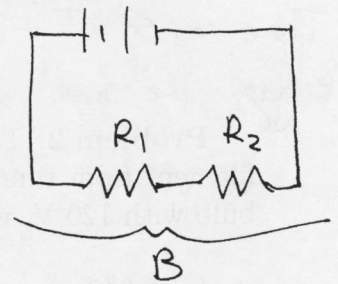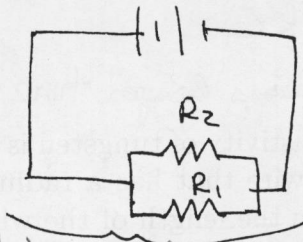- (a) greater in A than in B
- (b) the same for both A and B
- (c) greater in B than in A



$$P = \frac{(\Delta V)^2}{R}$$


$R_{\text{eff, series}} > R_{\text{eff, parallel}}$

\Rightarrow Power dissipated in A is greater

Problem 6: What is the total resistance of the circuit below?

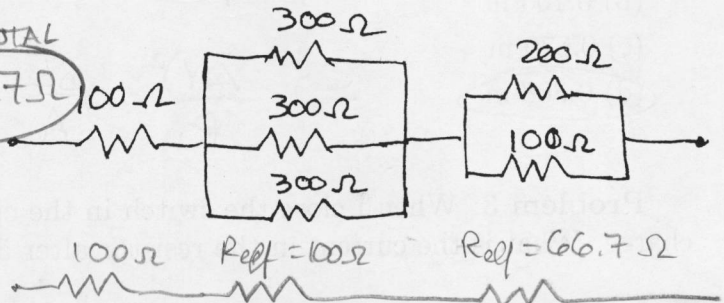- (a) 1400.0 ohms
- (b) 666.7 ohms
- (c) 366.7 ohms
- (d) 837.2 ohms

$\Rightarrow R_{\text{eff, total}} = 2(666.7 \Omega)$




(e) None of the above

Problem 7: Immediately after I close the switch in the circuit shown, what is the current in R_1 ?

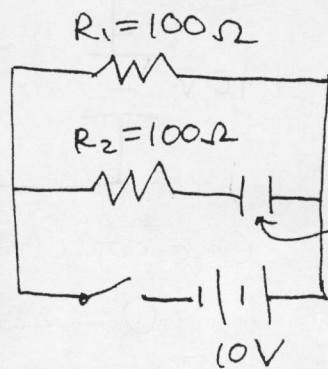- (a) zero
- (b) 0.10 A
- (c) 0.20 A
- (d) 0.05 A

Immediately after I close the switch, $t \sim 0$.



$$\Rightarrow V = IR_1$$

$$\Rightarrow I = \frac{V}{R_1}$$

$$\Rightarrow I = \frac{10\text{V}}{100 \Omega}$$

$$\Rightarrow I = 0.1 \text{ A}$$

$$\Rightarrow Q = Q_{\max} (1 - e^{-0.05/\tau})$$

$$= Q_{\max} (1 - 1) = 0$$

$$\Rightarrow Q = 0$$

\rightarrow therefore, circuit essentially becomes



Version B

Problem 8: Referring to the circuit above, what is the charge on the capacitor after a long time? Is there a current in R_1 ?

After a long time, $t \rightarrow \infty$

- (a) 10^{-7} C and no current in R_1
- (b) 10^{-5} C and yes, there is a current in R_1
- (c) 10^{-7} C and yes, there is a current in R_1
- (d) 10^{-5} C and no current in R_1


$\Rightarrow Q_{\max} = \mathcal{E}C$

$= (10V)(10^{-6}F) = 10^{-5}C$

And since R_1 is in a separate branch, it will still have a current

Problem 9: Use Kirchoff's rules to solve the following circuit. What is the current through the 5 ohm resistor? (Hint: Start at point "a" and go around each of the loops. Define a current direction.)

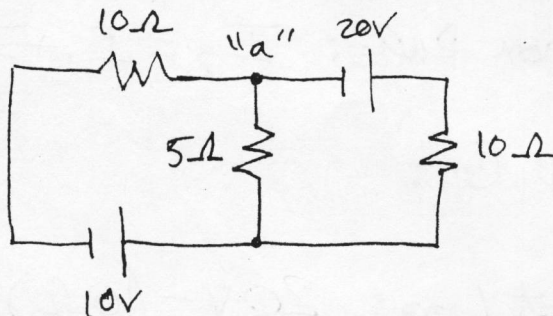- (a) 1.00 A
- (b) 1.25 A
- (c) 1.50 A
- (d) 2.00 A




(See next page)

Problem 10: A long, long time ago when I was young, one of the things at Christmas that drove me crazy was the Christmas tree lights because very often none of them lit up. How could this have happened?

- (a) I forgot to plug the string of lights in
- (b) They were connected in series and one burnt out bulb opened the circuit
- (c) Too many strings were connected together and a fuse blew
- (d) All of these
- (e) None of these

Mark Version B on your Scantron

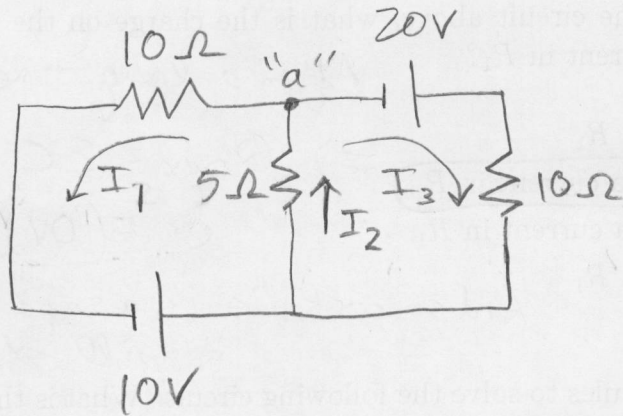

Junction Rule: $I_2 = I_1 + I_3$

Loop Rule:

Rightmost Loop: $20V - (10\Omega)I_3 - (5\Omega)I_2 = 0$

$$\Rightarrow 4A - 2I_3 - I_2 = 0$$

Leftmost Loop: $10V - (5\Omega)I_2 - (10\Omega)I_1 = 0$

$$\Rightarrow 2A - I_2 - 2I_1 = 0$$

$$\Rightarrow 6A - 2(I_1 + I_3) - 2I_2 = 0$$

$$\Rightarrow 6A - 2I_2 - 2I_2 = 0$$

$$\Rightarrow 6A = 4I_2$$

$$\Rightarrow I_2 = 1.5 A$$