

Problem

12. The current in an inductor is changing at the rate of 100 A/s, and the inductor emf is 40 V. What is its self-inductance?

Solution

From Equation 32-5, $L = |\mathcal{E}|/(dI/dt) = 40 \text{ V}/(100 \text{ A/s}) = 0.4 \text{ H}$.

Problem

15. A cardboard tube measures 15 cm long by 2.2 cm in diameter. How many turns of wire must be wound on the full length of the tube to make a 5.8-mH inductor?

Solution

From Equation 32-4, $N = \sqrt{L\ell/\mu_0 A} = [(5.8 \text{ mH})(15 \text{ cm})/(4\pi \times 10^{-7} \text{ H/m})(1.1 \text{ cm})^2]^{1/2} = 1.35 \times 10^3$ turns.

Problem

16. The current in a 2.0-H inductor is given by $I = 3t^2 + 15t + 8$, where t is in seconds and I in amperes. Find an expression for the magnitude of the inductor emf.

Solution

From Equation 32-5, $|\mathcal{E}| = |L dI/dt| = 2(6t + 15)$, where \mathcal{E} is in volts and t is in seconds.

Problem

18. The current in a 40-mH inductor is given by $I = I_0 e^{-bt}$, where $I_0 = 10 \text{ A}$ and $b = 20 \text{ s}^{-1}$. What is the magnitude of the inductor emf at (a) $t = 0$, (b) $t = 25 \text{ ms}$, and (c) $t = 50 \text{ ms}$?

Solution

The magnitude of the inductor emf is $|\mathcal{E}| = L|dI/dt| = LI_0 b e^{-bt}$, from Equation 32-5. (a) At $t = 0$, $|\mathcal{E}(0)| = (40 \text{ mH})(10 \text{ A})(20 \text{ s}^{-1}) = 8 \text{ V}$, so (b) at $t = 25 \text{ ms}$, $|\mathcal{E}(t)| = (8 \text{ V})e^{-0.5} = 4.85 \text{ V}$, and (c) $|\mathcal{E}(50 \text{ ms})| = 2.94 \text{ V}$.

Problem

21. The emf in a 50-mH inductor is given by $\mathcal{E} = E_p \sin \omega t$, where $E_p = 75 \text{ V}$ and $\omega = 140 \text{ s}^{-1}$. What is the peak current in the inductor? (Assume the current swings symmetrically about zero.)

Solution

From Equation 32-5, $dI/dt = (\mathcal{E}_p/L) \sin \omega t$, so integration yields $I(t) = (E_p/\omega L) \cos \omega t$. (Since $I(t)$ is symmetric about $I = 0$, the constant of integration is zero.) The peak current is $I_p = E_p/\omega L = 75 \text{ V}/(140 \text{ s}^{-1} \times 50 \text{ mH}) = 10.7 \text{ A}$.

Problem

4. Two coils have a mutual inductance of 580 mH. One coil is supplied with a current given by $I = 3t^2 + 2t + 4$, where I is in amperes and t in seconds. What is the induced emf in the other coil at time $t = 2.5 \text{ s}$?

Solution

Since $dI_1/dt = 6t \text{ A/s}$, Equation 32-2 gives, for $t = 2.5 \text{ s}$, $\mathcal{E}_2 = (580 \text{ mH})(6 \text{ A/s}) = 7.54 \text{ V}$ (see comment in solution to Problem 1).

Problem

8. Coils A and B have mutual inductance 25 mH . At time $t = 0$ the current in coil A is zero. Subsequently a time-varying current is supplied to A , and the induced emf in coil B is given by $\mathcal{E} = 50 + 0.2t$, with \mathcal{E} in V and t in ms. Find an expression for the time-varying current in coil A .

Solution

Equation 32-2 specifies $\mathcal{E}_B = -M dI_A/dt$, so $dI_A/dt = -(50 \text{ V} + (0.2 \text{ V/ms})t)/(25 \text{ mH})$. Integrating, and using $I_A(0) = 0$, we find $I_A(t) = -(2 \text{ A/ms})t + (4 \text{ A}/(\text{ms})^2)t^2$. The direction of I_A depends on how the coils are coupled.

Problem

9. A rectangular loop of length ℓ and width w is located a distance a from a long, straight, wire, as shown in Fig. 32-20. What is the mutual inductance of this arrangement?

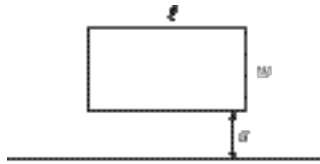


FIGURE 32-20 Problem 9.

Solution

When current I_1 flows to the left in the wire, the flux through the loop is $\Phi_{B,2} = (\mu_0 I_1/2\pi) \int_a^{a+w} \ell dr/r = (\mu_0 I_1 \ell/2\pi) \ln(1 + w/a)$ (see Example 31-2). Then Equation 32-1 gives $M = \Phi_{B,2}/I_1 = (\mu_0 \ell/2\pi) \ln(1 + w/a)$. (In calculating the flux, the normal to the loop area was taken into the page, so the positive sense of circulation around the loop is CW. This determines the direction of the induced emf \mathcal{E}_2 in Equation 32-2.)

Problem

10. Two wire loops of radii a and b lie in the same plane and have a common center. Find the mutual inductance of this arrangement, assuming $b \ll a$. *Hint:* With $b \ll a$, the magnetic field will be essentially uniform over the smaller loop. See Example 30-1.

Solution

If $b \ll a$ is assumed, the magnetic field from the large loop is essentially uniform over the small loop, and equal to the value at the center of the large loop, $B_b = \mu_0 I_b/2b$. Therefore, the flux through the small loop (due to current in the large loop) is $\Phi_{B,a} = B_b A_a = (\mu_0 I_b/2b)(\pi a^2)$, and the mutual inductance is $M = \Phi_{B,a}/I_b = \mu_0 \pi a^2/2b$. (Note: It would be more difficult to calculate $\Phi_{B,b} = \Phi_{B,b}$, from the dipole field of the small loop, but the result for M would be the same.)

Problem

28. In a series RL circuit like Fig. 32-8a, $\mathcal{E}_0 = 45 \text{ V}$, $R = 3.3 \text{ } \Omega$, and $L = 2.1 \text{ H}$. If the current is 9.5 A , how long has the switch been closed?

Solution

As in the previous problem, $t = (L/R) \ln(1 + I/I_0)$. Here, $I_0 = E_0/R = 45 \text{ V}/3.3 \Omega = 13.6 \text{ A}$, so $t = (2.1 \text{ H}/3.3 \Omega) \ln(1 + 9.5/13.6) = 0.759 \text{ s}$.

Problem

30. A series RL circuit like Fig. 32-8a has $E_0 = 60 \text{ V}$, $R = 22 \Omega$, and $L = 1.5 \text{ H}$. Find the rate of change of the current
 (a) immediately after the switch is closed and (b) 0.10 s later.

Solution

From Equations 32-5, and 7, $dI/dt = (E_0/L)e^{-Rt/L}$. (a) For $t = 0$, $dI/dt = E_0/L = 60 \text{ V}/1.5 \text{ H} = 40 \text{ A/s}$.
 (b) For $t = 0.1 \text{ s}$, $dI/dt = (40 \text{ A/s})e^{-(22 \Omega)(0.1 \text{ s})/(1.5 \text{ H})} = 9.23 \text{ A/s}$.

Problem

33. Resistor R_2 in Fig. 32-22 is to limit the emf that develops when the switch is opened. What should be its value in order that the inductor emf not exceed 100 V?

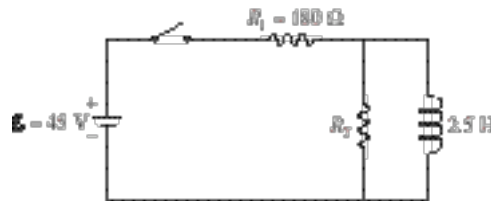


FIGURE 32-22 Problem 33.

Solution

As explained in Example 32-6, when the switch is opened (after having been closed a long time), the voltage across R_2 (which equals the inductor emf) is $V_2 = I_2 R_2 = E_0 R_2 / R_1$. If we choose to limit this to no more than 100 V, then $R_2 \leq (100 \text{ V})(180 \Omega) / 45 \text{ V} = 400 \Omega$.

Problem

36. In Fig. 32-23, take $E_0 = 12 \text{ V}$, $R_1 = 4.0 \Omega$, $R_2 = 8.0 \Omega$, $R_3 = 2.0 \Omega$, and $L = 2.0 \text{ H}$. What is the current I_2
 (a) immediately after the switch is first closed and (b) a long time after the switch is closed? (c) After a long time the switch is again opened. Now what is I_2 ?

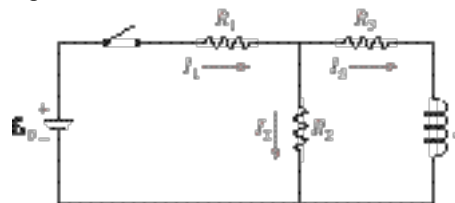


FIGURE 32-23 Problem 36.

Solution

(a) As explained in Example 32-6, the inductor current is zero just after the switch is closed. At this instant, the currents can be determined from the circuit with the inductance open-circuited, so that its branch can be removed. Thus, $I_3 = 0$, and $I_1 = I_2 = E_0 / (R_1 + R_2) = 12 \text{ V} / (4 + 8) \Omega = 1 \text{ A}$.




Problem 36 Solution (a)

(b) After the currents have been flowing a long time, they reach steady values ($di/dt = 0$), and the voltage across the inductance is zero. The currents can be found by short-circuiting the inductance (see Example 32-6 again, and refer to Chapter 28 if necessary):

$$I_1 = \frac{E}{R_1 + R_2 R_3 / (R_2 + R_3)} = \frac{12 \text{ V}}{4 + 8 \cdot 2 / 10} = 2.14 \text{ A},$$


$$I_2 = \frac{R_3}{R_2 + R_3} I_1 = \frac{2}{10} I_1 = 0.429 \text{ A}, \text{ and}$$
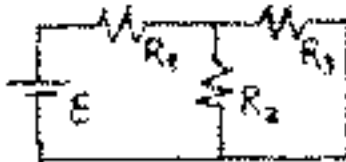
$$I_3 = I_1 R_2 / (R_2 + R_3) = \frac{4}{10} I_1 = 0.857 \text{ A}.$$



Problem 36 Solution (b)

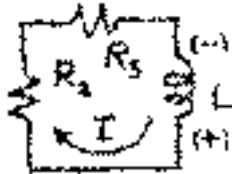(c) When the switch is reopened, no current flows through the battery's branch, $I_1 = 0$, which can be removed from the circuit to calculate $I_2 = I_3$ at this instant. The induced emf acts to keep the current flowing at its value in part (b) (as explained in Example 32-6), so $I_2 = I_3 = 0.857 \text{ A}$.



Problem 36 Solution (c)

Problem

37. In Fig. 32-24, take $E_0 = 20 \text{ V}$, $R_1 = 10 \Omega$, $R_2 = 5.0 \Omega$, and assume the switch has been open for a long time. (a) What is the inductor current immediately after the switch is closed? (b) What is the inductor current a long time after the switch is closed? (c) If after a long time the switch is again opened, what will be the voltage across R_1 immediately afterward?

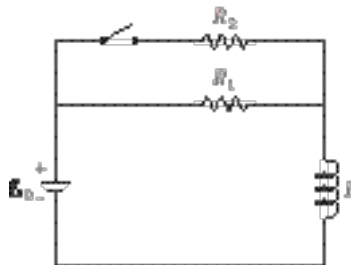


FIGURE 32-24 Problem 37.

Solution

(a) If the switch has been open a long time, a steady current flows through the inductance ($dI_L/dt = 0$). When the switch is closed (at $t = 0$), I_L cannot change instantaneously, so $I_L(0) = E/R_1 = 20 \text{ V}/10 \Omega = 2 \text{ A}$. (Of course, $I_1(0) = I_L(0)$, and $I_2(0) = 0$.) (b) After another long time ($t \gg \tau$), the currents are steady again and $E_L = 0$ (the inductance behaves like a short circuit). The resistors are in parallel; therefore $I_L(\infty) = E/(R_1 + R_2) = 20 \text{ V}(\frac{1}{5} + \frac{1}{10})^{-1} = 6 \text{ A}$. (c) When the switch is again opened, the current through R_2 is zero, but I_L cannot change instantly, so $I_L = I_1 = I_L(\infty) = 6 \text{ A}$. Thus, the voltage across R_1 is $V_1 = I_1 R_1 = (6 \text{ A})(10 \Omega) = 60 \text{ V}$.

Problem

38. How much energy is stored in a 5.0-H inductor carrying 35 A?

Solution

Equation 32-10 gives $U = \frac{1}{2}LI^2 = \frac{1}{2}(5 \text{ H})(35 \text{ A})^2 = 3.06 \text{ kJ}$.

Problem

43. The current in a 2.0-H inductor is decreased linearly from 5.0 A to zero over 10 ms. (a) What is the average rate at which energy is being extracted from the inductor during this time? (b) Is the instantaneous rate constant?

Solution

(a) The energy falls from $U_i = \frac{1}{2}LI^2 = \frac{1}{2}(2 \text{ H})(5 \text{ A})^2 = 25 \text{ J}$ to $U_f = 0$ in $\Delta t = 10 \text{ ms}$, so the rate of decrease is $\Delta U/\Delta t = 25 \text{ J}/10 \text{ ms} = 2.5 \text{ kW}$. (b) The discussion in the text leading to Equation 32-10 shows that the instantaneous power is $P_L = LI(dI/dt)$, so even if dI/dt is constant, I and P_L are not.

Problem

46. A 500-turn solenoid is 23 cm long, 1.5 cm in diameter, and carries 65 mA. How much magnetic energy does it contain?

Solution

Combining Equations 32-4 and 10, we find $U = \frac{1}{2}(\mu_0 N^2 A/\ell)I^2 = (2 \times 10^{-7} \text{ H/m})(\frac{1}{2})(500)^2(1.5 \text{ cm})^2(65 \text{ mA})^2 / (23 \text{ cm}) = 0.510 \text{ mJ}$.