

chapter 33

Problem

32. An LC circuit includes a $20\text{-}\mu\text{F}$ capacitor and has a period of 5.0 ms . The peak current is 25 mA . Find (a) the inductance and (b) the peak voltage.

Solution

(a) The inductance can be calculated from Equation 33-11:

$$L = \frac{1}{\omega^2 C} = \frac{T^2}{4\pi^2} \frac{1}{C} = \frac{(5\text{ ms})^2}{4\pi^2} \frac{1}{20\ \mu\text{F}} = 31.7\text{ mH}$$

(b) Fig. 33-12 and the expressions for the electric and magnetic energies for the LC circuit in the text imply that $\frac{1}{2} C V_p^2 = \frac{1}{2} L I_p^2$, so $V_p = I_p \sqrt{L/C} = (25\text{ mA}) \sqrt{31.7\text{ mH}/20\ \mu\text{F}} = 995\text{ mV}$.

Problem

37. One-eighth of a cycle after the capacitor in an LC circuit is fully charged, what are each of the following as fractions of their peak values: (a) capacitor charge, (b) energy in the capacitor, (c) inductor current, (d) energy in the inductor?

Solution

The equations in Section 33-3 give the desired quantities, which we evaluate when

$$\omega t = \omega(T/8) = 2\pi/8 = \frac{1}{4}\pi = 45^\circ$$

(i.e., $\frac{1}{8}$ cycle). (Note that phase constant zero corresponds to a fully charged capacitor at $t = 0$.) (a) From

Equation 33-10, $q = q_p \cos 45^\circ = \frac{1}{\sqrt{2}} q_p$. (b) From the equation for electric energy,

$$U_E = U_{E,p} \cos^2 45^\circ = \frac{1}{2} U_{E,p}$$

(c) From Equation 33-12, $i = -i_p \sin 45^\circ = -\frac{1}{\sqrt{2}} i_p$. (The direction of the current is away from the positive capacitor plate at $t = 0$.) (d) From the equation for magnetic energy,

$$U_B = U_{B,p} \sin^2 45^\circ = \frac{1}{2} U_{B,p}$$

Problem

38. Show from conservation of energy that the peak voltage and current in an LC circuit are related by

$$I_p = V_p \sqrt{C/L}$$

Solution

When all the energy is stored in the capacitor, $U_{\text{tot}} = \frac{1}{2} C V_p^2$, and when all is stored in the inductor,

$$U_{\text{tot}} = \frac{1}{2} L I_p^2$$

Therefore, $I_p = V_p \sqrt{C/L}$. (See Figure 33-10, parts (a), (c), (e), and (g).)

Problem

39. The $2000\text{-}\mu\text{F}$ capacitor in Fig. 33-30 is initially charged to 200 V . (a) Describe how you would manipulate switches A and B to transfer all the energy from the $2000\text{-}\mu\text{F}$ capacitor to the $500\text{-}\mu\text{F}$ capacitor. Include the times you would throw the switches. (b) What will be the voltage across the $500\text{-}\mu\text{F}$ capacitor once you've finished?

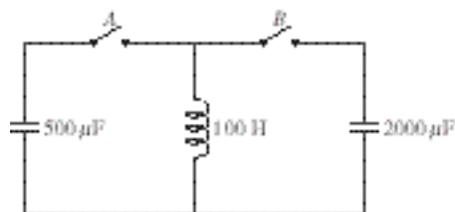


FIGURE 33-30 Problem 39.

Solution

(a) The energy initially stored in the first capacitor is $\frac{1}{2}(2 \text{ mF})(200 \text{ V})^2 = 40 \text{ J}$. First close switch B for one

quarter of a period of the LC circuit containing the $2000 \mu\text{F}$ capacitor, or

$t_B = \frac{1}{4}T_B = \frac{1}{4}(2\pi\omega_B) = \frac{1}{2}\pi\sqrt{LC_B} = \frac{1}{2}\pi\sqrt{(100 \text{ H})(2 \text{ mF})} = 702 \text{ ms}$. This transfers 40 J to the inductor.

Then open switch B and close switch A for one

quarter of a period of the LC circuit containing the $500 \mu\text{F}$ capacitor, or

$t_A = \frac{1}{2}\pi\sqrt{(100 \text{ H})(0.5 \text{ mF})} = \frac{1}{2}t_B = 351 \text{ ms}$.

This transfers 40 J to the second capacitor from the inductor. Finally, open switch A . (b) When the second capacitor

has 40 J of stored energy, its voltage is $\sqrt{2(40 \text{ J})(0.5 \text{ mF})} = 400 \text{ V}$.