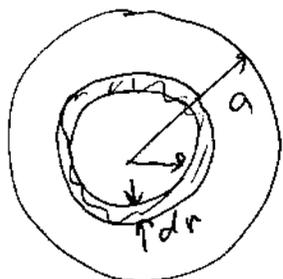


Homework 5

6.1A

$$j = j_0 r$$



in the small annulus of radius r and thickness dr we have

$$dA = 2\pi r dr$$

$$dI = j dr = j_0 r \cdot 2\pi r dr = 2\pi j_0 r^2 dr$$

Total current:

$$I = \int_0^a 2\pi j_0 r^2 dr = \underline{2\pi j_0 \frac{a^3}{3}}$$

6.1B

$$I = 10A$$

$$n = 10^{27}/m^3$$

$$A = 1mm^2 = 10^{-6}m^2$$

$$I = nevA$$

$$v = \frac{I}{neA} = \underline{0.0625 m/s}$$

6.1 C The period is

$$T = \frac{2\pi}{\omega}$$

current $I = \frac{q}{T} = \frac{\omega q}{2\pi}$

6.3 A

$$R = \frac{l}{A\sigma} = \frac{0,2 \text{ m}}{2 \cdot 10^{-4} \text{ m}^2 \cdot 0,59 \cdot 10^8 (\Omega \cdot \text{m})^{-1}}$$

$$R = 1,69 \cdot 10^{-5} \Omega$$

6.3 C

$$L = 0,1 \text{ m}$$

$$A = 2 \cdot 10^{-4} \text{ m}^2$$


$$R = 10^{-4} \Omega$$

$$L \rightarrow 0,05 \text{ m} = \frac{1}{2} L$$

to keep the same volume we need $A \rightarrow 2A$

$$R = \frac{\rho L}{A} \rightarrow \frac{\rho \frac{L}{2}}{2A} = \frac{R}{4} = \underline{\underline{2,5 \cdot 10^{-5} \Omega}}$$

6.4A

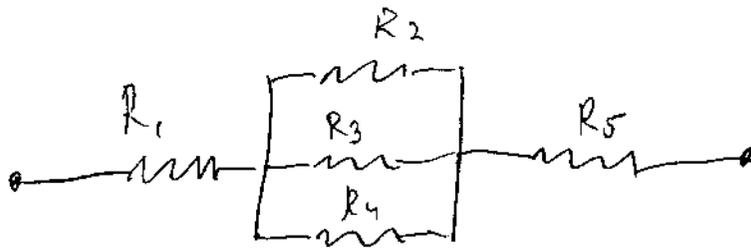

$$R_1 = 2 \Omega$$

$$R_2 = 3 \Omega$$

$$R_3 = 4 \Omega$$

$$R_4 = 6 \Omega$$

$$R_5 = 5 \Omega$$

a. 2, 3, 4 are in parallel;

$$\frac{1}{R_{234}} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} = \left(\frac{1}{3} + \frac{1}{4} + \frac{1}{6} \right) \Omega^{-1} =$$

$$= \frac{9}{12} \Omega^{-1} = \frac{3}{4} \Omega^{-1}$$

$$R_{234} = 1.33 \Omega$$

and is in series with 1 and 5

$$R = R_1 + R_{234} + R_5 = \underline{8.33 \Omega}$$

$$B. \quad V = 10V$$

$$I = \frac{V}{R} = 1.2A = I_1 = I_5 = I_{234}$$

$$P_1 = I_1^2 R_1 = \underline{2.88W}$$

$$P_5 = I_5^2 R_5 = \underline{7.2W}$$

Voltage for 2, 3, 4:


$$V_{234} = R_{234} \cdot I_{234} = 1.6V = V_2 = V_3 = V_4$$

$$P_2 = \frac{V_2^2}{R_2} = \underline{0.85W}$$

$$P_3 = \frac{V_3^2}{R_3} = \underline{0.64W}$$


$$P_4 = \frac{V_4^2}{R_4} = \underline{0.93W}$$

6, 4 B

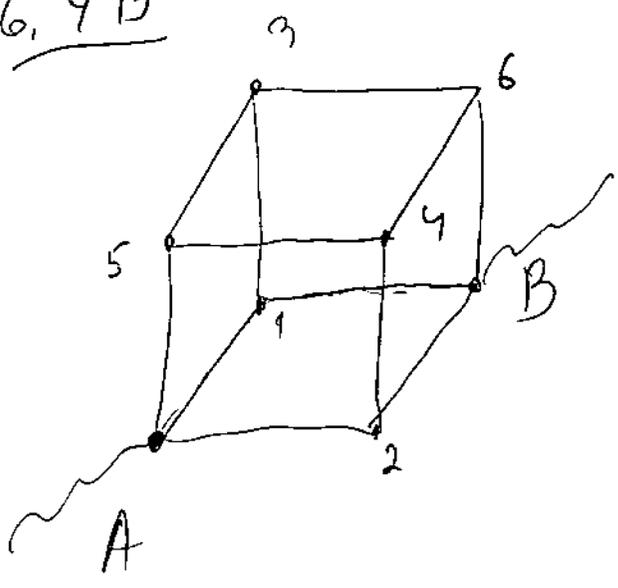


By symmetry, points 1 and 2 have the same potential, so they can be connected without changing the resistance. The same applies to points 3 and 4.

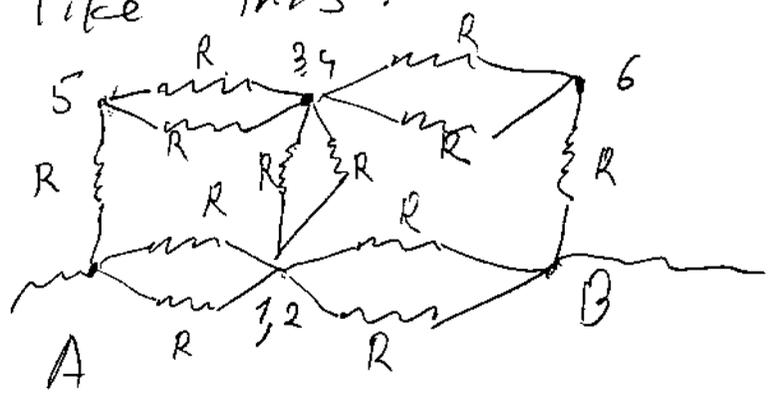The circuit can then be redrawn like this:




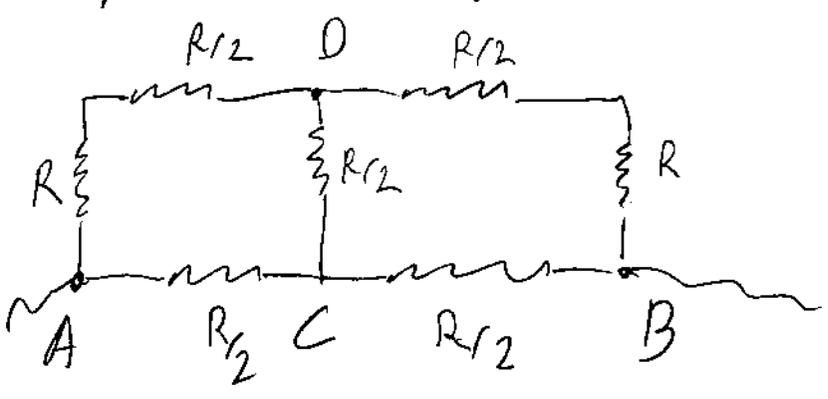Then pairs of parallel R-s can be replaced by $R/2$:



By symmetry, the current from A to C must be the same as the current from C to B, which means that there is no current from D to C, i.e. the resistance DC can be removed without changing anything.

Then we have

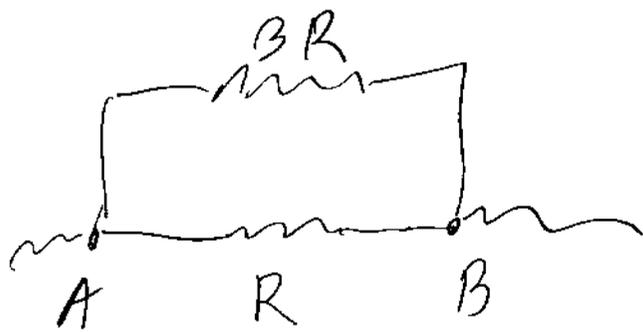


which gives

$$\frac{1}{R_{\text{total}}} = \frac{1}{R} + \frac{1}{3R} = \frac{4}{3R}$$

$$R_{\text{total}} = \frac{3R}{4}$$

6.4 E

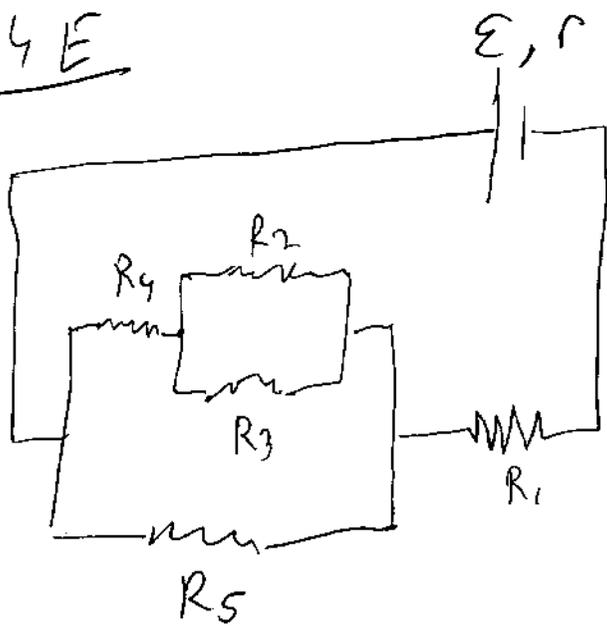

$$\mathcal{E} = 12 \text{ V}$$

$$r = 1 \Omega$$

$$R_1 = 1 \Omega$$

$$R_2 = 6 \Omega$$

$$R_3 = 12 \Omega$$

$$R_4 = 4 \Omega$$

$$R_5 = 8 \Omega$$

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} = \left(\frac{1}{6} + \frac{1}{12} \right) \Omega^{-1} = \frac{1}{4 \Omega}$$

$$R_{23} = 4 \Omega$$

$$R_{234} = R_{23} + R_4 = 8 \Omega$$

$$\frac{1}{R_{2345}} = \frac{1}{R_{234}} + \frac{1}{R_5} = \left(\frac{1}{8} + \frac{1}{8} \right) \Omega^{-1} = \frac{1}{4 \Omega}$$

$$R_{2345} = 4 \Omega$$

$$R_{12345} = R_1 + R_{2345} = 5 \Omega$$

$$R_{\text{total}} = R_{12345} + r = 6 \Omega$$

$$a. \quad I = \frac{\mathcal{E}}{R_{\text{total}}} = \underline{\underline{2 \text{ A}}}$$

$$b, c. I = I_1 = I_{2345} = \underline{2A}$$

$$P_1 = I_1^2 \cdot R_1 = \underline{4W}$$

$$V_{2345} = I_{2345} \cdot R_{2345} = 8V = V_{234} = V_5$$

$$I_5 = \frac{V_5}{R_5} = \underline{1A}$$

$$P_5 = I_5^2 \cdot R_5 = \underline{8W}$$

$$I_{234} = \frac{V_{234}}{R_{234}} = \underline{1A} = I_4 = I_{23}$$

$$P_4 = I_4^2 \cdot R_4 = \underline{4W}$$

$$V_{23} = I_{23} \cdot R_{23} = 4V = V_2 = V_3$$

$$I_2 = \frac{V_2}{R_2} = \underline{0,67A}$$


$$P_2 = I_2^2 \cdot R_2 = \underline{2,67W}$$

$$I_3 = \frac{V_3}{R_3} = \underline{0,33A}$$

$$P_3 = \underline{1,33W}$$

$$P_{\text{Battery}} = I^2 \cdot r = \underline{4W}$$

$$\underline{6.5A}$$

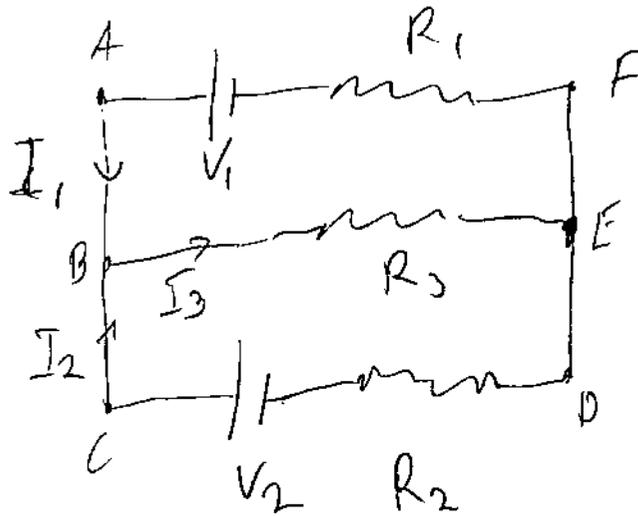

$$V_1 = 5V$$

$$V_2 = 2V$$

$$R_1 = 3\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 4\Omega$$

$$I_1 + I_2 = I_3$$

from loop ABEF:

$$-I_3 R_3 - I_1 R_1 + V_1 = 0$$

from loop CBED:

$$-I_3 R_3 - I_2 R_2 + V_2 = 0$$

putting together:

$$\begin{cases} I_1 + I_2 = I_3 \\ 3I_1 + 4I_3 = 5 \\ 2I_2 + 4I_3 = 2 \end{cases} \Rightarrow \begin{cases} I_1 + I_2 = I_3 \\ I_1 = \frac{5 - 4I_3}{3} \\ I_2 = \frac{2 - 4I_3}{2} \end{cases}$$

$$\frac{5 - 4I_3}{3} + \frac{2 - 4I_3}{2} = I_3$$

$$10 - 8I_3 + 6 - 12I_3 = 6I_3$$

$$16 = 26I_3$$

$$I_3 = \frac{8}{13} \text{ A}$$


$$I_1 = \frac{5 - 4I_3}{3} = \frac{11}{13} \text{ A}$$

$$I_2 = \frac{2 - 4I_3}{2} = -\frac{3}{13} \text{ A}$$

this means that the direction of I_2 is opposite to what we initially guessed,

6.5 B

a.

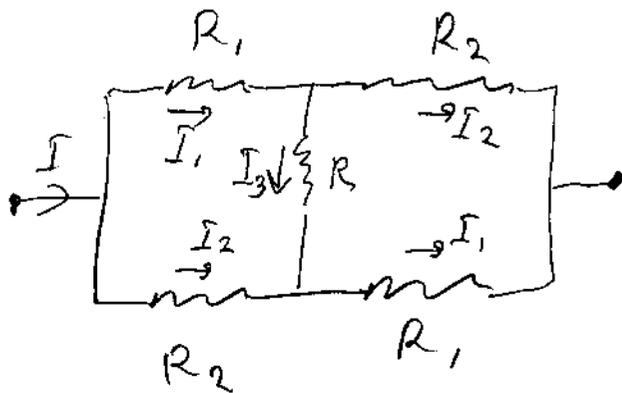

By symmetry, the current is the same through both R_1 -s, also through both R_2 -s, We have then

$$\begin{cases} I_3 = I_1 - I_2 \\ V = I_1 R_1 + I_2 R_2 \\ -I_1 R_1 - I_3 R + I_2 R_2 = 0 \end{cases}$$

plugging the first equation into the last one;

$$-I_1 R_1 - (I_1 - I_2) R + I_2 R_2 = 0$$

$$-I_1 (R_1 + R) + I_2 (R_2 + R) = 0$$

$$I_2 = \frac{I_1 (R_1 + R)}{R_2 + R}$$

from the second equation

$$V = I_1 \left(R_1 + R_2 \frac{R_1 + R}{R_2 + R} \right) = I_1 \frac{2R_1 R_2 + R_1 R + R_2 R}{R_2 + R}$$

$$I_1 = V \frac{R_2 + R}{2R_1 R_2 + R_1 R + R_2 R}$$

$$I_2 = V \frac{R_1 + R}{2R_1 R_2 + R_1 R + R_2 R}$$


$$I = I_1 + I_2 = V \frac{R_1 + R_2 + 2R}{2R_1 R_2 + R_1 R + R_2 R}$$

$$R_{\text{total}} = \frac{V}{I} = \frac{2R_1 R_2 + R_1 R + R_2 R}{R_1 + R_2 + 2R}$$

$$b. R_{\text{total}} = \frac{2 \cdot 4 \cdot 2 + 4 + 2}{4 + 2 + 2} \Omega = \underline{2.75 \Omega}$$

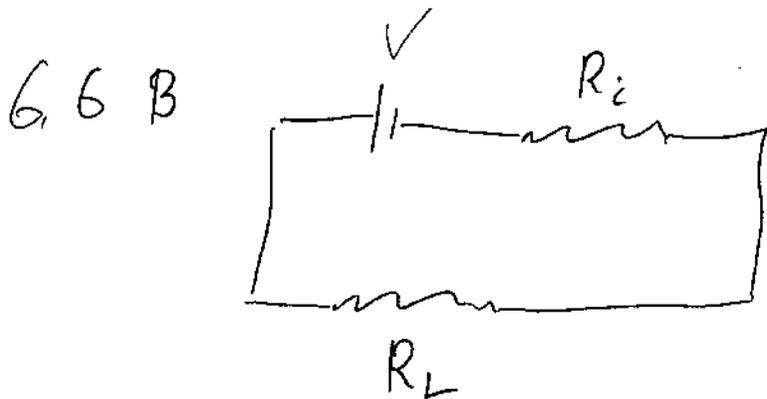c. If R is removed, we have two $(R_1 + R_2)$'s in parallel, i.e.

$$R_{\text{total}} = \frac{R_1 + R_2}{2} = \underline{3 \Omega}$$



$$I = \frac{V}{R_i + R_L}$$

$$P_L = I^2 R_L = \frac{V^2}{(R_i + R_L)^2} \cdot R_L = \frac{V^2}{R_L^2 (1+x)^2} \cdot R_L =$$

$$= \frac{V^2}{(1+x)^2} \cdot \frac{R_i}{R_L} \cdot \frac{1}{R_i} = \frac{V^2}{R_i} \cdot \frac{x}{(1+x)^2}$$

where $x = \frac{R_i}{R_L}$

since V and R_i are fixed, we just need to maximize

$$f(x) = \frac{x}{(1+x)^2} = x(1+x)^{-2}$$

$$f'(x) = (1+x)^{-2} - 2x(1+x)^{-3} = 0$$

$$\frac{1}{(1+x)^2} = \frac{2x}{(1+x)^3}$$

$$1+x = 2x$$

$$\boxed{x = 1}$$