

Homework 9

11.7 A

$$V = V_0 \sin \omega t$$

$$a. Z = \sqrt{R^2 + \omega^2 L^2}$$

$$I_0 = \frac{V_0}{Z} = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}}$$

$$I(t) = I_0 \cos(\omega t - \theta)$$

$$I(t) = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t - \theta)$$

where $\tan \theta = \frac{\omega L}{R}$

b. The inductance and the resistance are in series, so the current is the same, the phase angle is 0.

c. V_R is $\frac{\pi}{2}$ behind V_L .

$$d. V_R = R I_0 = \frac{R V_0}{\sqrt{R^2 + \omega^2 L^2}}$$

$$V_L = X_L I_0 = \frac{\omega L V_0}{\sqrt{R^2 + \omega^2 L^2}}$$

e. \vec{V}_R and \vec{V}_L are perpendicular,
that is why $|V_R| + |V_L| \neq V_0$

but

$$V_0^2 = V_R^2 + V_L^2$$

$$V_0^2 = \frac{R^2 V_0^2}{R^2 + \omega^2 L^2} + \frac{\omega^2 L^2 V_0^2}{R^2 + \omega^2 L^2}$$



11.1 B a. $Z = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$

$$I_0 = \frac{V_0}{Z} = \frac{V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$$

$$I(t) = I_0 \cos(\omega t - \theta)$$

$$I(t) = \frac{V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \cos(\omega t - \theta)$$

where $\tan \theta = \frac{-\frac{1}{\omega C}}{R} = -\frac{1}{\omega C R}$

b. The currents are the same, phase angle is 0.

c. V_R is $\frac{I_0}{2}$ ahead of V_C .

$$d. V_R = R I_0 = \frac{R V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$$

$$V_C = X_C I_0 = \frac{V_0}{\omega C \sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$$

e. \vec{V}_R and \vec{V}_C are perpendicular

so $|V_R| + |V_C| \neq V_0$ but

$$V_R^2 + V_C^2 = V_0^2$$

$$V_0^2 = \frac{R^2 V_0^2}{R^2 + \frac{1}{\omega^2 C^2}} + \frac{V_0^2}{\omega^2 C^2 (R^2 + \frac{1}{\omega^2 C^2})}$$



11.1 c a. $L = 2\text{H}$

$$f = 60\text{ Hz}$$

$$X_L = \omega L = 2\pi f L = \underline{754\ \Omega}$$

b. $C = 50 \cdot 10^{-6}\text{ F}$


$$f = 60\text{ Hz}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \underline{53\ \Omega}$$

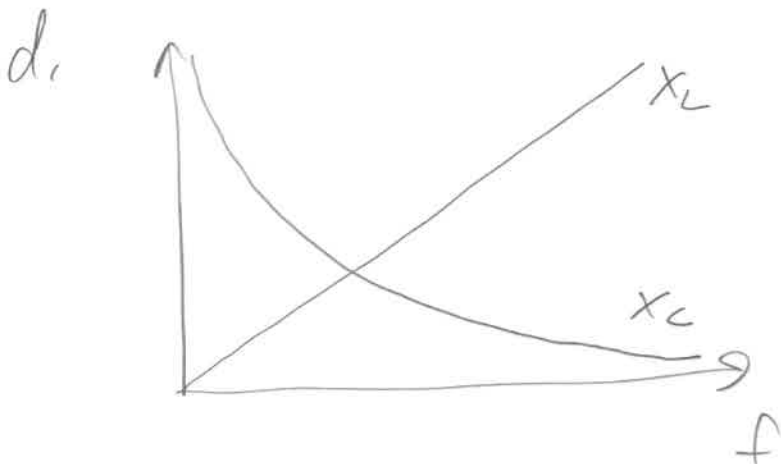c. $2\pi f L = \frac{1}{2\pi f C}$

$$(2\pi f)^2 = \frac{1}{LC}$$

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \underline{15.9\text{ Hz}}$$



$$\underline{11.9 \text{ E}} \quad R = 400 \Omega$$

$$f = 60 \text{ Hz}$$

$$V_{\text{eff}} = 80 \text{ V}$$

$$I_{\text{eff}} = 0,1 \text{ A}$$

$$a. \quad Z = \frac{V_{\text{eff}}}{I_{\text{eff}}} = \underline{800 \Omega}$$

$$b. \quad P = V_{\text{eff}} I_{\text{eff}} \cos \theta$$

$$\cos \theta = \frac{R}{Z} = \frac{1}{2}$$

$$P = \underline{4 \text{ W}}$$

$$c. \quad Z = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$\frac{1}{\omega^2 C^2} = Z^2 - R^2$$

$$C = \frac{1}{\omega \sqrt{Z^2 - R^2}} = \frac{1}{251 \text{ f} \sqrt{Z^2 - R^2}}$$

$$\underline{C = 3,83 \cdot 10^{-6} \text{ F}}$$

11.3 A a. $\omega_0 = \sqrt{\frac{1}{LC}}$

b. $Z_0 = \sqrt{R^2 + \left(\omega_0 L - \frac{1}{\omega_0 C}\right)^2} = R$ ($R = R_1 + R_2$)

$$I_0 = \frac{V_0}{Z_0} = \frac{V_0}{R} = \frac{V_0}{R_1 + R_2}$$

c. $I = \frac{I_0}{2} \rightarrow Z = 2Z_0 = 2R$

$$\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = 2R$$

$$\omega L - \frac{1}{\omega C} = \pm \sqrt{3} R$$

$$\omega^2 LC \mp \sqrt{3} R \omega C - 1 = 0$$

$$\omega = \frac{\pm \sqrt{3} R C \pm \sqrt{3 R^2 C^2 + 4 L C}}{2 L C}$$


Need to choose only positive solutions:

$$\omega = \frac{\pm \sqrt{3} R C + \sqrt{3 R^2 C^2 + 4 L C}}{2 L C}$$


d. $\mathcal{E} = \infty$ for $\omega = 0$ or $\omega = \infty$

for which $I = 0$.

11.9 A

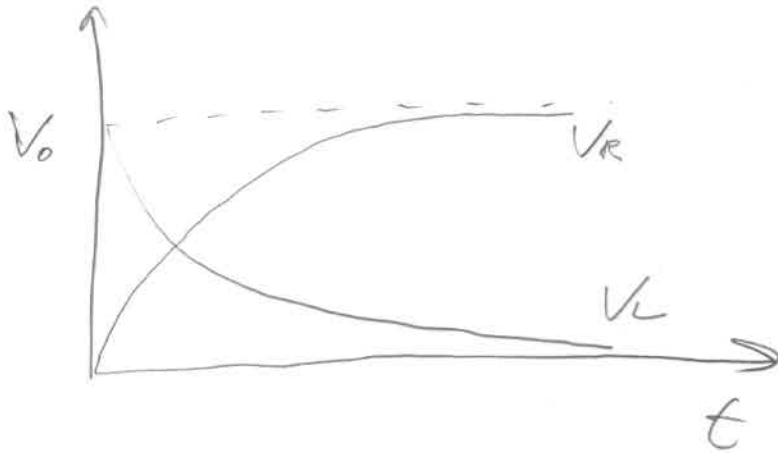

$V_R + V_L$ is always V_0 :

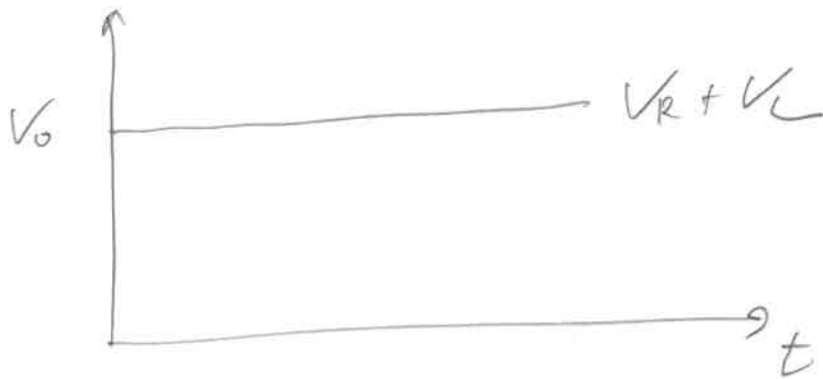

$$b. V_L(t) = V_0 e^{-t/\tau}$$

$$V_R(t) = V_0 (1 - e^{-t/\tau})$$

$$\text{where } \tau = \frac{L}{R}$$

$$V_L = V_R \Rightarrow e^{-t/\tau} = 1 - e^{-t/\tau}$$

$$e^{-t/\tau} = \frac{1}{2}$$

$$t/\tau = \ln 2$$

$$t = \tau \ln 2 = \frac{L}{R} \ln 2$$


C. $\tau = \frac{L}{R}$

11.4 C See week 6!

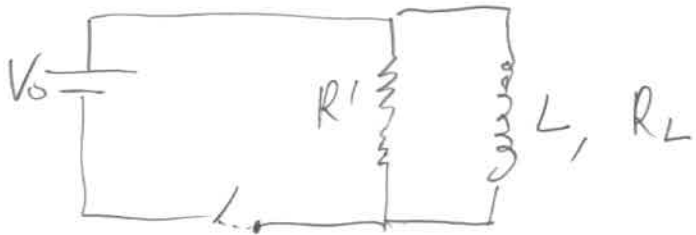11.4 D $L = 10 \text{ mH}$

$$R_L = 100 \Omega$$

$$V_0 = 20 \text{ V}, \quad V_{\text{max}} = 100 \text{ V}$$



After opening the switch we have a circuit:



with the same initial current as before opening the switch:

$$I_0 = \frac{V_0}{R_L} = 0.2 \text{ A}$$

The voltage across the coil is the same as the voltage across R' , which initially is

$$V = I_0 R' \leq V_{\max}$$

$$R' \leq \frac{V_{\max}}{I_0} = \underline{500 \Omega}$$

$$I(t) = I_0 e^{-t/\tau}$$

$$\text{with } \tau = \frac{L}{R_{\text{total}}} = \frac{L}{R_L + R'}$$

$$\frac{dI}{dt} = - \frac{I_0}{\tau} e^{-t/\tau}$$

Initially:

$$\left| \frac{dI}{dt} \right|_{t=0} = \frac{I_0}{\tau} = \frac{I_0 R_{\text{total}}}{L} = \underline{12 \frac{\text{A}}{\text{s}}}$$