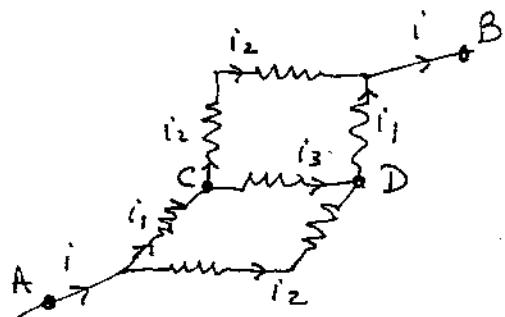


Problem 1

$$i = i_2 + i_3$$

$$i_1 R + i_3 R = 2i_2 R \Rightarrow i_1 + i_3 = 2i_2$$

$$\Rightarrow i_3 = 2i_2 - i_1$$

$$i_1 = i_2 + 2i_2 - i_1 \Rightarrow 2i_1 = 3i_2 \Rightarrow \boxed{i_2 = \frac{2}{3}i_1, i_3 = \frac{1}{3}i_1}$$

$$i = i_1 + i_2 = \frac{5}{3}i_1 \Rightarrow \boxed{i_1 = \frac{3}{5}i}$$

If  $V_{AB}$  the potential difference between points A and B,

$$V = i_1 R + 2i_2 R \quad (\text{equivalently } V = i_1 R + i_3 R + i_1 R)$$

$$\Rightarrow V = i_1 R + \frac{4}{3}i_1 R = \frac{7}{3}i_1 R = \frac{7}{3} \cdot \frac{3}{5}i_1 R = \frac{7}{5}R \cdot i$$

$$\Rightarrow \frac{V}{i} = \frac{7}{5}R \Rightarrow \boxed{R_{\text{eq}} = \frac{7}{5}R} \text{ equivalent resistance}$$

$$(b) \text{ Voltage drop between A and C: } V_{AC} = i_1 R = \frac{3}{5}i R$$

$$\text{Total voltage drop between A and B: } V_{AB} = i R_{\text{eq}} = \frac{7}{5}i R$$


$$\text{So } V_{AC} = \frac{3}{7}V_{AB}; \text{ given that } V_{AB} = 14V \Rightarrow \boxed{V_{AC} = 6V}$$

Voltage drop between D and B = 6 V, by symmetry  $\Rightarrow$  between C and D = 2 V

$$\text{Or: } V_{CD} = i_3 R = \frac{1}{3}i_1 R = \frac{1}{5}i R = \frac{1}{7}V_{AB} = 2V$$

$$\text{Hence, } \boxed{V_A = 14V, V_C = 8V, V_D = 6V, V_B = 0}$$

## Problem 2

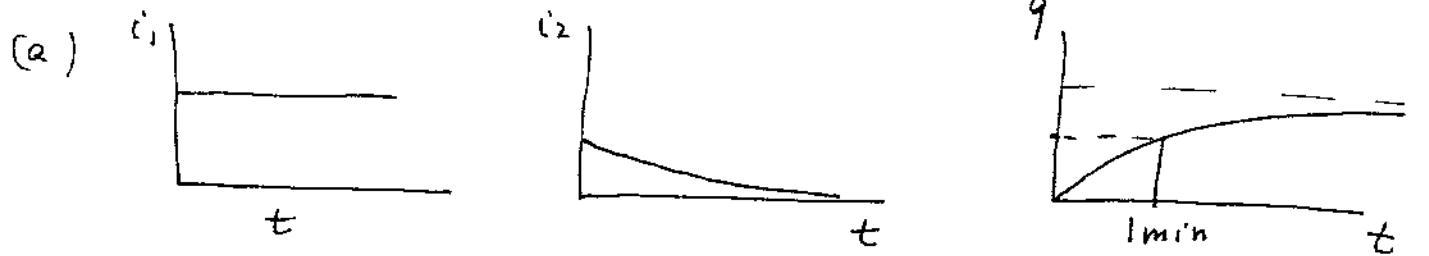

(b) right after switch is closed:

$$i_1 = \frac{E}{R} , \quad i_2 = \frac{E}{2R} \quad (\text{capacitor acts as a short-circuit, no potential drop})$$

(c) 1 minute after S is closed, the charge in capacitor is  $\frac{1}{2}$  of what it is after a long time (1 hour). For  $i_1$ , no change.  $i_1 = \frac{E}{R}$  still.

For  $i_2$ , we have a circuit with emf  $E$  and resistance  $2R$ . So the charge in capacitor is

$$q(t) = C E (1 - e^{-t/2RC}) ; \text{ for } t = t_0 = 1\text{ min}, q(t_0) = \frac{1}{2} q(t=\infty)$$

$$\Rightarrow e^{-t_0/2RC} = \frac{1}{2} . \quad \text{The current is}$$

$$i_2(t_0) = \frac{d q}{dt} = - \frac{E}{2R} e^{-t_0/2RC} = - \frac{E}{4R} \Rightarrow i_2 = \frac{E}{4R} \text{ half of value at } t=0$$

(d) When the switch is opened again, capacitor discharges across a resistance  $= 3R$ . So charge as function of time is:

$$q(t) = q_0 e^{-t/3RC} = \frac{q_0}{2} \quad (\text{charge goes from } q_0 = 100C \text{ to } 50C)$$

$$\Rightarrow e^{-t/3RC} = \frac{1}{2} = e^{-t_0/2RC} \Rightarrow t = \frac{3}{2} t_0$$

$$\text{since } t_0 = 1\text{ min} \Rightarrow t = 90 \text{ seconds}$$

### Problem 3

Magnetic field at center of circular loop:  $B = \frac{\mu_0 i}{2R}$  ( $R$  = radius)

Mag. field of  $\infty$  straight wire at distance  $r$ :  $B = \frac{\mu_0 i}{2\pi r}$

(a) We need to add field from  $\frac{1}{2}$  circular loops of radii  $b$  and  $2b$ ,


$$B = \frac{1}{2} \left( \frac{\mu_0 i}{2b} + \frac{\mu_0 i}{4b} \right) \Rightarrow B = \frac{3\mu_0 i}{8b} \text{ points } \underline{\text{into paper}}$$

(b) We have half of  $\infty$  wire twice, distances  $a$  and  $2a$ , in opposite directions:

$$B = \frac{1}{2} \left( \frac{\mu_0 i}{2\pi a} - \frac{\mu_0 i}{4\pi a} \right) \Rightarrow B = \frac{\mu_0 i}{8\pi a} \text{ points } \underline{\text{out of paper}}$$

(since closer wire gives bigger field)

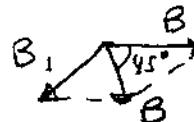(c) The fields are of equal magnitude at  $90^\circ$  angle



$$B_1 = \frac{\mu_0 i}{2R} \quad ; \quad B = \sqrt{2} B_1 \Rightarrow$$

$$B = \frac{\mu_0 i}{\sqrt{2} R}$$

points to the right and out of the paper at  $45^\circ$  as shown above