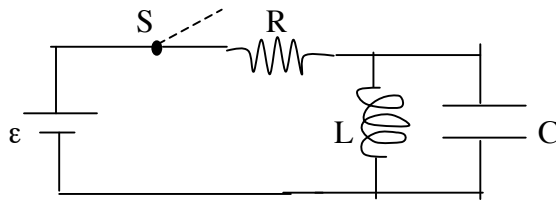


Problem 1 (10 pts)



In the circuit in the figure, $\epsilon=100\text{V}$, $R=5\Omega$, $L=10\text{mH}$ and $C=10\text{mF}$. The switch S has been closed for a long time. At time $t=0$ the switch S is opened.


- What is the current through the resistor right before S is opened?
- What is the charge in the capacitor right before S is opened?
- What is the energy stored in the inductor right before S is opened?
- What is the maximum charge that will be stored in the capacitor after S is opened?
- How long after S is opened will the capacitor for the first time have maximum charge?

Problem 2 (10 pts)

An alternating emf of amplitude 100V and angular frequency $\omega=100\text{s}^{-1}$ is connected in series with a 2Ω resistance, a 50mH inductor and a capacitor. The current in this circuit is in phase with the emf.

- What is the value of the capacitance of this capacitor?
- What is the impedance of this circuit and the amplitude of the current?
- What is the maximum voltage across the inductor?

Problem 3 (10 pts)

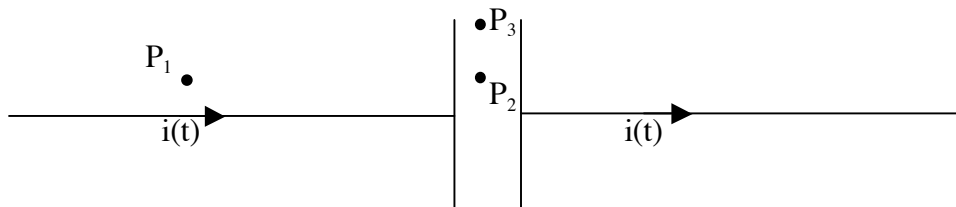

The capacitor in the figure is being charged by a straight wire carrying current $i(t)$ connected to a circuit not shown. The capacitor is made of circular plates of radius R that are at distance $d=1\text{cm}$ from each other. The point P_2 is between the capacitor plates at distance $R/2$ from the center, the point P_3 is at the edge of the capacitor (distance R from the center). The point P_1 is at distance $R/2$ from the wire far from the capacitor. The magnetic field at point P_1 at a certain instant is 0.4mT when the current is 200A . At that instant:

- What is the magnitude of the magnetic field at point P_2 ?
- What is the magnitude of the magnetic field at point P_3 ?
- What is the value of dE/dt , where E is the electric field between the capacitor plates? Give your answer in $\text{V}/(\text{m s})$. Use $\epsilon_0=8.85 \times 10^{-12} \text{C}^2/(\text{Nm}^2)$, $\mu_0=4\pi \times 10^{-7} \text{T m /A}$.