

Problem 1

$$(a) \quad i = \frac{\mathcal{E}}{R} = \frac{100 \text{ V}}{5 \Omega} = 20 \text{ A}$$

$$(b) \quad Q = 0$$

$$(c) \quad U = \frac{1}{2} L i^2 = \frac{1}{2} \cdot 10 \cdot 10^{-3} \cdot 20^2 \text{ J} = \frac{1}{2} \cdot \frac{400}{100} \text{ J}$$

$$\Rightarrow U = 2 \text{ J}$$

(d) When all the energy is in the capacitor

$$U = \frac{Q^2}{2C} \Rightarrow Q^2 = 2CU = 2 \cdot 10 \cdot 10^{-3} \cdot 2 \left(= \frac{4}{100} \right) \text{ C}^2$$


$$\Rightarrow Q = 0.2 \text{ C}$$

(e) Frequency of oscillation is $\omega = \frac{1}{\sqrt{LC}}$

$$\omega = 2\pi f = \frac{2\pi}{T} \quad \text{Charge does}$$

$$T = \frac{2\pi}{\omega}$$

So maximum charge is at $T/4 \equiv t$

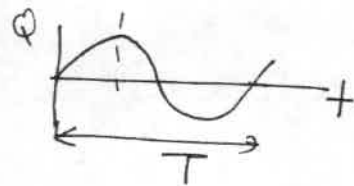

$$t = \frac{T}{4} = \frac{2\pi}{4\omega} = \frac{2\pi}{4} \sqrt{LC} = \frac{\pi}{2} \sqrt{10 \cdot 10^{-3} \cdot 10 \cdot 10^{-3}} \text{ s} =$$

$$= \frac{\pi}{2} \cdot 10^{-2} \text{ s} = \frac{\pi}{200} \text{ s} \Rightarrow t = 0.0157 \text{ s}$$

Problem 2

$$E = V_0 \cos \omega t$$

$$i = I_0 \cos(\omega t - \theta)$$

$$\tan \theta = \frac{\omega L - 1/\omega C}{R}$$

$$I_0 = \frac{V_0}{Z}, \quad Z = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

(a) $\theta = 0 \Rightarrow$

$$\omega L = \frac{1}{\omega C} \Rightarrow C = \frac{1}{\omega^2 L} = \frac{1}{100^2 \cdot 50 \cdot 10^{-3}} \text{ F} =$$

$$= \frac{1}{500} \text{ F} \Rightarrow \boxed{C = 2 \text{ mF}}$$

(b) $\boxed{Z = R = 2 \Omega}$ $\boxed{I_0 = \frac{V_0}{R} = 50 \text{ A}}$

(c) $V_L = X_L I_0 = \omega L I_0 =$

$$= 100 \cdot 50 \cdot 10^{-3} \cdot 50 \text{ V} \Rightarrow \boxed{V_L = 250 \text{ V}}$$

Problem 3

The Ampere-Maxwell law is

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 \int \vec{j} \cdot d\vec{S} + \mu_0 \epsilon_0 \int \frac{d\vec{E}}{dt} \cdot d\vec{S}$$

For point P_1 : $B_1 \cdot 2\pi r = \mu_0 i \Rightarrow \boxed{B_1 = \frac{\mu_0 i}{2\pi r}}$

For point P_2 : $B_2 \cdot 2\pi r = \mu_0 \epsilon_0 \frac{dE}{dt} \cdot \pi r^2 \Rightarrow$

$$B_2 = \frac{\mu_0 \epsilon_0}{2} \frac{dE}{dt} \cdot r \quad ; \quad E = \frac{\sigma}{\epsilon_0} = \frac{Q}{A \epsilon_0} \Rightarrow \frac{dE}{dt} = \frac{i}{A \epsilon_0} = \frac{i}{\pi R^2 \epsilon_0}$$

where $A = \pi R^2$ is the area of the capacitor plate. So,

$$B_2 = \frac{\mu_0 \epsilon_0}{2} \frac{i}{\pi R^2 \epsilon_0} r \Rightarrow \boxed{B_2 = \frac{\mu_0 i}{2\pi} \frac{r}{R^2}}$$

So for $r = \frac{R}{2}$, $B_1 = \frac{\mu_0 i \cdot 2}{2\pi R} = \frac{\mu_0 i}{\pi R}$, $B_2 = \frac{\mu_0 i}{2\pi} \frac{1}{2R} = \frac{\mu_0 i}{4\pi R} \Rightarrow$

$\Rightarrow B_2 = \frac{1}{4} B_1$, since $B_1 = 0.4 \text{ mT} \Rightarrow \boxed{B_2 = 0.1 \text{ mT}}$

(b) At point P_3 : $r = R \Rightarrow \boxed{B_3 = \frac{\mu_0 i}{2\pi R}} \Rightarrow B_3 = \frac{B_1}{2} \Rightarrow$

$$\boxed{B_3 = 0.2 \text{ mT}}$$

(c) $B_2 = \frac{\mu_0 \epsilon_0}{2} \frac{dE}{dt} \cdot r \Rightarrow \frac{dE}{dt} = \frac{2 B_2}{\mu_0 \epsilon_0 r}$; for we set $r = 1 \text{ mm}$

$$B_1 = \frac{\mu_0 i}{2\pi r} \Rightarrow r = \frac{\mu_0 i}{2\pi B_1} = \frac{4\pi \cdot 10^{-7} \cdot 200}{2\pi \cdot 0.4 \times 10^{-3}} = \frac{10^{-5}}{0.1 \cdot 10^{-3}} \text{ m} = 0.1 \text{ m} = 10 \text{ cm}$$

$$\frac{dE}{dt} = \frac{2 \cdot 0.1 \times 10^{-3}}{4\pi \cdot 10^{-7} \cdot 8.854 \cdot 10^{-12} \cdot 0.1} \frac{\text{V}}{\text{m} \cdot \text{s}} \Rightarrow \boxed{\frac{dE}{dt} = 1.8 \times 10^{14} \frac{\text{V}}{\text{m} \cdot \text{s}}}$$