



FIG. 1: Figures A, B respectively

1B quiz 2 version B

- To stun its prey, the electric eel generates a current of .8 Amp, applied across a potential difference of 650V. How much energy is deposited by the eel in its victim every 2 seconds?
  - a. 130 J
  - b. 260 J
  - c. 520 J
  - d. 1040 J
- An aluminum wire of length  $5L$  and a copper wire of length  $L$  have precisely the same resistance. The resistivity of the two materials are: aluminum,  $2.8 \times 10^{-8}\Omega - m$  and copper  $1.7 \times 10^{-8}\Omega - m$ . What is the ratio of the radius of the copper wire to the aluminum wire?
  - a. .05
  - b. .12
  - c. .35
  - d. .87
- A 1 000-V battery, a 3 000- $\Omega$  resistor and a 0.50- $\mu$ F capacitor are connected in series with a switch. The capacitor is initially uncharged. What is the value of the current the moment after the switch is closed?

- a. 0. A
  - b. .33 A
  - c. .66A
  - d. 3.0 A
4. How long is a wire made from a volume  $100 \text{ cm}^3$  of copper if its resistance is 8.5 ohms? The resistivity of copper is  $1.7 \times 10^{-8} \Omega\text{-m}$ .
- a. 7.1 m
  - b.  $1.7 \times 10^2 \text{ m}$
  - c.  $2.2 \times 10^2 \text{ m}$
  - d.  $3.0 \times 10^3 \text{ m}$
5. An electric toaster requires 1 100 W at 110 V. What is the resistance of the heating coil?
- a.  $7.5 \Omega$
  - b.  $9.0 \Omega$
  - c.  $11.0 \Omega$
  - d.  $13.0 \Omega$
6. The resistors in the circuit shown in Fig B each have a resistance of  $100 \Omega$ . What is the equivalent resistance of the circuit?
- a.  $25 \Omega$
  - b.  $50 \Omega$
  - c.  $75 \Omega$
  - d.  $100 \Omega$
7. Gold has one electron per atom available as charge carriers. The mass density of gold is  $19.3 \text{ kg/m}^3$  and its atomic weight is 197 amu. Find the drift speed of the electrons in a wire with circular cross section of radius  $3 \text{ mm}$  and which is carrying a current of carrying .1A.

- a.  $1.4 \times 10^{-4}$  m/s
- b.  $3.7 \times 10^{-4}$  m/s
- c.  $5.9 \times 10^{-5}$  m/s
- d.  $2.7 \times 10^{-2}$  m/s

8. How much current flows through the central resistor in Fig A shown above?

- a. .55 A
- b. .67 A
- c. .33 A
- d. 1.11 A