



FIG. 1: Figures A, B respectively

1B quiz 2 version C

1. How long is a wire made from a volume 100 cm^3 of copper if its resistance is 8.5 ohms?

The resistivity of copper is $1.7 \times 10^{-8} \Omega\text{-m}$.

- a. 7.1 m
- b. 1.7×10^2 m
- c. 2.2×10^2 m
- d. 3.0×10^3 m

2. How much current flows through the central resistor in Fig A shown above?

- a. .55 A
- b. .67 A
- c. .33 A
- d. 1.11 A

3. To stun its prey, the electric eel generates a current of .8 Amp, applied across a potential difference of 650V. How much energy is deposited by the eel in its victim every 2 seconds?

- a. 130 J
- b. 260 J
- c. 520 J

- d. 1040 J
4. An aluminum wire of length $5L$ and a copper wire of length L have precisely the same resistance. The resistivity of the two materials are: aluminum, $2.8 \times 10^{-8} \Omega - m$ and copper $1.7 \times 10^{-8} \Omega - m$. What is the ratio of the radius of the copper wire to the aluminum wire?
- a. .05
 - b. .12
 - c. .35
 - d. .87
5. A 1 000-V battery, a 3 000- Ω resistor and a 0.50- μ F capacitor are connected in series with a switch. The capacitor is initially uncharged. What is the value of the current the moment after the switch is closed?
- a. 0. A
 - b. .33 A
 - c. .66A
 - d. 3.0 A
6. The resistors in the circuit shown in Fig B each have a resistance of 100 Ω . What is the equivalent resistance of the circuit?
- a. 25 Ω
 - b. 50 Ω
 - c. 75 Ω
 - d. 100 Ω
7. Gold has one electron per atom available as charge carriers. The mass density of gold is 19.3 kg/m^3 and its atomic weight is 197 amu. Find the drift speed of the electrons in a wire with circular cross section of radius 3 mm and which is carrying a current of carrying .1A.

- a. 1.4×10^{-4} m/s
- b. 3.7×10^{-4} m/s
- c. 5.9×10^{-5} m/s
- d. 2.7×10^{-2} m/s

8. An electric toaster requires 1 100 W at 110 V. What is the resistance of the heating coil?

- a. 7.5Ω
- b. 9.0Ω
- c. 11.0Ω
- d. 13.0Ω