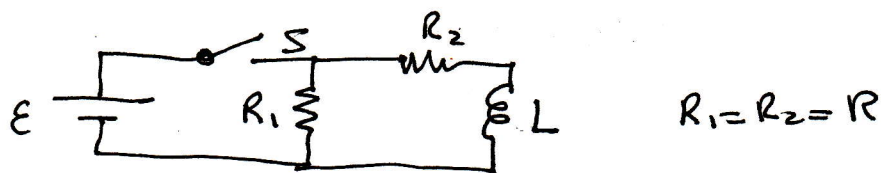



Problem 1

(a) The current through R_2 is given by

$$I = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau_L}) \quad \text{with } \tau_L = L/R.$$

So at $t = t_0$: $1 - e^{-t_0/\tau_L} = \frac{2}{3} \Rightarrow e^{-t_0/\tau_L} = \frac{1}{3} \Rightarrow$
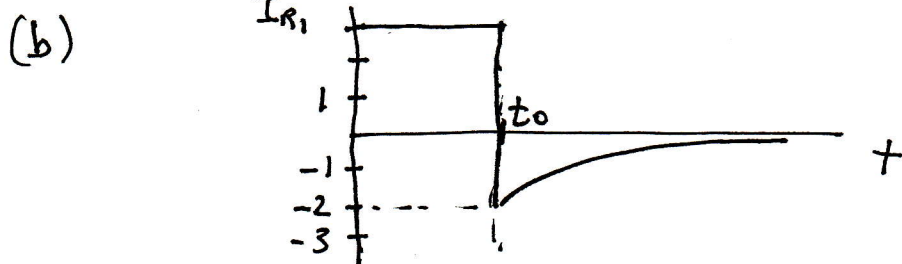
$$\ln \frac{t_0}{\tau_L} = \ln 3 \Rightarrow \boxed{t_0 = \frac{L}{R} \ln 3 = 1.1 \frac{L}{R}}$$



note: when S is opened again, I_{R_1} changes sign and takes the value $2A$, same as through L .

(c) After t_0 , current through R_1 is given by

$$I_{R_1} = I_0 e^{-t_1/\tau_L'} \quad \text{with } I_0 = 2A \text{ and } \tau_L' = \frac{L}{2R}$$

So it will be $= 1A$ for $e^{-t_1/\tau_L'} = \frac{1}{2} \Rightarrow$

$$\frac{t_1}{\tau_L'} = \ln 2 \Rightarrow t_1 = \frac{L}{2R} \ln 2. \quad \text{Now this } t_1 \text{ is measured from } t_0$$

on. The total time is $t = t_0 + \frac{L}{2R} \ln 2$. Since $t_0 = \frac{L}{R} \ln 3$

$$\boxed{t = t_0 + t_0 \frac{\ln 2}{2 \ln 3} = t_0 \left(1 + \frac{\ln 2}{2 \ln 3} \right) = 1.315 t_0}$$

Problem 2

$$(a) P = I_{rms} V_{rms} = V_{rms}^2 / R \Rightarrow$$

$$R = V_{rms}^2 / P = 120^2 / 75 \Omega \Rightarrow \boxed{R = 192 \Omega}$$

(b) With the capacitor in series, the impedance is

$$|Z| = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}$$

we have $\omega = 2\pi f$, $f = 60 \text{ Hz} \Rightarrow \omega = 377 \text{ s}^{-1} \Rightarrow$ with $C = 5 \mu\text{F}$,

$$\Rightarrow \frac{1}{\omega C} = \frac{1}{377 \times 5 \times 10^{-6}} \Omega = 530 \Omega$$

$$\Rightarrow |Z| = \sqrt{192^2 + 530^2} \Omega = 564 \Omega$$

The power is now $P = V_{rms}^2 / |Z| \cos \phi = I_{rms}^2 R$

$$I_{rms} = V_{rms} / |Z| \text{ decreased by factor } 192 / 564 = 0.34$$

$$\Rightarrow \text{power decreased by } 0.34^2 = \boxed{0.116} \Rightarrow \text{now it is } \boxed{8.7 \text{ watt}}$$

Check: angle ϕ is: $\tan \phi = \frac{1/\omega C}{R} = \frac{530}{192} = 2.76 \Rightarrow \phi = 1.22$

$$\Rightarrow \cos \phi = 0.34 \leftarrow P = I_{rms} V_{rms} \cos \phi = \frac{V_{rms} (\cos \phi)^2}{R}$$

(c) With an inductor alone, to get same impedance:


$$\omega L = \frac{1}{\omega C} \Rightarrow L = \frac{1}{\omega} \frac{1}{\omega C} = \frac{530}{377} \text{ H} \Rightarrow \boxed{L = 1.405 \text{ H}}$$

(d) If this L and C are connected in series, their effect cancels

$$\text{since } Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} = R \Rightarrow \text{both there}$$

is same as initially, $\boxed{75 \text{ watts}}$

Problem 3

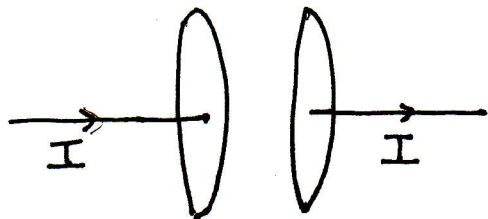

$$(a) \quad B = \frac{\mu_0 I}{2\pi r} = \frac{24\pi \times 10^{-7} \times 3}{2\pi \times 0.01} \text{ T} = 6 \times 10^{-5} \text{ T} = \boxed{0.6 \text{ Gauss}}$$

(b) Between capacitor plates:

$$\oint \vec{B} \cdot d\vec{\ell} = \mu_0 \epsilon_0 \int \frac{\partial \vec{E}}{\partial t} \cdot d\vec{a} \Rightarrow B \cdot 2\pi r = \mu_0 \epsilon_0 \frac{\partial E}{\partial t} \cdot \pi r^2 \Rightarrow$$

$$\Rightarrow B = \mu_0 \epsilon_0 \frac{\partial E}{\partial t} \cdot \frac{r}{2} \quad ; \quad E = \frac{\sigma}{\epsilon_0} = \frac{Q}{A \epsilon_0} \Rightarrow \frac{\partial E}{\partial t} = \frac{I}{A \epsilon_0} \Rightarrow$$

$$\Rightarrow B = \mu_0 I \frac{1}{A} \frac{r}{2} = \frac{\mu_0 I r}{2\pi R^2} = \frac{\mu_0 I}{2\pi r} \left(\frac{r}{R}\right)^2 \quad \text{since } R = 0.1 \text{ m and}$$

$$r = 0.01 \text{ m} \Rightarrow r/R = 0.1 \Rightarrow$$

$$B = 0.6 \times 0.1^2 \text{ G} \Rightarrow \boxed{B = 0.006 \text{ G}}$$

$$(c) \quad \frac{\partial E}{\partial t} = \frac{I}{A \epsilon_0} = \frac{3}{\pi \cdot 0.1^2 \cdot 8.85 \times 10^{-12}} \frac{\text{V}}{\text{m}\cdot\text{s}}$$

$$\Rightarrow \boxed{\frac{\partial E}{\partial t} = 1.08 \times 10^{13} \frac{\text{V}}{\text{m}\cdot\text{s}}}$$